

RLC

circuit

analysis

(~ 3 weeks)

## Intro:

Physics 116A - Analog Electronics

### Grading:

ME1 - 15%

ME2 - 15%

FE - 20%

Lab - 30%

HW - 20%

→ Late HW can be turned in (self-graded) for 50% credit at end of term.

→ Drop lowest

Text: The Art of Electronics

→ You'll love it eventually, but don't be alarmed if you don't follow everything!


Lectures: Will loosely follow text.

You should take notes while reading, in case exams are open note.
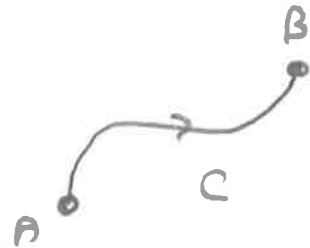
# Review:

Change in potential energy for a conservative force is

$$\Delta U(A \rightarrow B) \equiv -W_{\text{CSU}} = - \int_C \vec{F}_{\text{CSU}} \cdot d\vec{x}$$



If we choose a reference point 'A' as  $U=0$ , we can define a potential  $U(\vec{x})$

$$U(\vec{x}) = - \int_A^{\vec{x}} \vec{F}_{\text{CSU}} \cdot d\vec{x}$$

Conservative if  $\oint_{\text{closed}} \vec{F}_{\text{CSU}} \cdot d\vec{x} = 0$


From Electrostatics, we have

$$\vec{E} \equiv \frac{\vec{F}}{q}$$

$$V(\vec{x}) \equiv \frac{U(\vec{x})}{q}$$

$$\text{in } q \rightarrow 0$$

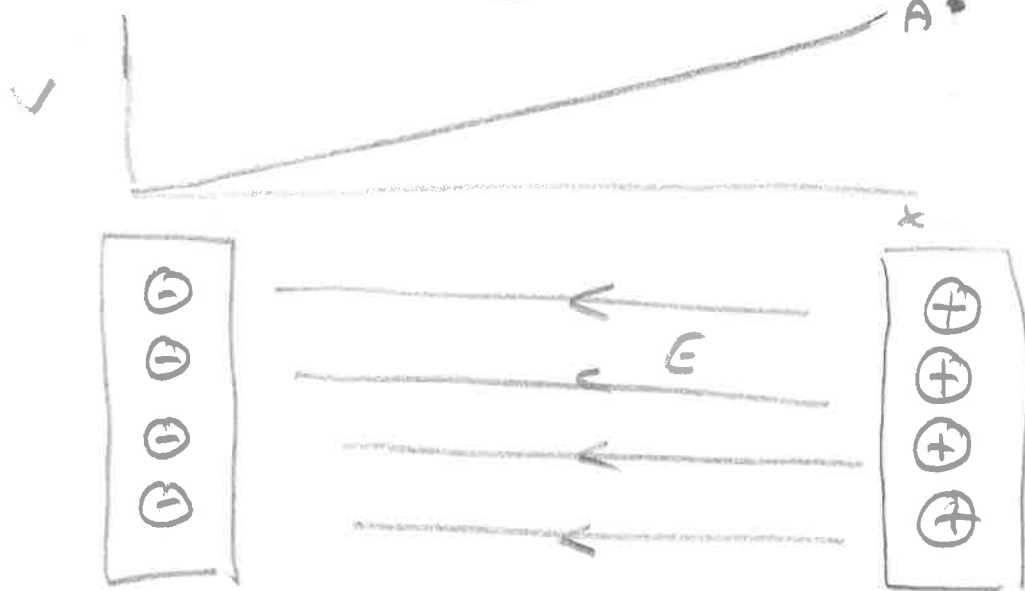
$$V(\vec{x}) = - \int_C \vec{E} \cdot d\vec{x}$$



$\ominus$  seek high  $V$

$\oplus$  seek low  $V$

X

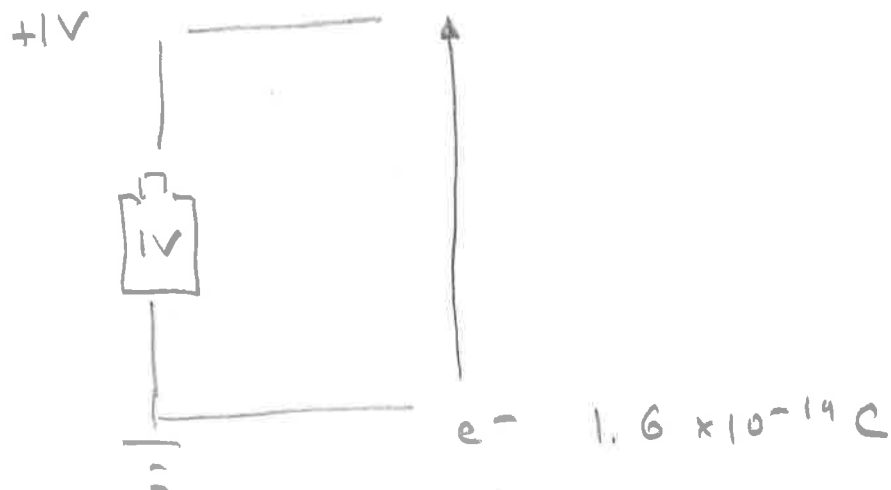

$$K = 1.6 \times 10^{-19} \text{ J} \equiv 1 \text{ eV}$$

Volt is a useful scale in many contexts.

- your car battery (12), toaster (120V)
- Kinetic energy of photo-electron ( $\sim 1 \text{ eV}$ )
- CMB energy density  $0.25 \text{ eV/cm}^3$

Current:

$$I = \frac{dq}{dt}$$

$$|A = C/s$$

Power:


$$W = \int V dq = \int V \frac{dq}{dt} dt$$

$$= \int VI dt$$

$$\frac{dW}{dt} = \boxed{VI = P}$$

Conservation Laws for circuits

KVL

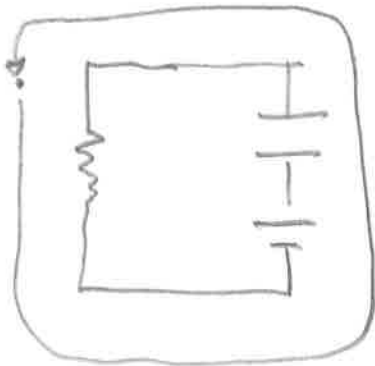

$$\sum V = 0$$




$$\sum_{\text{source}} \Delta V = \sum_{\text{load}} \Delta V$$


$$0 = \sum_{\text{source}} \Delta V + \sum_{\text{load}} (-\Delta V)$$

"Source" vs "Load"


KCL

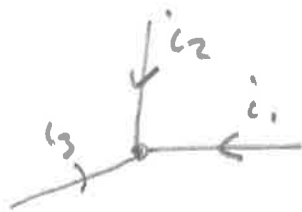


$$i_1 + i_2 + i_3 = 0$$

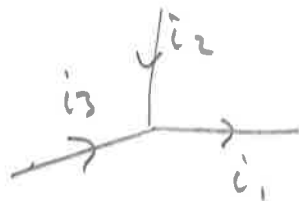

$$i_1 + i_2 = i_3$$

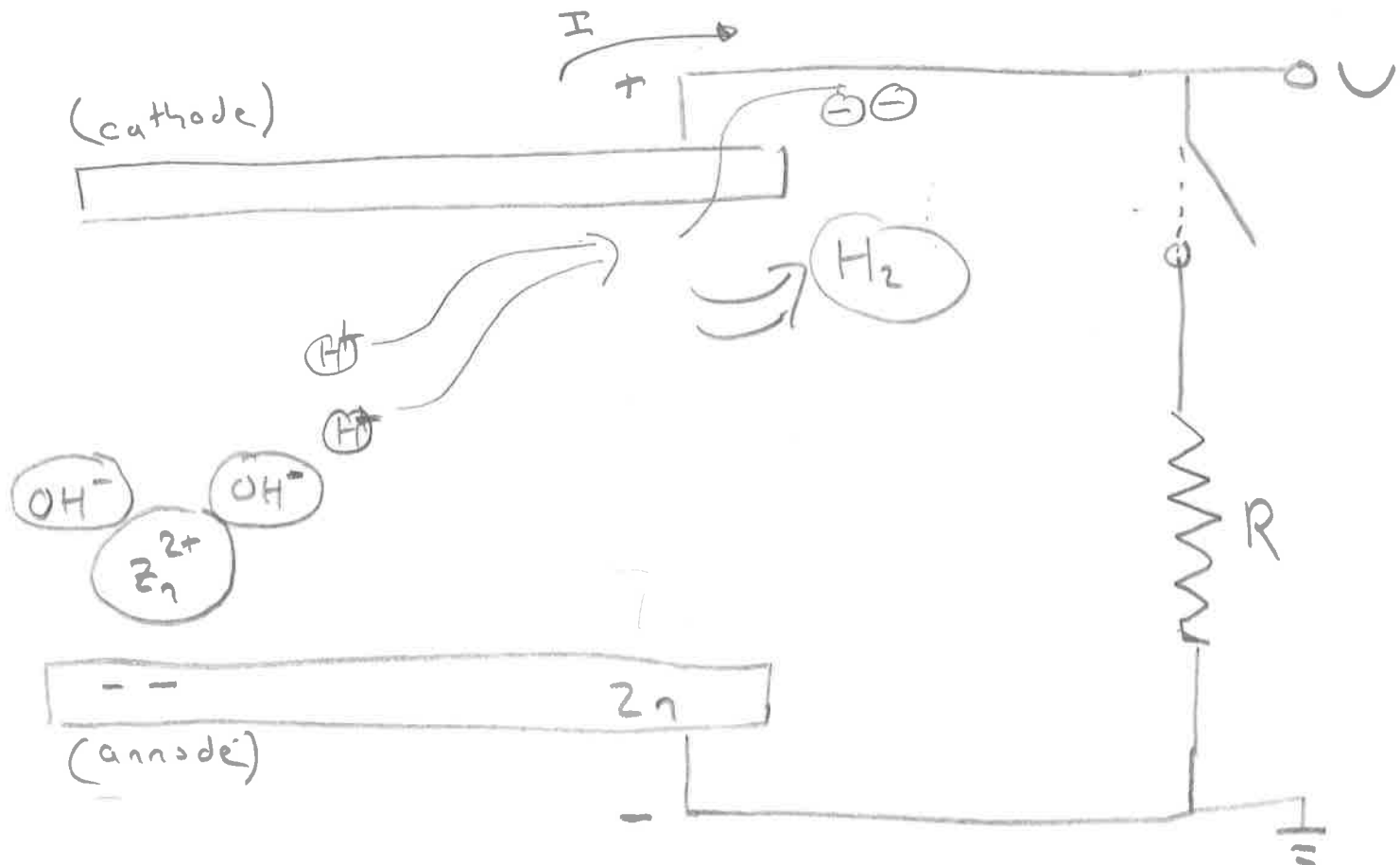

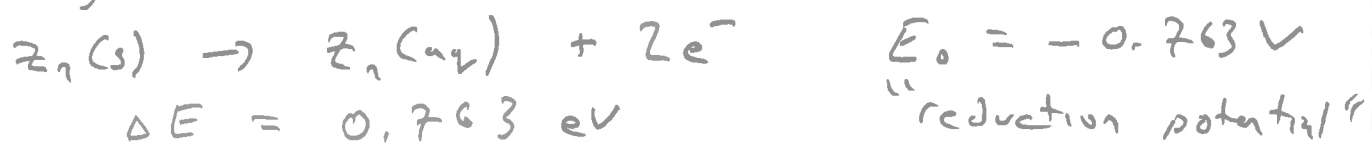- Dissolving  $Zn$  in water is energetically favorable:



- As  $H^{+}$  ions accumulate in brine,  $e^{-}$  on  $Zn$ , the voltage increases.
- When  $V \sim 0.763 \text{ V}$  dissolving  $Zn$  no longer energetically favorable (equilibrium)
- When switch closed, electrons can flow through circuit to reach Cu cathode where they combine w/  $H^{+}$  to make  $H_2$ 

$$2H^{+} + 2e^{-} \rightarrow H_2(g) \quad E_0 = 0 \text{ (ref)}$$
- Now  $Zn$  is continuously dissolved, and  $H_2$  gas bubbles out, producing the energy that drives the circuit!



## (Extra Note)

Chemistry: (Not for lecture)

Oxidation is loss of electron,

Reduction is gain of electron,

("OIL RIG")

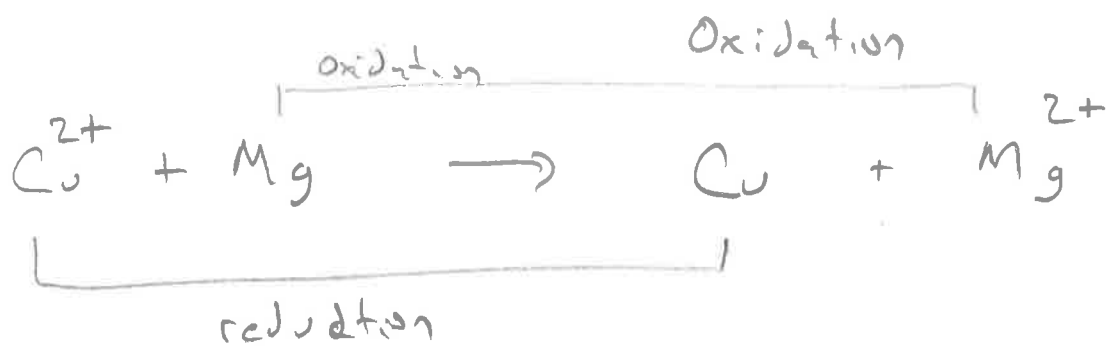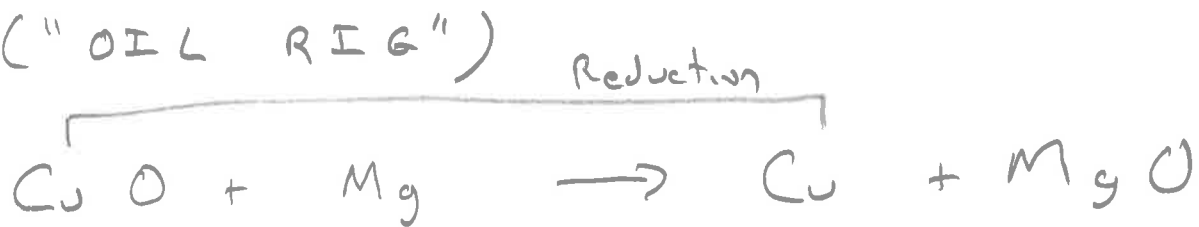

Reduction Potentials:

$E^\circ (\text{V})$



0 (reference)



- 0.763 V

\* Actual value will vary with PH.  
(Nernst Formula) \*

# Simple Drude Model

$$\langle p_0 \rangle = \text{const}$$

$$\langle \vec{p}_0 \rangle = 0 \quad (1)$$

$$\langle t - t_0 \rangle \equiv \tau \quad (2)$$

time since last collision

$$U_{\text{peak}} = \sqrt{\frac{2kT}{m}}$$

$$\neq \langle U \rangle$$

$$\langle U \rangle = \frac{2}{\sqrt{\pi}} U_{\text{peak}}$$



$$\vec{p} = \vec{p}_0 + qE(t - t_0)$$

$$\langle \vec{p} \rangle = \langle \vec{p}_0 \rangle + qE \langle t - t_0 \rangle$$

$$\langle \vec{p} \rangle = qE\tau$$

$$\langle \vec{U} \rangle = \frac{q}{m} \vec{E} \tau$$

(1) Clear simplifying assumption, since E-field imposes preferred direction. Assumption is that Thermal Equilibrium drives  $\langle \vec{p}_0 \rangle = 0$ .

(2) Factor of two confusion... might reason  $\langle t - t_0 \rangle = \frac{\tau}{2}$  if  $\tau$  is mean time between collisions... we avoid by defining  $\langle t - t_0 \rangle \equiv \tau$



## Relaxation Time Verma:

$$\frac{d\vec{p}}{dt} = 0 \quad \rightarrow \quad \frac{d\vec{p}}{dt} = -\frac{\vec{p}}{\tau}$$

Where  $\tau$  is relaxation time

$$\vec{p}(t) = \vec{p}_0 \exp(-t/\tau)$$

In presence of  $\vec{E}$ -field

$$\frac{d\vec{p}(t)}{dt} + \frac{\vec{p}}{\tau} = q\vec{E}$$

$$\frac{d}{dt} \langle \vec{p} \rangle + \frac{\langle \vec{p} \rangle}{\tau} = q\vec{E}$$

Steady state:  $\frac{d}{dt} \langle \vec{p} \rangle = 0$

$$\langle \vec{p} \rangle = q\vec{E}\tau$$

$$\langle \vec{v} \rangle = \frac{q\tau}{m}\vec{E}$$

## Current density


$$I = \frac{\Delta Q}{\Delta t}$$

$$= q \frac{\Delta N}{\Delta t}$$

$$= q n \frac{\Delta V}{\Delta t}$$

$$= q n A \frac{\Delta x}{\Delta t}$$

$$= q n A v_x$$

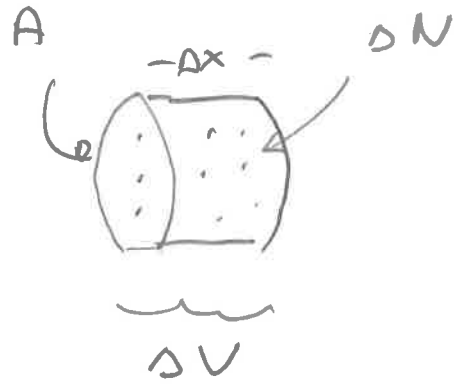

$$\frac{I}{A} = q n v_x$$

$$\vec{j} \equiv \frac{I}{A} = q n \langle \vec{v} \rangle$$

$$\vec{j} = q n \langle \vec{v} \rangle$$



$$\langle \vec{v} \rangle = \frac{q}{m} \vec{E} \tau$$

$$\vec{j} = \frac{q^2 n \tau}{m} \vec{E}$$

$$\boxed{\vec{j} = \sigma \vec{E}}$$

Linear Relationship between current  
and applied field ... (valid)

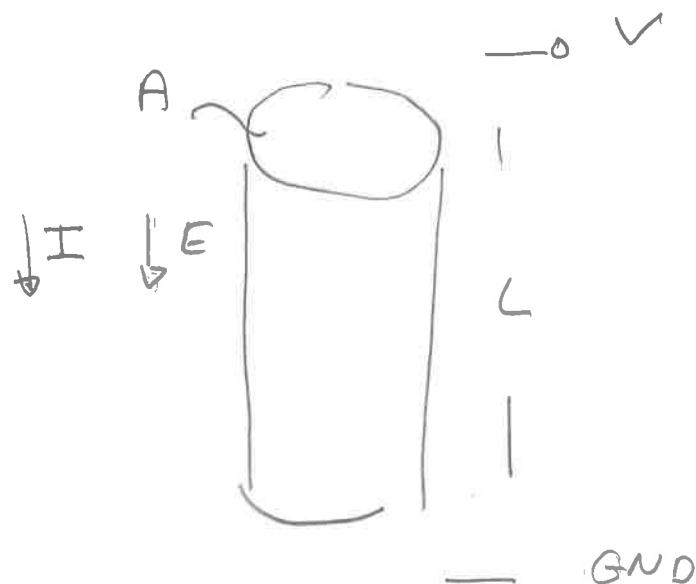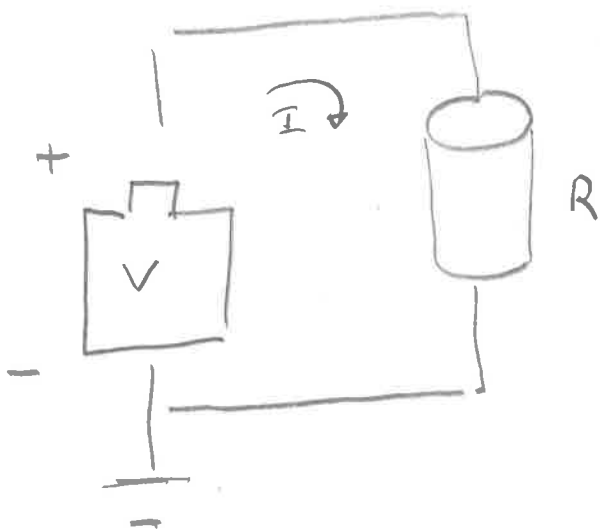( Temperature dependence ... does not work  
Failure of Drude model was evidence  
for Quantum theory )



$V = -\int \vec{E} \cdot d\vec{l}$ , so for  $E, I$  down  
in above diagram  $V = EL$

$$j = \sigma E$$

$$\frac{I}{A} = \sigma \left( \frac{V}{L} \right)$$

$$V = \frac{L}{\sigma A} I$$

$$\boxed{V = IR} \quad *$$

$$(R = \frac{L}{\sigma A})$$



$$V_2 = V_1 - IR$$


$V$  is a drop in  
direction of  
current

$$\Delta V = 0 - (V) \\ = -V$$



$$V_2 = V_1 + IR$$

## Exercise 1:

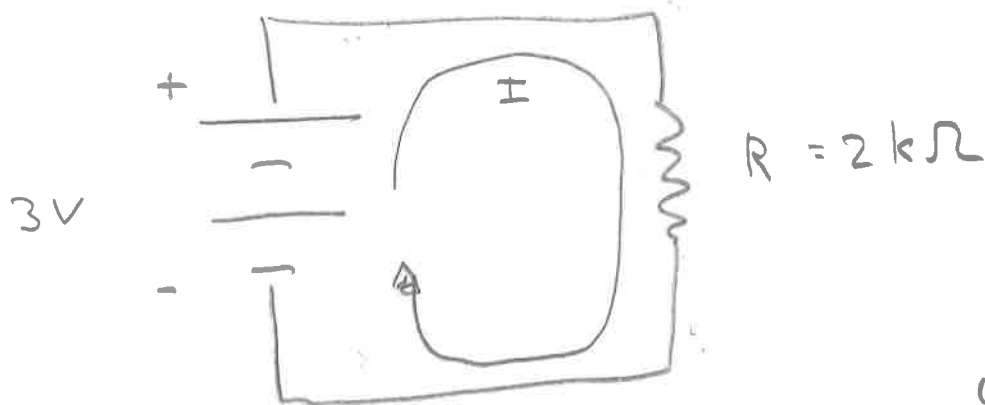

$$\text{or } +V_{\text{bat}} = +IR$$

↙

Solution:

$$\Delta V_{\text{loop}} = 0 = (+V_{\text{bat}}) - IR$$

$$\Rightarrow I = \frac{U_{\text{bat}}}{R} = \frac{3V}{2k\Omega} = \frac{3}{2} \text{ mA}$$

In other direction



$$\Delta V_{\text{loop}} = 0 = (-V_{\text{bat}}) - IR$$



$$\Rightarrow I = -\frac{U_{\text{bat}}}{R} = -\frac{3}{2} \text{ mA}$$

(best to draw positive current,  
when possible!)

\* Always draw current directions and  
note signs! \*


## Exercise 2:

1/11/1

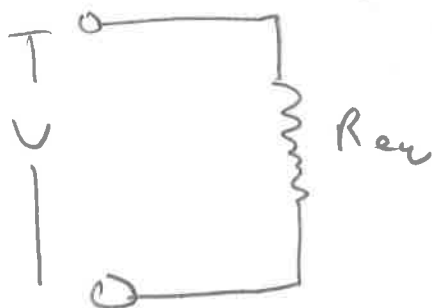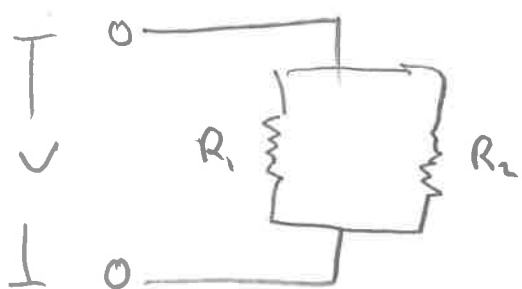

$$I = I_1 + I_2$$

$$V = I R_{eq} = I_1 R_1 = I_2 R_2$$

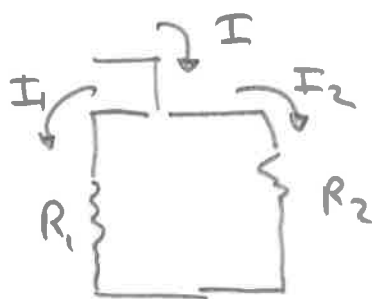

$$I R_{eq} = I_1 R_1$$

$$R_{eq} = \frac{I_1}{I} R_1$$


$$I_1 R_1 = I_2 R_2 = (I - I_1) R_2$$

$$I_1 = I \frac{R_2}{R_1 + R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} (+ \dots)$$

### Exercise 3:

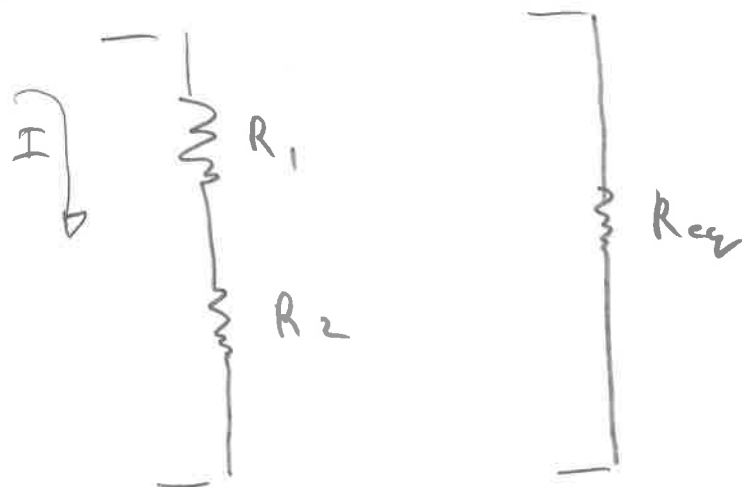

$$V = I R_{ser} = I R_1 + I R_2$$

$$R_{ser} = R_1 + R_2$$

### Exercise 4: Show from Drude model:



$$R \sim \frac{d}{A}$$

$$\text{series: } R_{ser} \sim \frac{d_1 + d_2}{A} = R_1 + R_2$$



$$\text{parallel: } \frac{1}{R_{ser}} \sim \frac{A}{L} = \frac{A_1 + A_2}{L} = \frac{1}{R_1} + \frac{1}{R_2}$$

# IV Curves and Operating Points



Load IV, assume our circuit consumes current supplied externally

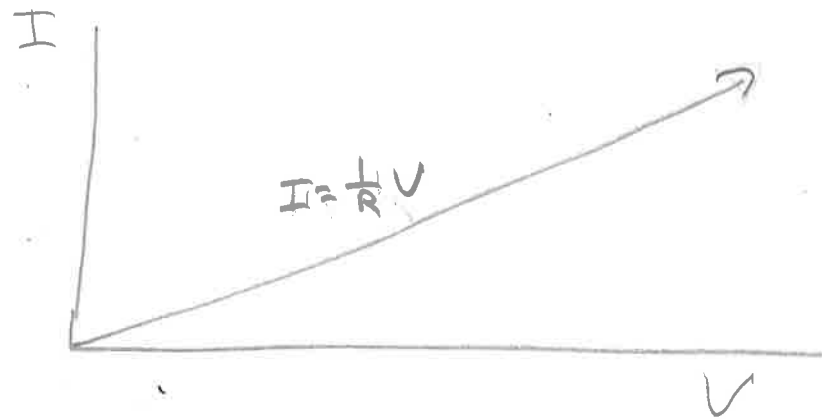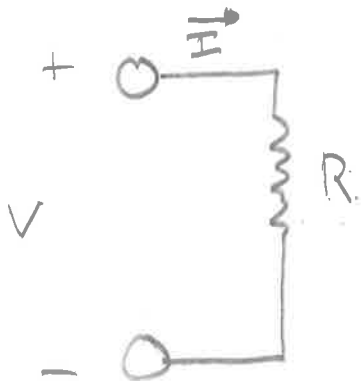

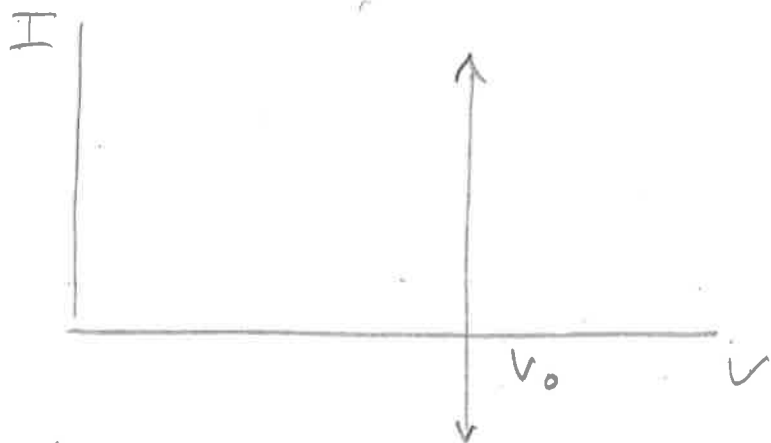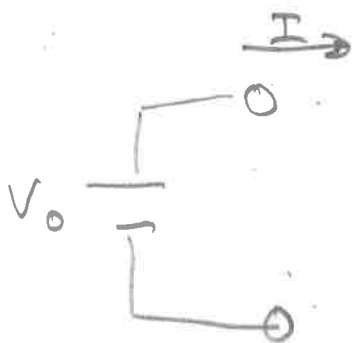Source IV: now  $I$  is assumed to be provided to load circuit







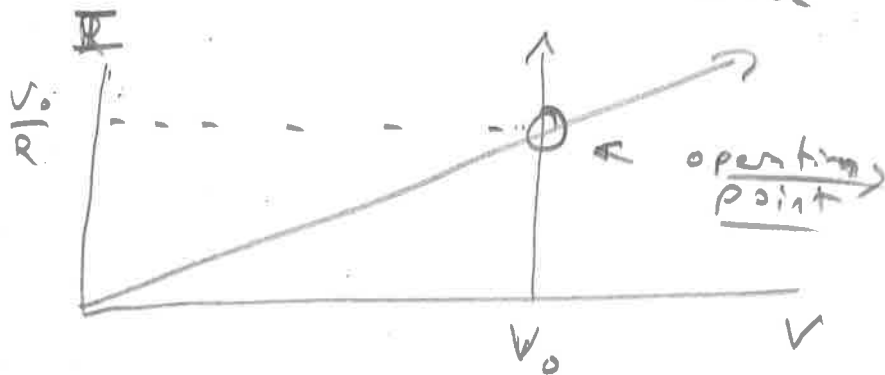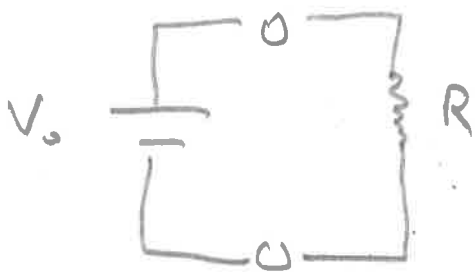Operating Point is the intersection of supply IV curve with load IV curve





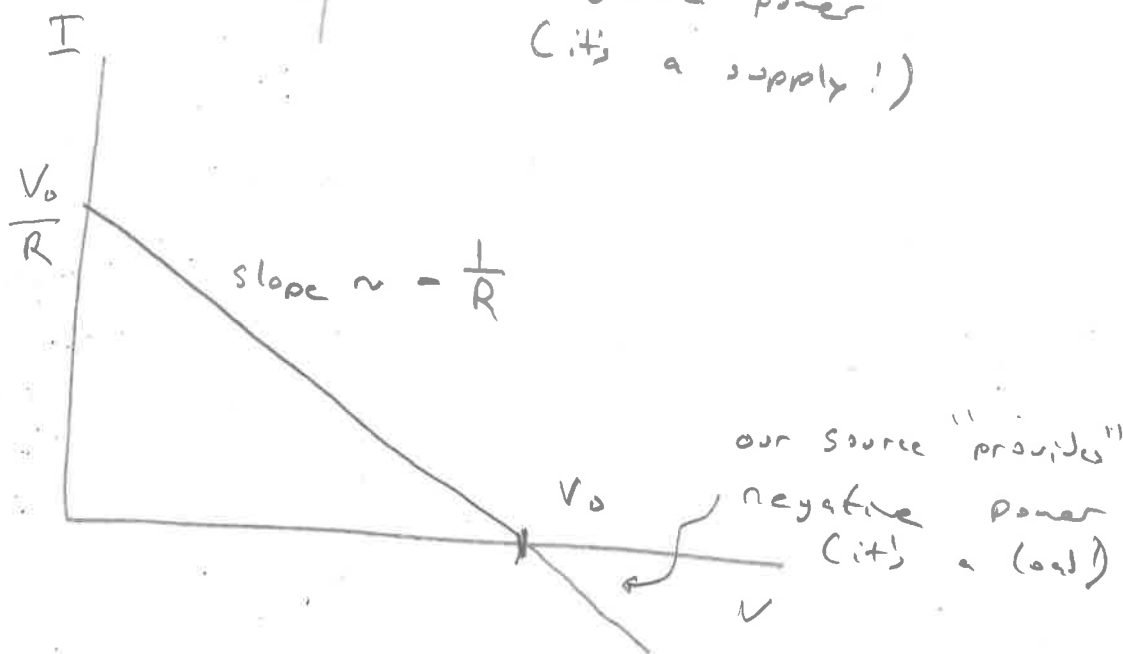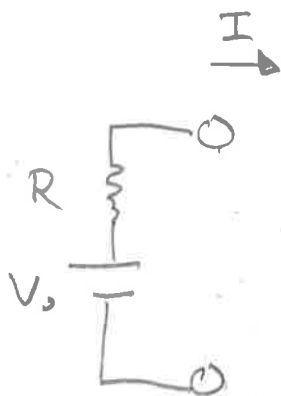
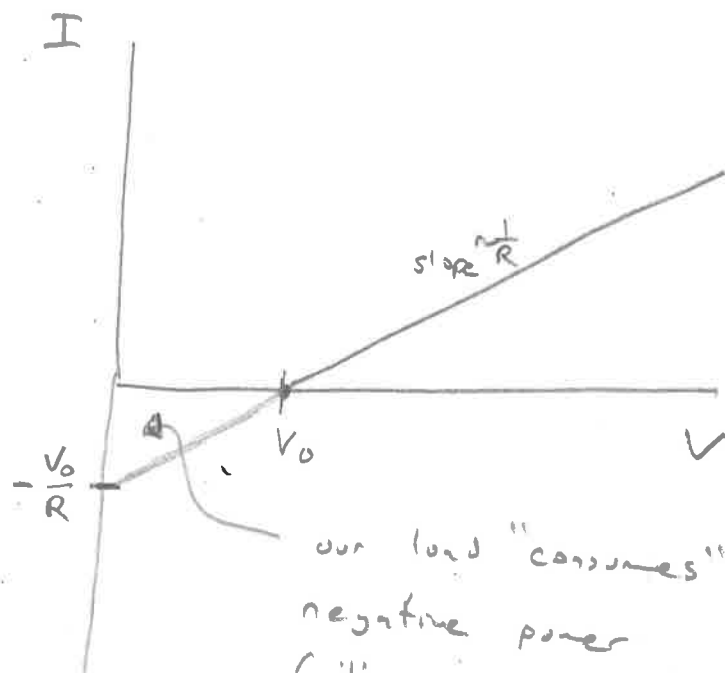
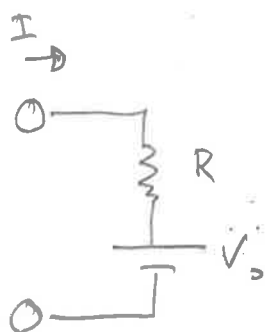
We can mix  $R$ 's and  $V$ -sources and still have Load  $I V$  and Source  $I V$



(Notice that lower plot is just upper part reflected across  $V$ -axis, since they are same with  $I \rightarrow -I$ )
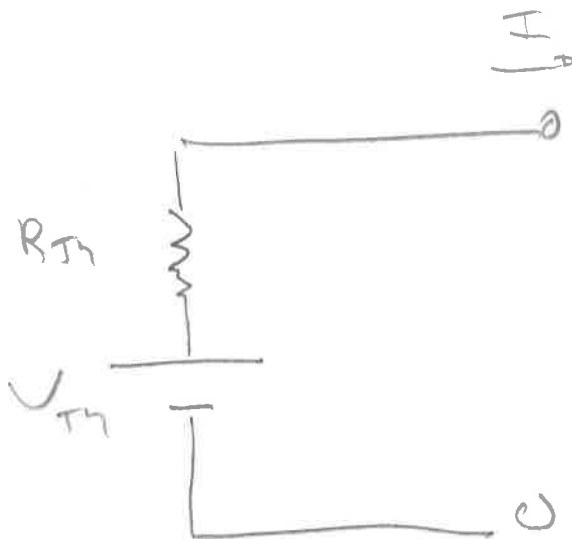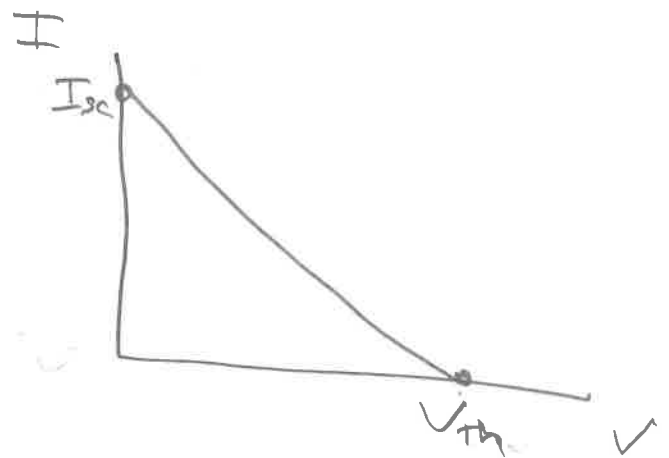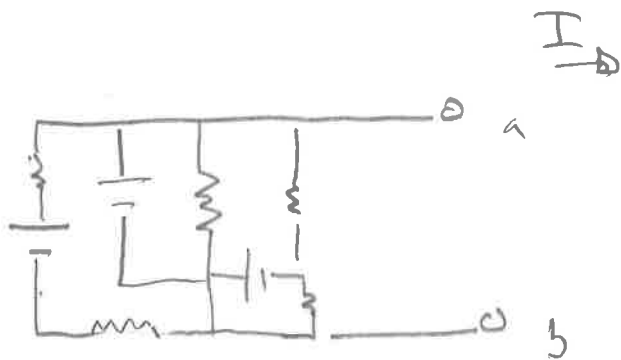
# Thevenin Equivalent Circuits

Because of superposition principle of  $E + M$ , combining linear components always has a linear response... all circuits consisting of  $R$ ,  $V$ , and  $I$ -sources have a linear  $I$   $U$  curves




$U_{th}$  is open circuit voltage



$I_{sc}$  is short circuit current

$$R_{th} = U_{th} / I_{sc}$$


# Norton Equivalent

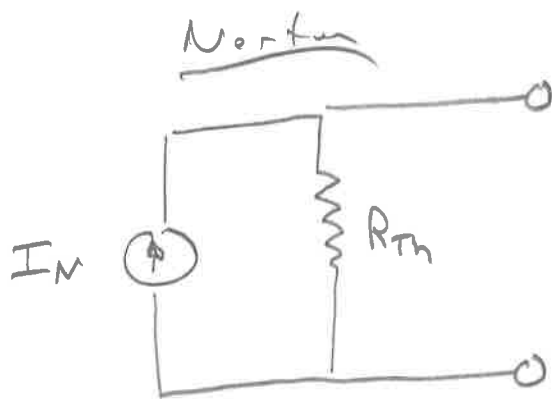

|||

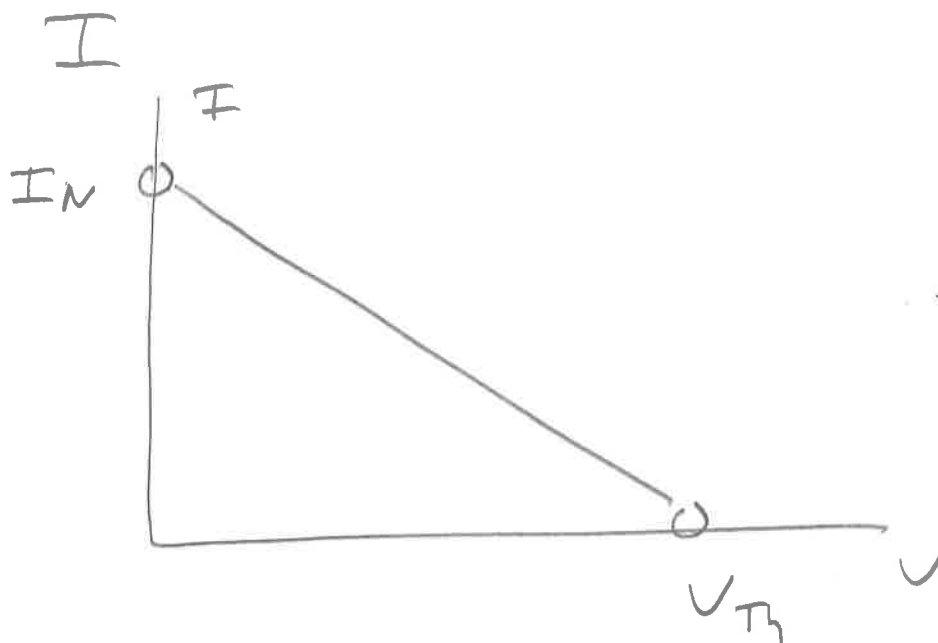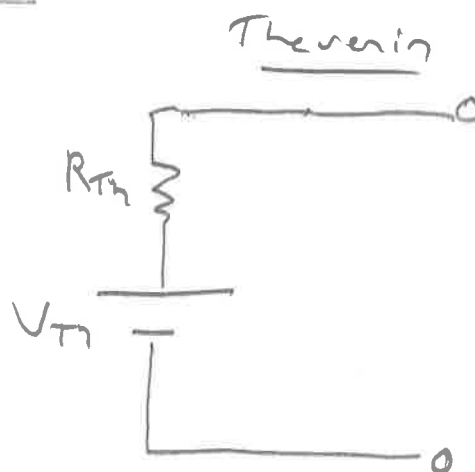

## Voltage Divider

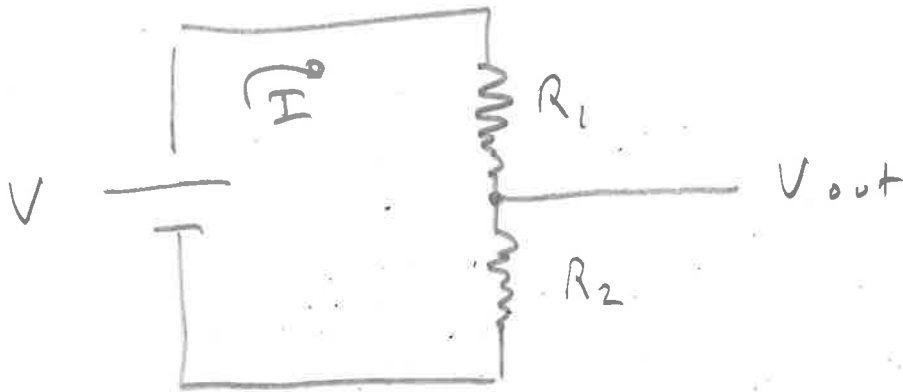


$$V = IR_1 + IR_2$$

$$V_{out} = IR_2$$

$$\frac{V_{out}}{V} = \frac{R_2}{R_1 + R_2}$$

$$V_{out} = \frac{R_2}{R_1 + R_2} V$$

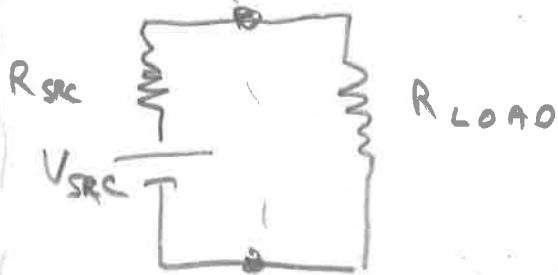
From T.E., nearly any resistive source  
makes a voltage divider:



Good designs have  
(usually)  $R_{src} \ll R_{load}$

T.E.

## Current Divider

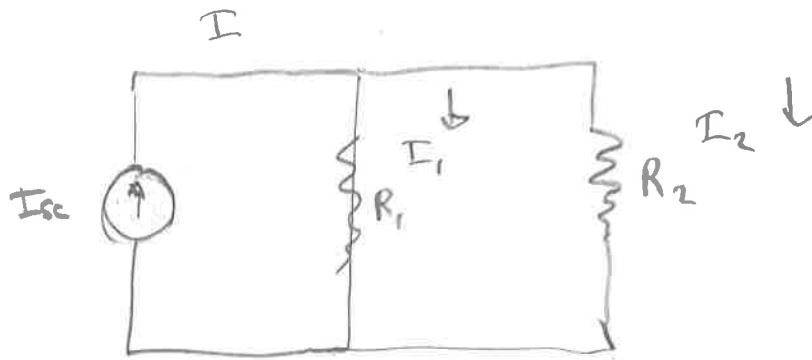


$$I = I_1 + I_2$$

$$V = I_1 R_1 = I_2 R_2$$

$$\frac{I_1 R_1}{I_2 R_2} = \frac{V}{V} = 1$$

$\Rightarrow$
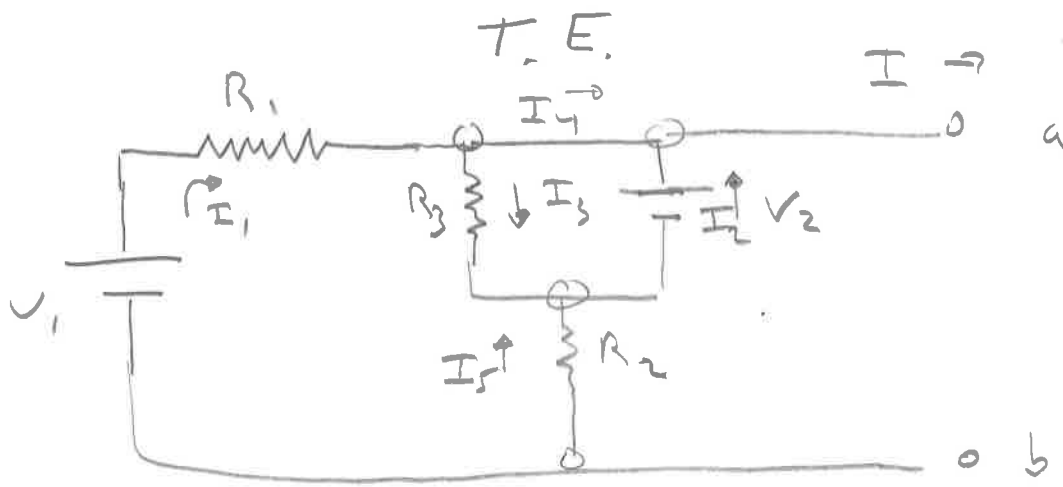
$$\boxed{\frac{I_1}{I_2} = \frac{R_2}{R_1}}$$



For open-circuit voltage, our earlier calculation of  $I_1$  still holds:

$$U_{Th} = U_1 - I_1 R_1$$

$$= U_1 - \frac{U_1 - U_2}{R_1 + R_2} R_1$$

$$U_{Th} = \frac{R_2 U_1 + R_1 U_2}{R_1 + R_2}$$

But for  $I_{sc}$ , currents change ( $I_1 \neq I_2 + I_3$ )

$$I_1 = I_3 + I_4 \quad I_4 + I_2 = I$$

$$I_2 = I_3 + I_5$$

$$I = I_1 + I_5$$

$$V_1 - I_1 R_1 - V_2 + I_5 R_2 = 0$$

$$V_2 - I_5 R_2 = 0$$

(other loop not needed!)

$$I_5 = V_2 / R_2$$

$$V_1 - I_1 R_1 - V_2 + \left( \frac{V_2}{R_2} \right) R_2$$

$$I_1 = V_1 / R_1$$

$$I = I_1 + I_5 = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$


$$I_{sc} = \frac{V_1 R_2 + V_2 R_1}{R_1 R_2}$$

$$R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{\frac{R_2 V_1 + R_1 V_2}{R_1 + R_2}}{\frac{R_2 V_1 + R_1 V_2}{R_1 R_2}}$$

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$$

Easier ways?

### Example

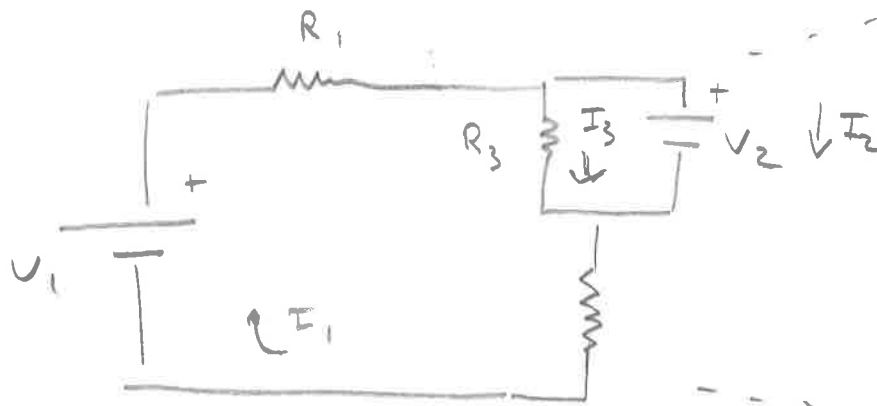

(currents drawn for  
my guess if  
 $U_1 \gg U_2$ )

$$I_1 = I_2 + I_3$$

$$U_2 + (-I_3 R_3) = 0$$

$$U_1 - I_1 R_1 - U_2 - I_1 R_2 = 0$$

$$I_1 = \frac{U_1 - U_2}{R_1 + R_2} \quad (\text{independent of } R_3)$$

$$I_3 = U_2 / R_3$$

$$I_2 = I_1 - I_3 = \frac{U_1 - U_2}{R_1 + R_2} - \frac{U_2}{R_3}$$

$$= \frac{R_3 U_1 - (R_1 + R_2 + R_3) U_2}{(R_1 + R_2) R_3}$$

$$R_3 = 0, \quad I_2 \rightarrow \infty \quad (\text{supplying a SC!}) \quad \checkmark$$

$$R_3 = \infty \quad I_2 \rightarrow \frac{U_1 - U_2}{R_1 + R_2} = I_1 \quad \checkmark$$



### Claim


Because of superposition principle,  
you can solve any circuit by  
setting  $V=0$  for all but one voltage  
source at a time, then add  
contributions, ....

### Corollary:


For T.E. resistance, you can  
short all voltage sources, and  
calculate effective resistance of  
network.

Lastly, you can replace a  
sub network (between two terminals)  
with its T.E. (provided you  
don't care about details of  
sub network)

Fast way

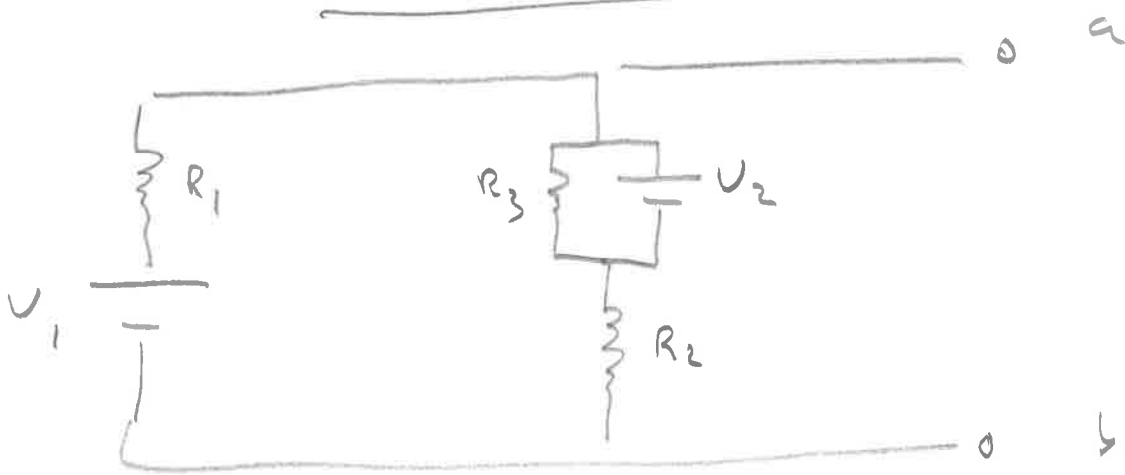

///

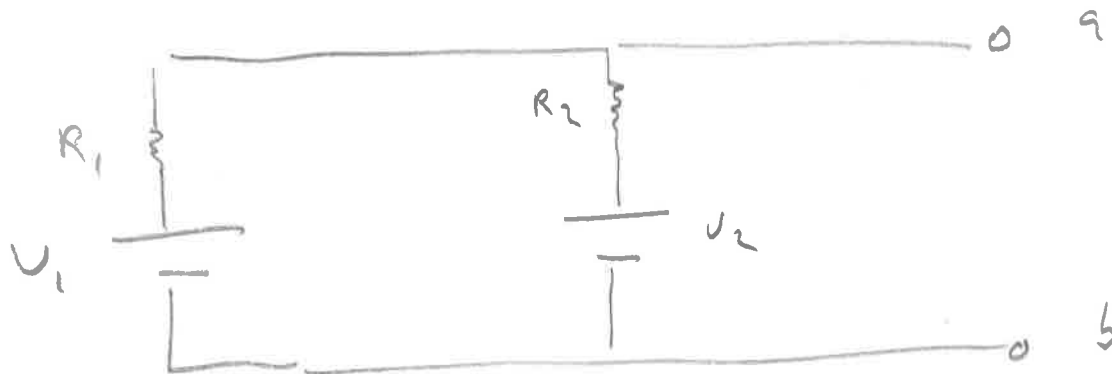



$$U_{TH} = U_{TH}(U_2=0) + U_{TH}(U_1=0)$$

$$U_{TH} = U_1 \cdot \frac{R_2}{R_1 + R_2} + U_2 \cdot \frac{R_1}{R_1 + R_2}$$

$$= \frac{U_1 R_2 + U_2 R_1}{R_1 + R_2}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

# Capacitor Model

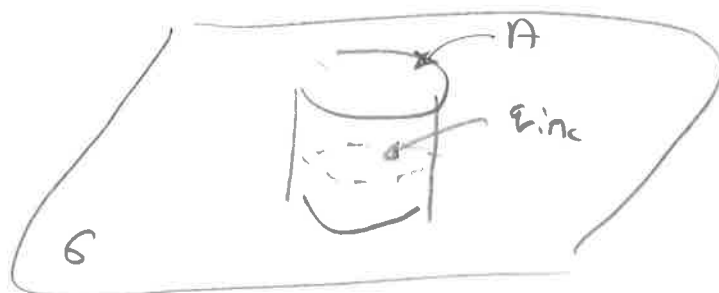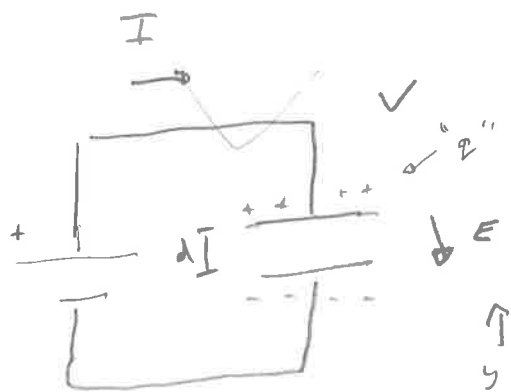

Don't know

$$E_y = - \frac{q_{inc}}{\epsilon_0 A}$$

$$V = - \int_0^d dy \left( - \frac{q_{inc}}{\epsilon_0 A} \right)$$

$$= \frac{d}{\epsilon_0 A} q$$

$$q = \frac{\epsilon_0 A}{d} V$$

$$q = CV$$

$$C = \frac{\epsilon_0 A}{d}$$

$$\vec{D} \cdot \vec{E} = \frac{1}{\epsilon_0} \rho$$

$$\int \vec{D} \cdot \vec{E} dV = \int \frac{1}{\epsilon_0} \rho dV$$

$$\int \vec{E} \cdot d\vec{A} = \frac{q_{inc}}{\epsilon_0}$$

$$EA = \frac{q_{inc}}{\epsilon_0}$$

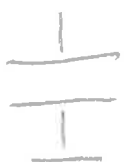

$$E = \frac{q_{inc}}{\epsilon_0 A}$$

Units:  $[F] = \frac{C}{V} = \frac{As}{V} = \frac{s}{\Omega}$

$(F \cdot \Omega = s) !!!$


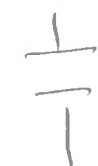
Exercise 1 From  $C = \epsilon_0 \frac{A}{d}$ , deduce

$C_{eq}$  for capacitors in parallel and in series:

$A_{eq} = A$  
  
 $d_{eq} = d_1 + d_2$  



$$\epsilon_0 C_{eq} = \epsilon_0 \frac{A_{eq}}{d_{eq}} = \frac{\epsilon_0 A}{d_1 + d_2}$$

$$\frac{1}{C_{eq}} = \frac{d_1}{\epsilon_0 A} + \frac{d_2}{\epsilon_0 A} = \frac{1}{C_1} + \frac{1}{C_2}$$

$A_{eq} = A_1 + A_2$  
  
 $d_{eq} = d$  

$$C_{eq} = \epsilon_0 \frac{A_{eq}}{d_{eq}} = \epsilon_0 \frac{A_1 + A_2}{d} = C_1 + C_2$$

## Exercise 2

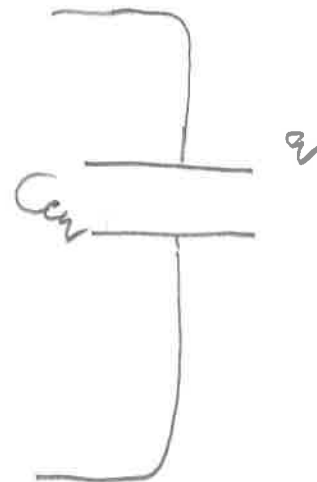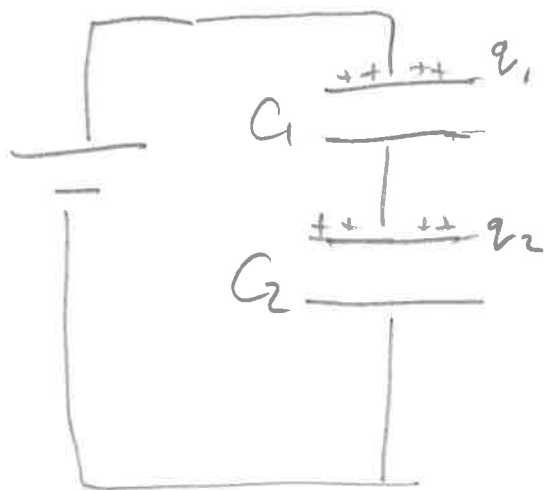

$$q = \int I dt$$

$$I = I_1 = I_2$$

$$\Rightarrow q = q_1 = q_2 \quad (*)$$


(\*) assumes initially uncharged! But in real system, leaks will tend to equalize the capacitance.)

$$V = \frac{q}{C_{eq}} = \frac{q_1}{C_1} + \frac{q_2}{C_2} = \frac{q}{C_1} + \frac{q}{C_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

### Exercise 3

HW

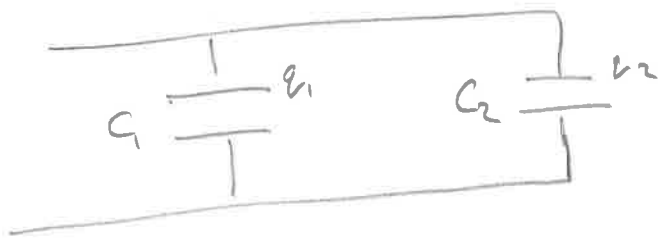

$$I = I_1 + I_2 \quad \Rightarrow \quad q = q_1 + q_2$$


$$V = \frac{q}{C}$$

$$\Rightarrow q = CV$$

$$C_{eq}V = C_1V + C_2V$$

$$C_{eq} = C_1 + C_2$$

## Current in Solenoid

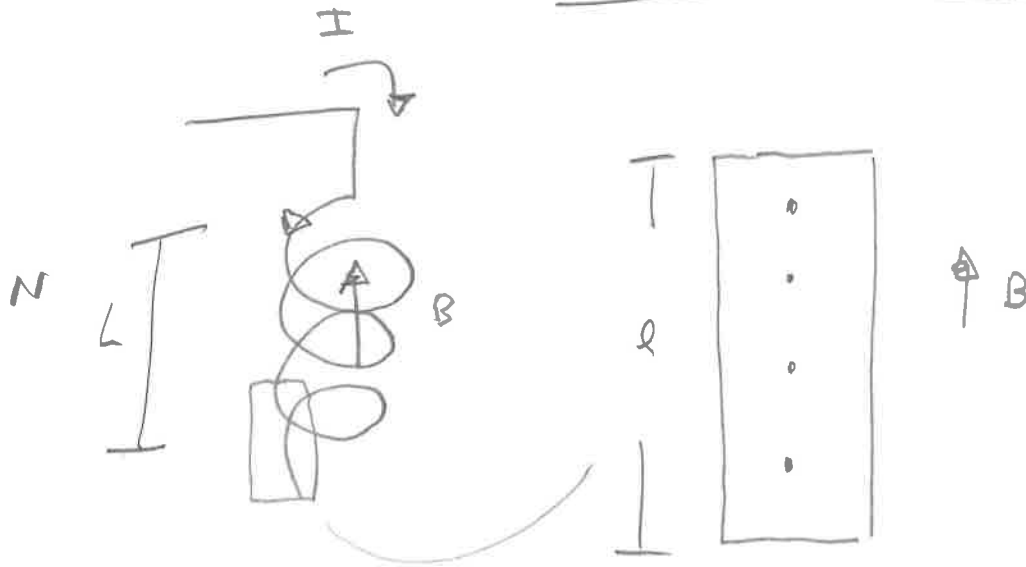



$$\vec{\nabla} \times \vec{B} = \mu_0 \vec{J}$$

$$\int \vec{\nabla} \times \vec{B} \cdot d\vec{A} = \mu_0 \int \vec{J} \cdot d\vec{A}$$

$$\int \vec{B} \cdot d\vec{l} = \mu_0 \int \vec{J} \cdot d\vec{A}$$

$$B l = \mu_0 \left( I l \cdot \frac{N}{L} \right)$$

$$B = \mu_0 I \frac{N}{L}$$

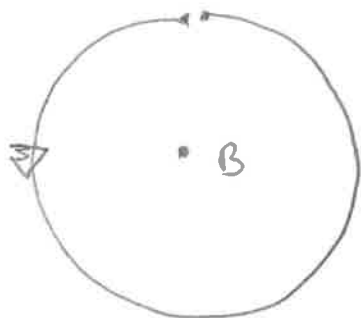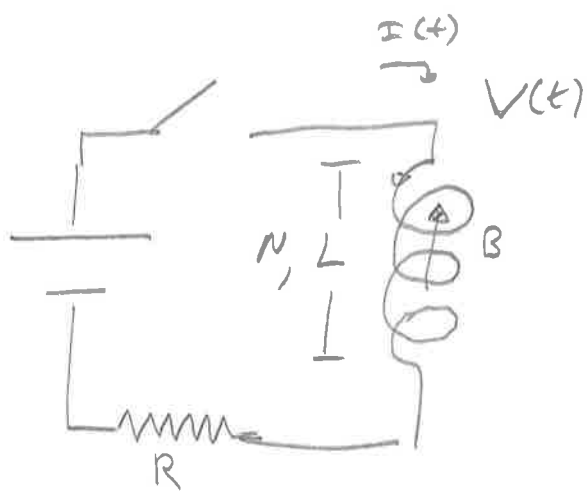

## Self Inductance

$$\vec{\nabla} \times \vec{E} = - \frac{\partial \vec{B}}{\partial t}$$

$$\int \vec{\nabla} \times \vec{E} \cdot d\vec{A} = - \int \frac{d\vec{B}}{dt} \cdot d\vec{A}$$

$$- \int \vec{E} \cdot d\vec{\lambda} = \int \frac{d\vec{B}}{dt} \cdot d\vec{A}$$

$$V_{loop} = - \frac{d}{dt} B A$$

$$= \frac{d}{dt} \left( \mu_0 \frac{N}{L} I \right) A$$

$$= \mu_0 \frac{A N^2}{L} \frac{dI}{dt}$$

$$V = N V_{loop} = \mu_0 \frac{A N^2}{L} \frac{dI}{dt}$$

$$V = L \frac{dI}{dt}$$

$$L = \mu_0 \frac{N^2 A}{L}$$

$$[L] = H = \frac{Vs}{A} = \Omega s$$

$$(H/\Omega = s)$$



### Exercise 1




$$I = I_1 + I_2 \quad \Rightarrow \quad \frac{dI}{dt} = \frac{dI_1}{dt} + \frac{dI_2}{dt}$$

$$\left( V = L \frac{dI}{dt} \right) \quad \Rightarrow \quad \frac{V}{L_{eq}} = \frac{V}{L_1} + \frac{V}{L_2}$$

$$\Rightarrow \quad \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

### Exercise 2

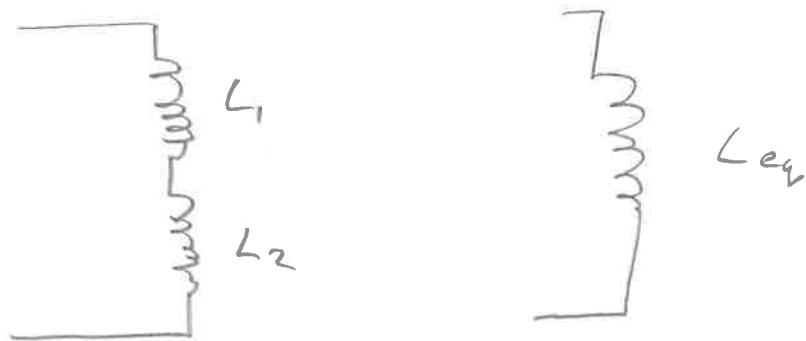

$$V = V_1 + V_2 \quad L_{eq} \frac{dI}{dt} = L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt}$$

$$\boxed{L_{eq} = L_1 + L_2}$$

Exercise: Fran

$$L \sim n^2 \frac{A}{d}$$

Can you guess equivalent inductance for  
series inductors,

ANS:  $L \sim n^2 \frac{A}{d} = \overset{\text{const}}{\left(\frac{2}{d}\right)} n A$

$n$  adds linearly,

Inductors are like resistors re equivalence.

\* Assuming no cross -inductance \*

R L C

Summary

$$R \sim \frac{d}{A}$$

$$C \sim \frac{A}{d}$$

$$L \sim \frac{A}{d} n^2$$

$$V = I R$$

$$V = \frac{q}{C}$$

$$V = L \frac{dI}{dt}$$

series = sum

series = ~~sum~~

series = sum

# Solutions to Linear Differential Equation

↙ solve

$$\underset{\substack{\uparrow \\ \text{given}}}{L} y(t) = \underset{\substack{\uparrow \\ \text{given}}}{f(t)}$$

Linear means:

$$L [\alpha x(t) + \beta y(t)] = \alpha L x(t) + \beta L y(t)$$

Homogeneous diff Eqs

$$L y(t) = 0$$

$$L x(t) = 0$$

$$\Rightarrow L (\alpha x(t) + \beta y(t)) = 0$$

\* "easy to solve for general case"

For Non-homogeneous, suffices to find  
one solution

$$L z(t) = f(t)$$

Then


$$L (z(t) + \alpha x(t) + \beta y(t)) = f(t)$$

\*\* Also can do  $L z_1(t) = f_1(t)$ ,  $L z_2(t) = f_2(t)$  \*\*

Maxwell Equations are linear (until  
material interactions are strong!)

\* We'll see later, even non-linear problems  
can be linearized near the operating point! \*

## RC circuit

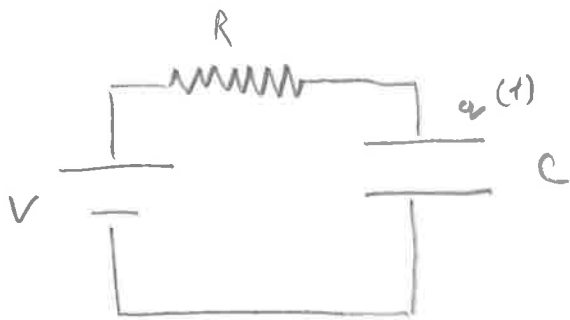

KVL:  $0 = V - IR - \frac{q}{C}$  or  $V = IR + \frac{q}{C}$

$$V = \frac{dq}{dt} R + \frac{q}{C}$$

$q = \text{const}$  is a special solution:  $V = \frac{q}{C} \Rightarrow q = CV$

Now solve  $\frac{dq}{dt} R + \frac{q}{C} = 0$

$q(t) = A \exp^{\beta t}$   $\frac{dq}{dt} = \beta A \exp^{\beta t} = \beta q$

$$\beta R q + \frac{q}{C} = 0 \Rightarrow \beta = -\frac{1}{RC}$$

General Solution:



$$q(t) = CV + A \exp\left(-\frac{t}{RC}\right)$$

IF  $q = 0$  at  $t = 0$


$$q(t) = CV \left(1 - \exp\left(-\frac{t}{RC}\right)\right)$$

$$I(t) = \frac{dq}{dt} = \frac{CV}{RC} \exp\left(-\frac{t}{RC}\right)$$

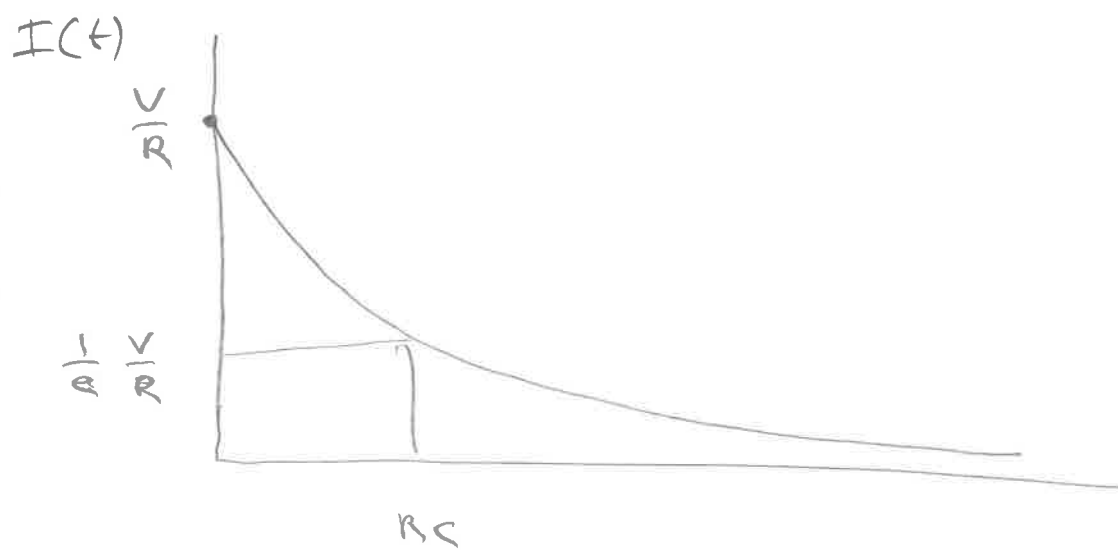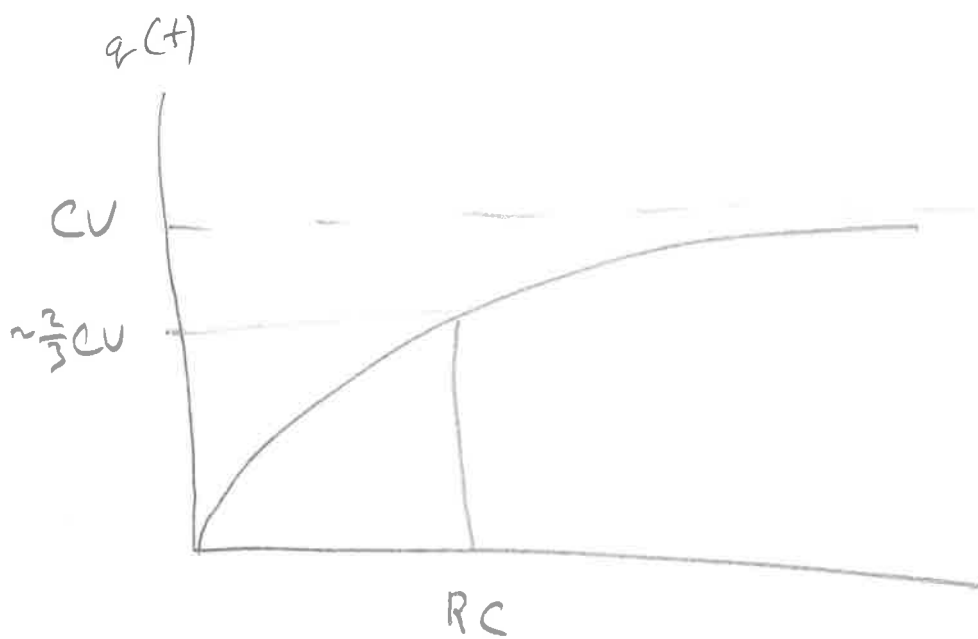
$$= \frac{V}{R} \exp\left(-\frac{t}{RC}\right)$$



## An L circuit

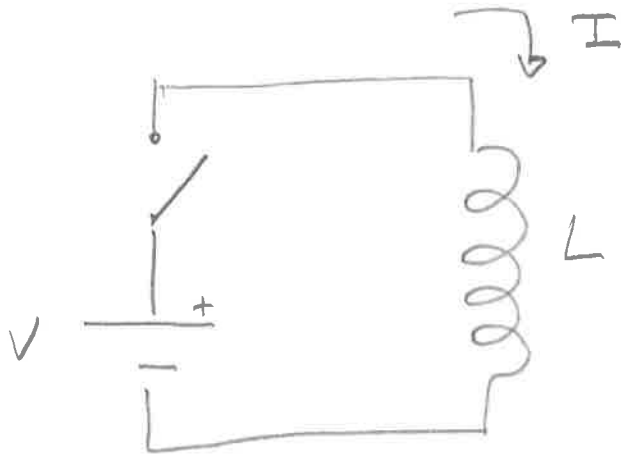

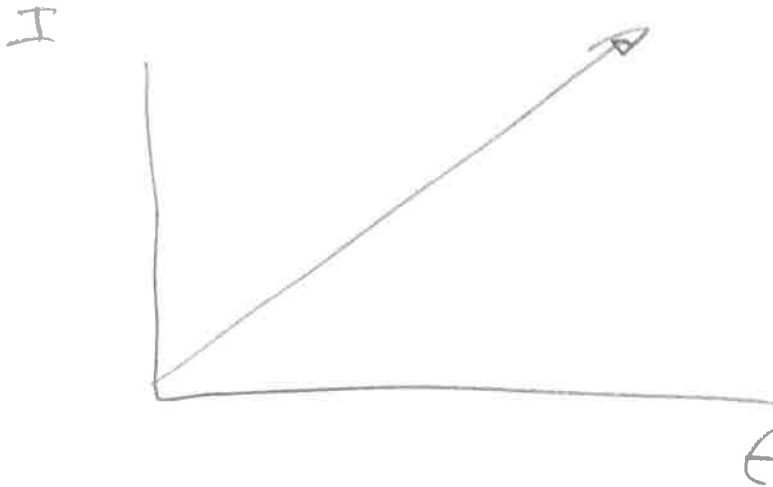
$$V = L \frac{dI}{dt} \Rightarrow I = \frac{V}{L} t + \text{const}$$



$$P = IV = \frac{V^2}{L} t \quad \text{is increasing ...}$$

... not very physical.

## An LR circuit

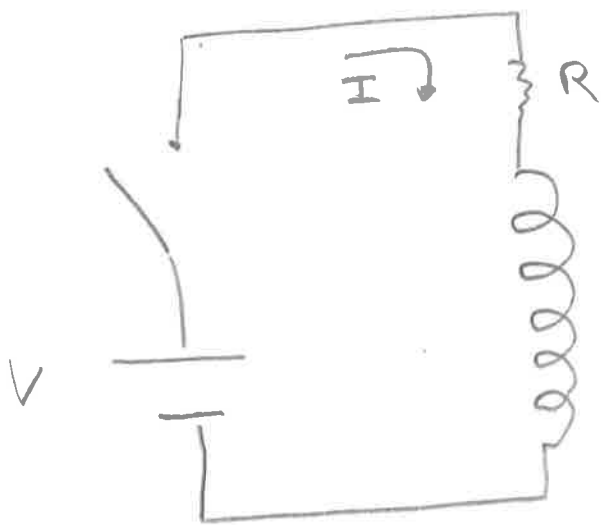

$$V = IR + L \frac{dI}{dt}$$

Special solution:  $I = \text{const} \Rightarrow I = \frac{V}{R}$

Now solve:  $0 = IR + L \frac{dI}{dt}$

$$I = A \exp Bt \quad \frac{dI}{dt} = BI$$

$$0 = IR + LBI \Rightarrow B = -\frac{R}{L}$$

General solution:  $I = \frac{V}{R} + A \exp\left(-\frac{t}{L/R}\right)$



$$I = 0 \text{ at } t=0 \text{ (continuity)}$$

$$\Rightarrow I(t) = \frac{V}{R} \left(1 - \exp\left(-\frac{t}{L/R}\right)\right)$$


$$V_L = L \frac{dI}{dt} = V \exp\left(-\frac{t}{L/R}\right)$$

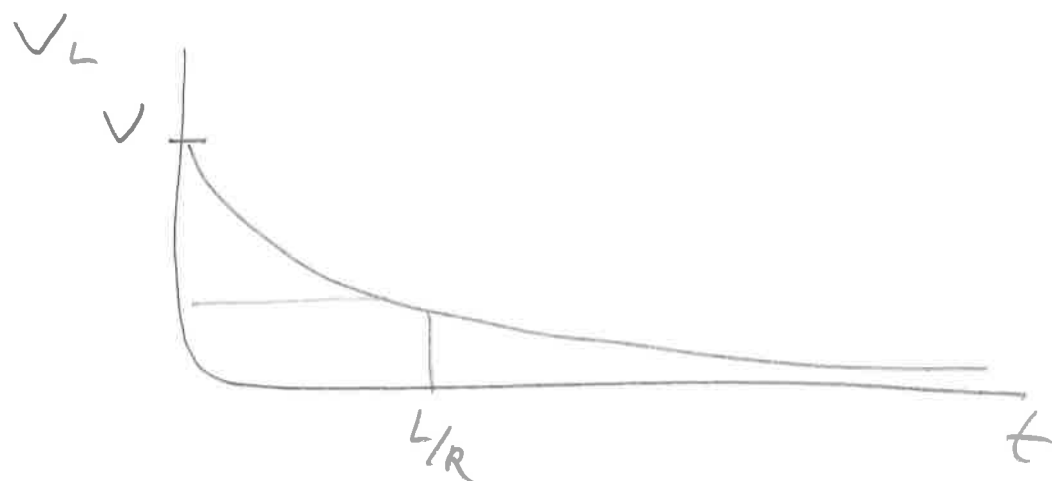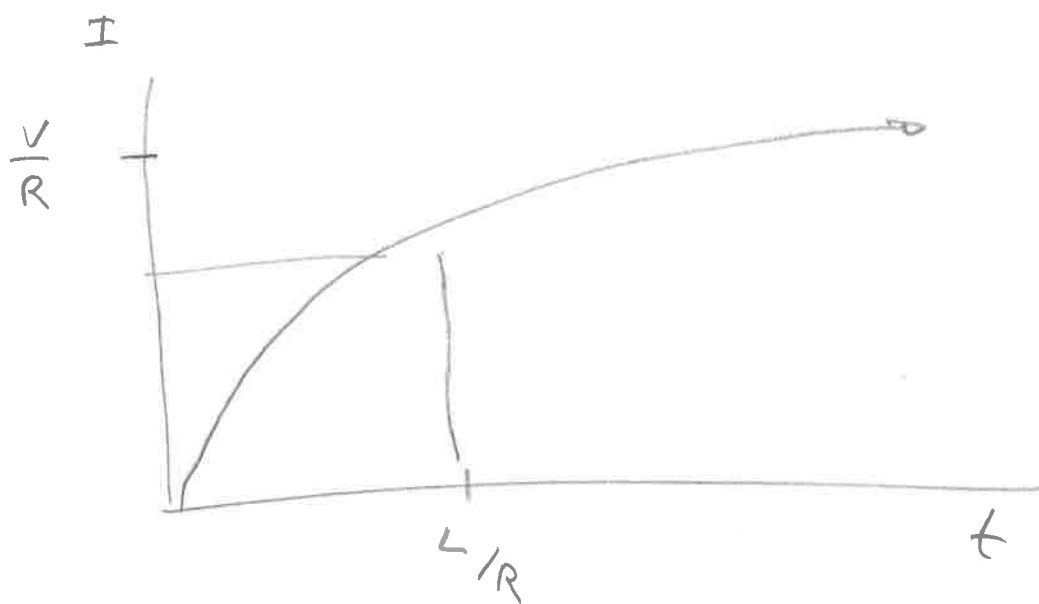Note: small  $t \ll L/R$ , recover  $I = \frac{V}{L} t$





# LC circuit

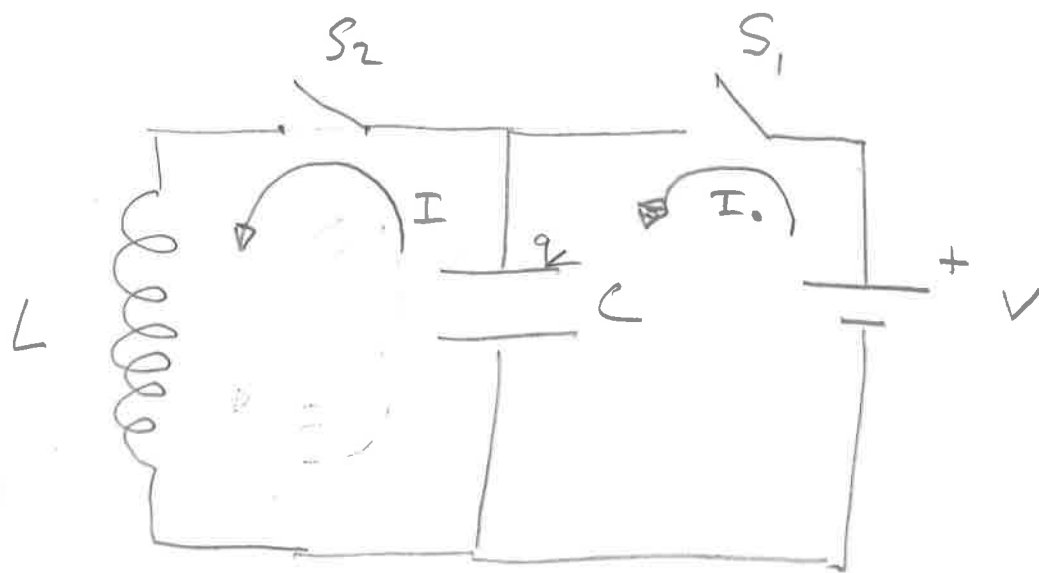

$S_1$  is initially closed for long time, with  $S_2$  open, so capacitor charges to  $q = CV$ , and  $V_{cap} = V$

$$\frac{q}{C} = L \frac{dI}{dt} \quad I = -\frac{dq}{dt}$$

$$q = -LC \frac{d^2 q}{dt^2}$$

$$q = A \cos \omega t + B \sin \omega t$$

$$\frac{d^2 q}{dt^2} = -\omega^2 q \Rightarrow \omega = \sqrt{LC} = \frac{2\pi}{T}$$

$$I = -\omega A \sin \omega t + \omega B \cos \omega t$$

$$I = 0 \text{ at } t = 0 \Rightarrow B = 0$$


$$q = A = CV$$

$$q(t) = CV \cos \omega t$$

$$V_{\text{cap}}(t) = \frac{q(t)}{C} = V \cos t / \sqrt{LC}$$



$$V_L(t) = L \frac{dI}{dt} = V \cos t / \sqrt{LC}$$

(as required by KVL)

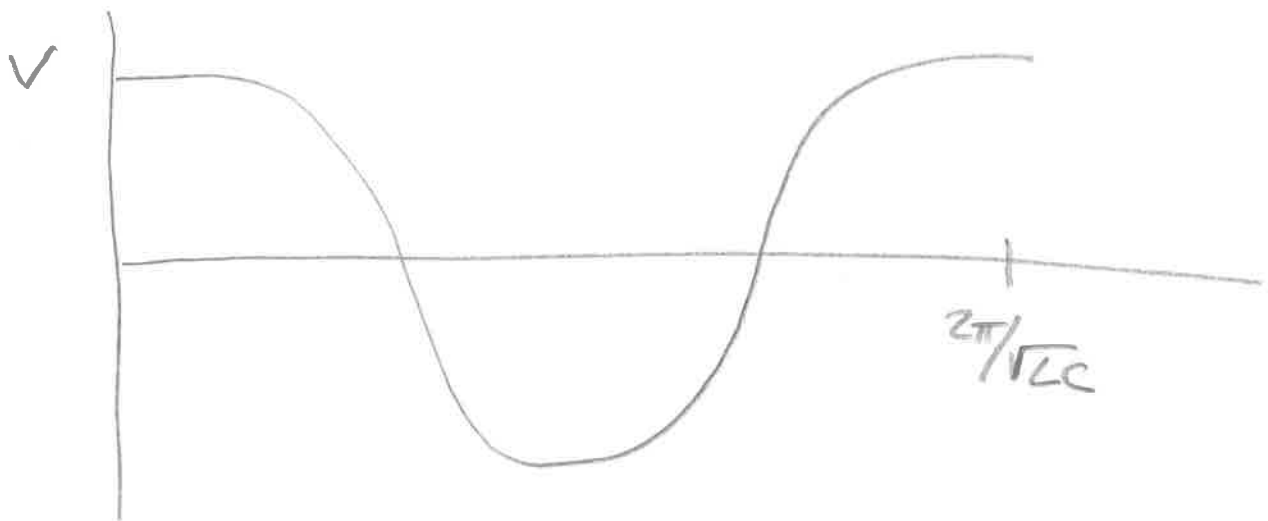

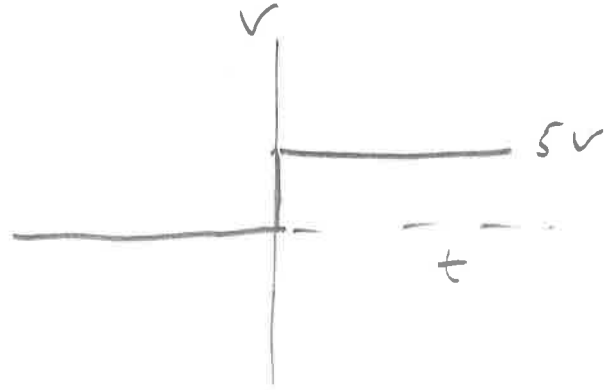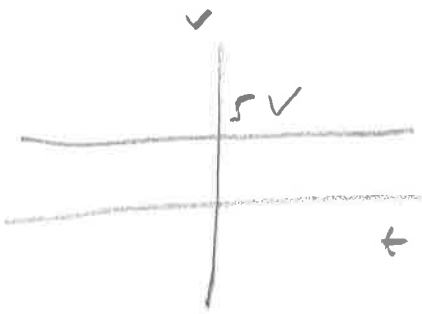
## Alternating Current

So far we've dealt w/ direct current, possibly switched on/off.




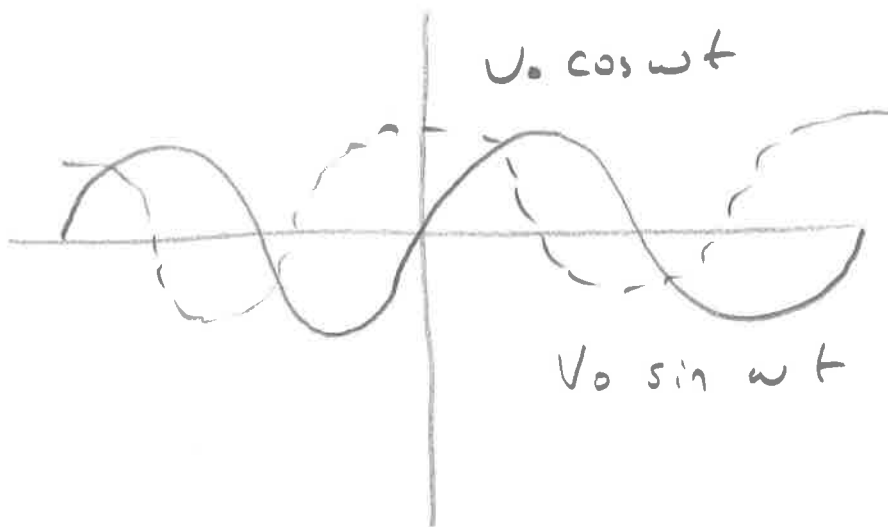Now we'll consider time varying voltages, particularly, sines and cosines:





Convention of text: AC signals lower case.


# AC circuits w/ R, C, L

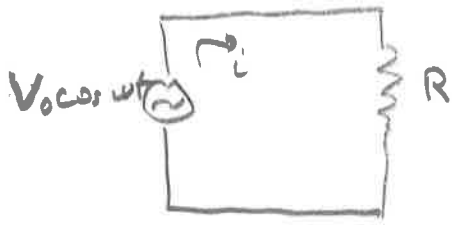
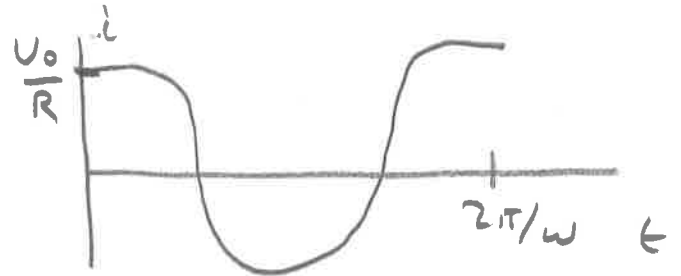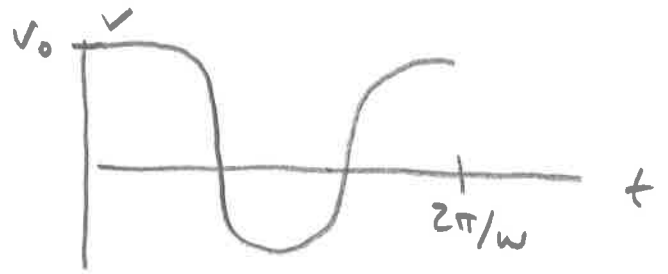
$$i = \frac{V}{R} = \frac{V_0}{R} \cos \omega t$$





$$I_{max} = V_0/R \quad \phi = 0$$

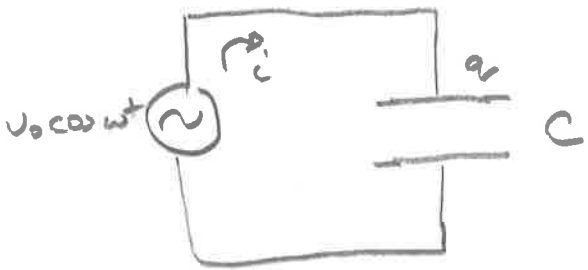

$$q(t) = C V(t) = C V_0 \cos \omega t$$

$$i = \frac{dq}{dt} = -\omega C V_0 \sin \omega t$$
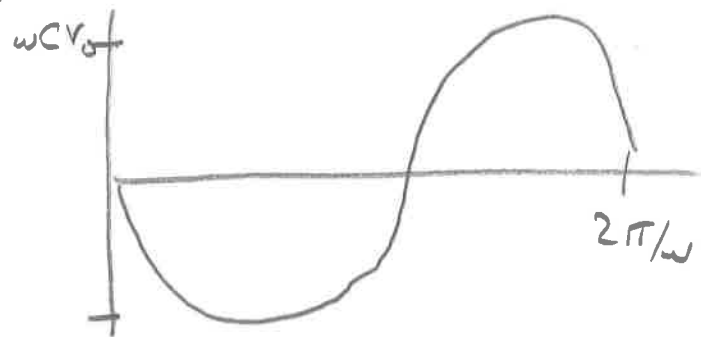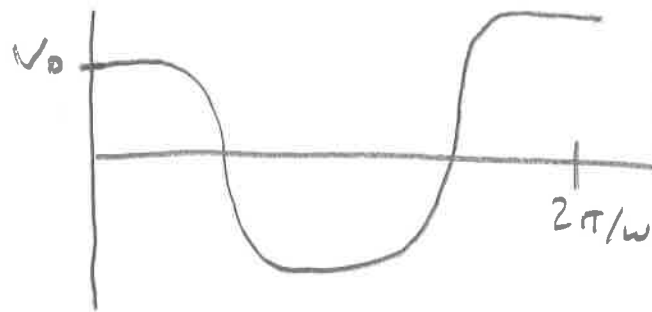
$$= \omega C V_0 \cos(\omega t + \frac{\pi}{2})$$




$$I_{max} = \omega C V_0$$

$$\phi = (-)^* \frac{\pi}{2}$$

(current lags voltage  $\frac{1}{4}$  period)

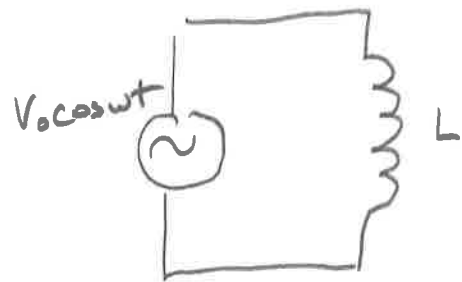\* ( $\phi$  of voltage relative to current)



$$v = V_0 \cos \omega t = L \frac{di}{dt}$$

$$\frac{d\epsilon}{dt} = \frac{V_0}{L} \cos \omega t$$

$$i = \frac{V_0}{L} \int \cos \omega t \, dt$$

$$i = \frac{V_0}{\omega L} \sin \omega t + \phi$$

~~$\phi$~~   
vanishes w/  
any  $R$ !



$$= \frac{V_0}{\omega L} \cos \left( \omega t - \frac{\pi}{2} \right)$$

$$I_{\max} = \frac{V_0}{\omega L}$$

$$\phi = (+)^* \frac{\pi}{2}$$

(current lags voltage  $\frac{1}{4}$  period)

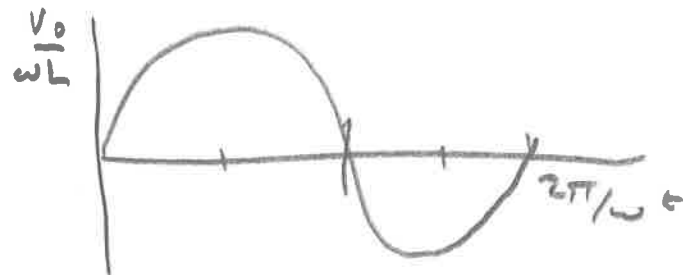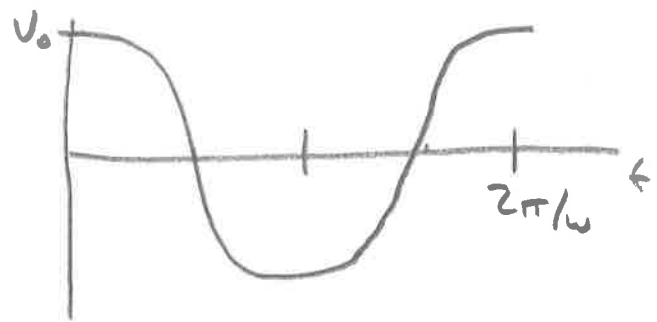\* ( $\phi$  of voltage relative to current)



To summarize:

<u>Component</u>	<u><math>I_{\max}</math></u>	<u><math>\phi</math></u>
R	$V_0 / R$	0
C	$\omega C V_0$	$-\frac{\pi}{2}$
L	$V_0 / \omega L$	$\frac{\pi}{2}$

R has resistance R

C has reactance  $\frac{1}{\omega C}$

L has reactance  $\omega L$

But what about phase?

→ Co-plex Plane!

## "Phase Vectors" or "Phasors"

An AC signal:

$$v(t) = V_0 \cos(\omega t + \phi)$$

can be rearranged as

$$\begin{aligned} v(t) &= \operatorname{Re} \left\{ V_0 e^{j(\omega t + \phi)} \right\} \\ &= \operatorname{Re} \left\{ \underbrace{[V_0 e^{j\phi}]}_{\substack{\text{magnitude and phase} \\ \text{of our specific} \\ \text{signal}}} e^{j\omega t} \right\} \end{aligned}$$

↑ generic AC  
with freq  $\omega$

$\tilde{V}$  is a complex number, representing

AC signal by

$$v(t) \equiv \operatorname{Re} \left\{ \tilde{V} e^{j\omega t} \right\}$$

We call  $\tilde{V}$  the "phase vector" or  
"phasor" for the AC signal  $v(t)$ .

Given:  $v(t) = V_0 \cos(\omega t + \phi)$

$$\tilde{V} \equiv V_0 e^{j\phi}$$



Example:

$$\underline{\tilde{V} = V_0}$$

$$\begin{aligned} v(t) &= \operatorname{Re} \{ \tilde{V} e^{i\omega t} \} \\ &= \operatorname{Re} \{ V_0 \cos \omega t + j V_0 \sin \omega t \} \\ &= V_0 \cos \omega t \end{aligned}$$

$$\underline{\tilde{V} = j V_0}$$

$$\begin{aligned} v(t) &= \operatorname{Re} \{ (j V_0) e^{i\omega t} \} \\ &= \operatorname{Re} \{ j V_0 \cos \omega t + j V_0 j \sin \omega t \} \\ &= -V_0 \sin \omega t \end{aligned}$$

$$\underline{\tilde{V} = V_0 e^{j\phi}}$$


$$\begin{aligned} v(t) &= \operatorname{Re} \{ V_0 e^{j\phi} \cdot e^{j\omega t} \} \\ &= \operatorname{Re} \{ V_0 e^{j(\omega t + \phi)} \} \\ &= \operatorname{Re} \{ V_0 \cos(\omega t + \phi) + j V_0 \sin(\omega t + \phi) \} \\ &= V_0 \cos(\omega t + \phi) \end{aligned}$$

\* Nothing magical here, just a nice compact notation... so far! \*

\* Important Example \*

$$\tilde{V} = a + bj$$
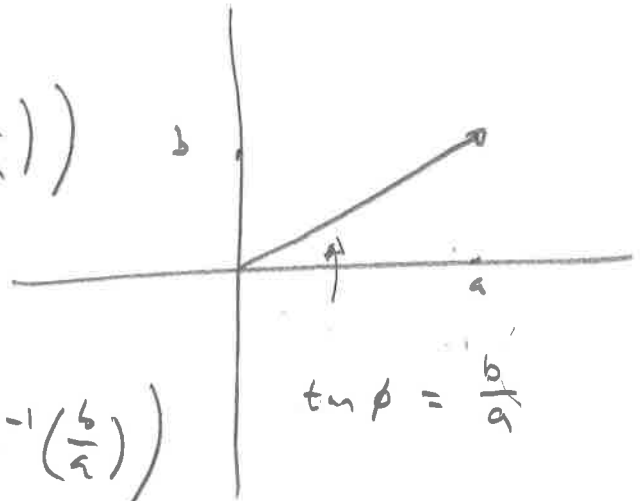
$$= \sqrt{a^2 + b^2} \exp\left(j \tan^{-1}\left(\frac{b}{a}\right)\right)$$



$$v(t) = \sqrt{a^2 + b^2} \cos\left(\omega t + \underbrace{\tan^{-1}\left(\frac{b}{a}\right)}_{\phi}\right)$$

$$\tan \phi = \frac{b}{a}$$

So why is 4.3 useful?


$$x(t) = \operatorname{Re} \{ \tilde{X} e^{j\omega t} \}$$

$$\begin{aligned} \frac{dx}{dt} &= \operatorname{Re} \left\{ \tilde{X} \frac{d}{dt} e^{j\omega t} \right\} \\ &= \operatorname{Re} \{ (j\omega \tilde{X}) e^{j\omega t} \} \end{aligned}$$

$$\begin{aligned} \int x \, dt &= \operatorname{Re} \left\{ \tilde{X} \int dt \, e^{j\omega t} \right\} \\ &= \operatorname{Re} \left\{ \frac{\tilde{X}}{j\omega} e^{j\omega t} + \cancel{\text{term}} \right\} \\ &\quad \text{(typically vanishes)} \end{aligned}$$

To take  $\frac{d}{dt}$ , multiply phasor by  $j\omega$

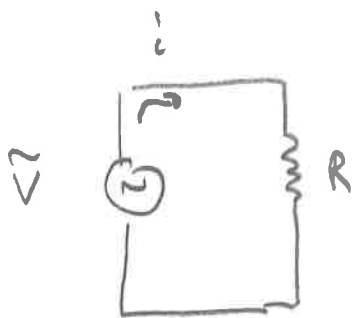To integrate, multiply phasor by  $\frac{1}{j\omega}$




$$v(t) = \text{Re} \{ \tilde{V} e^{j\omega t} \}$$

$$i(t) = \frac{v(t)}{R} = \text{Re} \left\{ \frac{\tilde{V}}{R} e^{j\omega t} \right\}$$

$$\tilde{I} = \frac{\tilde{V}}{R}$$

$$\boxed{\tilde{V} = R \tilde{I}}$$

Recover Ohm's Law

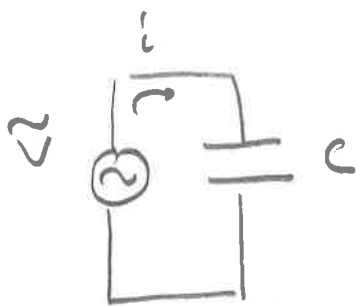

$$v(t) = \text{Re} \{ \tilde{V} e^{j\omega t} \}$$

$$q(t) = C v(t) = \text{Re} \{ C \tilde{V} e^{j\omega t} \}$$


$$i(t) = \frac{dq}{dt} = \text{Re} \{ j\omega C \tilde{V} e^{j\omega t} \}$$

$$\tilde{I} = (j\omega C) \tilde{V}$$

$$\tilde{V} = \left( \frac{1}{j\omega C} \right) \tilde{I}$$

Ohm's Law for  
a Capacitor !!!

## Phasor in L circuit

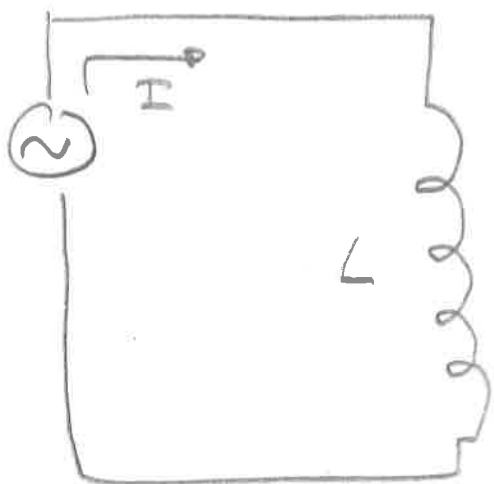

$$V(t) = \text{Re} \{ V_0 e^{j\phi} e^{j\omega t} \}$$

$$V = L \frac{dI}{dt}$$

$$\Rightarrow \frac{dI}{dt} = \frac{V}{L}$$

$$I = \frac{1}{L} \int V dt$$


$$= \text{Re} \left\{ \frac{V_0}{L} e^{j\phi} \int dt e^{j\omega t} \right\}$$

$$= \text{Re} \left\{ \frac{V_0 e^{j\phi}}{j\omega L} e^{j\omega t} \right\}$$

$$\tilde{I} = \frac{\tilde{V}}{j\omega L}$$

$$\tilde{V} = (j\omega L) \tilde{I}$$

## Phasor's in L circuit

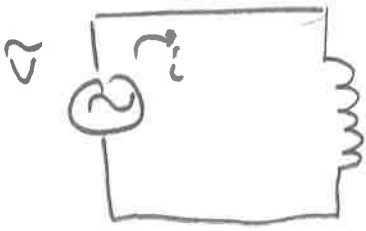

$$v(t) = \text{Re} \left\{ \tilde{V} e^{j\omega t} \right\}$$

$$v = L \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{v}{L} = \text{Re} \left\{ \frac{\tilde{V}}{L} e^{j\omega t} \right\}$$

$$i = \text{Re} \left\{ \frac{\tilde{V}}{L} \int e^{j\omega t} dt \right\}$$

$$= \text{Re} \left\{ \frac{\tilde{V}}{j\omega L} e^{j\omega t} + \cancel{\phi} \right\}$$


$$\tilde{I} = \frac{\tilde{V}}{j\omega L}$$

$$\boxed{\tilde{V} = (j\omega L) \tilde{I}}$$

Ohm's Law for  
Inductor.

# Summary

	$Z$	$\phi (V \text{ wrt } \pm)$
R	R	0
C	$\frac{1}{j\omega C}$	$-\frac{\pi}{2}$
L	$j\omega L$	$\frac{\pi}{2}$

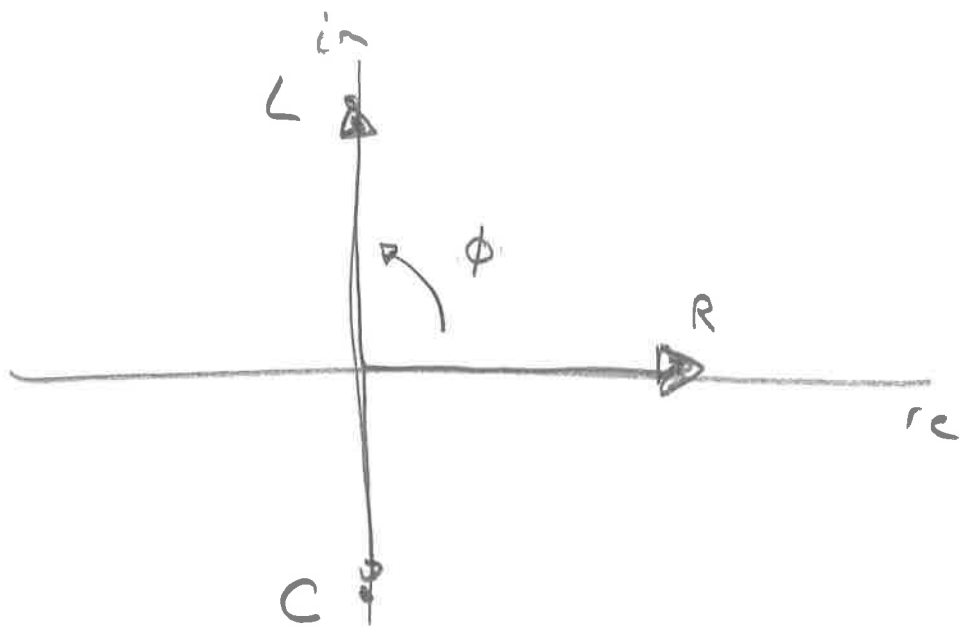

$$\tilde{V} = Z \tilde{I}$$

To Recap:

$$\tilde{V} = R \tilde{I}$$

$$\tilde{V} = \frac{1}{j\omega C} \tilde{I}$$

$$\tilde{V} = j\omega L \tilde{I}$$

We replace diff eqs with complex algebra!

New Ohm's Law:

$$\begin{array}{ccccccc} \tilde{Z} & = & A & + & B & j \\ \uparrow & & \uparrow & & \uparrow & & \\ \text{Impedance} & & \text{Resistance} & & \text{Reactance} & & \end{array}$$

$$\boxed{\tilde{V} = \tilde{Z} \tilde{I}}$$

Because Impedance follows Ohm's law,  
calculate equivalent impedance exactly  
as for resistance



## Decibels (dB)

Used often by Engineers, decibel initially related power to a reference power by a logarithmic scale:

$$P [\text{dB}] = 10 \log_{10} (P/P_0)$$

For electrical systems, we have

$$P = \frac{V^2}{R}$$

So

$$\begin{aligned} P [\text{dBV}] &= 10 \log_{10} (P/P_0) \\ &= 10 \log_{10} \left( \frac{V^2/R}{V_0^2/R} \right) \\ &= 20 \log_{10} (V/V_0) \end{aligned}$$

Confusion:

What is  $P_0$  or  $V_0$  ...

Factors of 20 / 10 ...

## Bode Plot Cheat Sheet

$$20 \log_{10} \sqrt{2} = 3$$

$$20 \log_{10} 10 = 20$$

$$20 \log_{10} 100 = 40$$

$$\tan^{-1}(1) = \frac{\pi}{4} = 45^\circ$$

$$\tan^{-1}(0.1) = 6^\circ$$

$$\tan^{-1}(10,0) = 90^\circ - 6^\circ$$

Particularly interesting point (we'll see)  
is when


$$P = \frac{1}{2} P_0 \quad \text{or} \quad V = \frac{1}{\sqrt{2}} V_0$$

i.e.

$$\begin{aligned} P[\text{dB}] &= 10 \log_{10} \left( \frac{1}{2} \right) \\ &= -10 \log_{10} 2 = -3.01 \\ &= 20 \log_{10} \left( \frac{1}{\sqrt{2}} \right) \\ &= -10 \log_{10} (2) = -3.01 \end{aligned}$$

The "-3 dB" is where power drops  
by  $1/2$ , voltage by  $1/\sqrt{2}$ .

# Low pass Filter

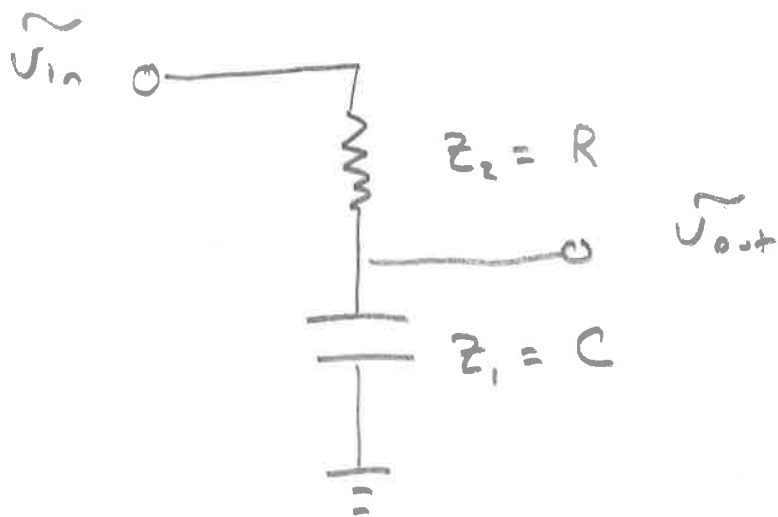

$$H \equiv \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = \frac{Z_1}{Z_1 + Z_2} = \frac{1/j\omega C}{R + 1/j\omega C}$$

$$= \frac{1}{1 + j\omega RC} = \frac{1}{1 + j(\omega/\omega_0)}$$

$$\omega_0 \equiv 1/RC$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi RC}$$

$$H = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = \frac{1 - j(\omega/\omega_0)}{1 + (\omega/\omega_0)^2}$$

At  $\omega = \omega_0$ :


$$|H| = \frac{1}{\sqrt{2}}$$

Gain:

$$G = \frac{|\tilde{V}_{out}|}{|\tilde{V}_{in}|} = \frac{V_{out}}{V_{in}} = |H| = \left[ \frac{1}{\sqrt{2}} \right]$$

$$20 \log_{10} G = -3.01$$

$\omega_0$  is the -3dB point...

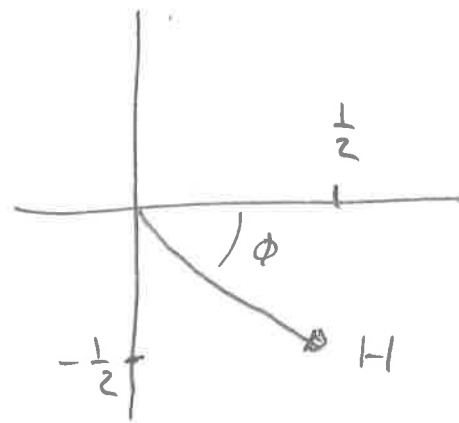

$$\phi = -45^\circ$$

from plot or

$$\phi = \tan^{-1}\left(\frac{-1}{1}\right)$$


# Low pass Filter

$$G = |H| = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}$$

On dB scale:


$$\begin{aligned} G[\text{dB}] &= 20 \log_{10} G \\ &= -10 \log_{10} [1 + (\omega/\omega_0)^2] \end{aligned}$$

$\omega/\omega_0$	$G[\text{dB}]$
1	-3
10	-20
100	-40
∞	∞

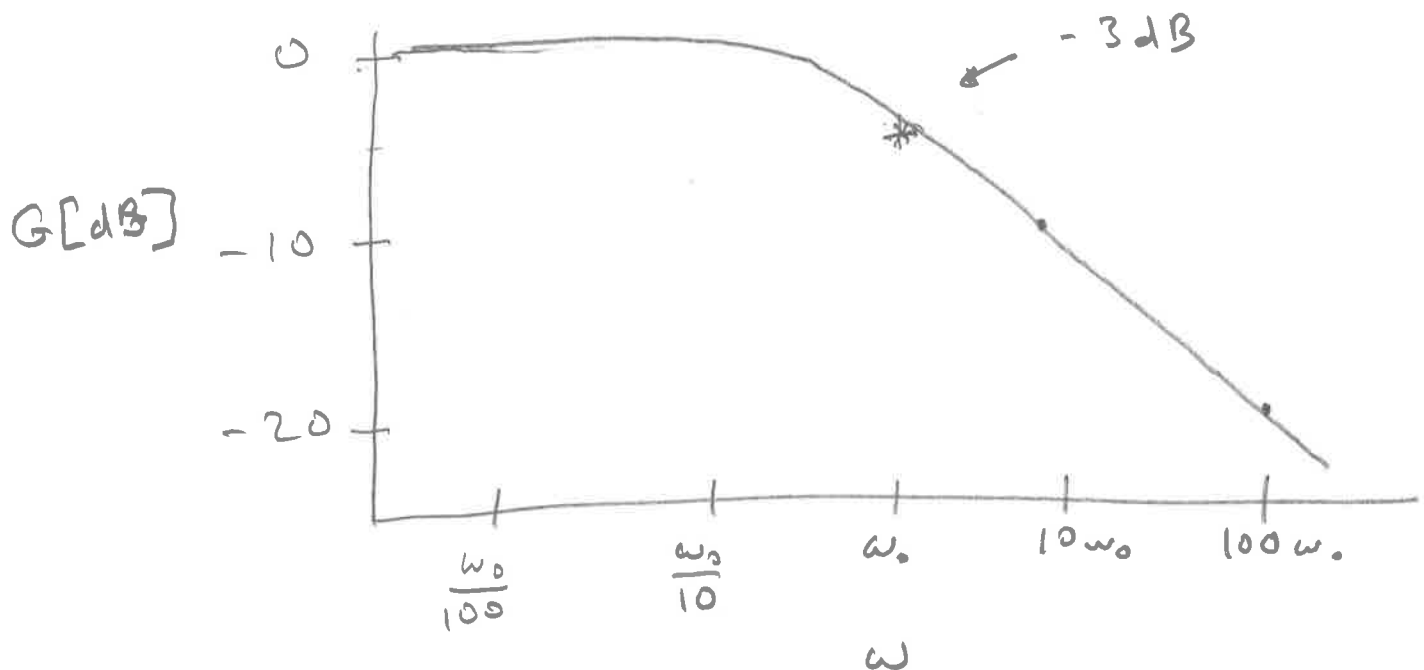
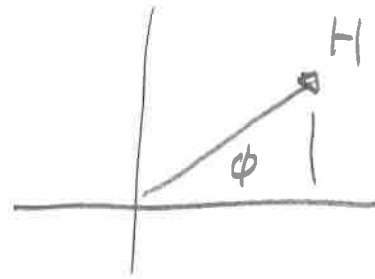
# Phase of Low-pass Filter

$$\phi(H) = \tan^{-1} \left( \frac{\text{Im}(H)}{\text{Re}(H)} \right)$$



$$H = \frac{1 - j(\omega/\omega_0)}{1 + (\omega/\omega_0)^2}$$

$$\tan \phi = \frac{-(\omega/\omega_0)}{1}$$

$$\phi = -\tan^{-1}(\omega/\omega_0)$$

$$\frac{\omega/\omega_0}{1}$$

0.1

10.0

0°

-45°

-6°

-(90° - 6°)


-45°

-90°

$\frac{\omega_0}{10}$

$\omega_0$


$10\omega_0$

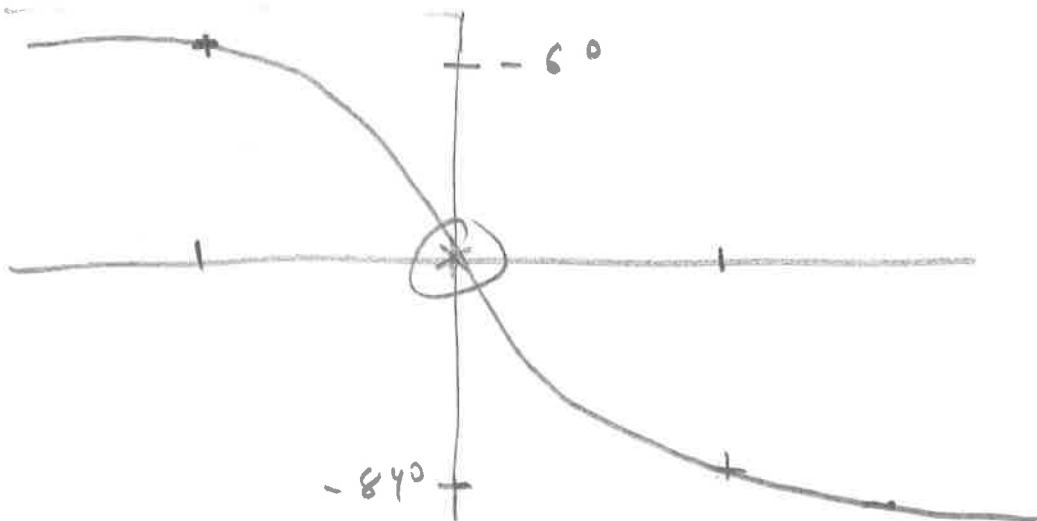

In general:

$$\frac{\tilde{V}_{out}}{\tilde{V}_{in}} = \frac{1 - j(\omega/\omega_0)}{1 + (\omega/\omega_0)^2}$$
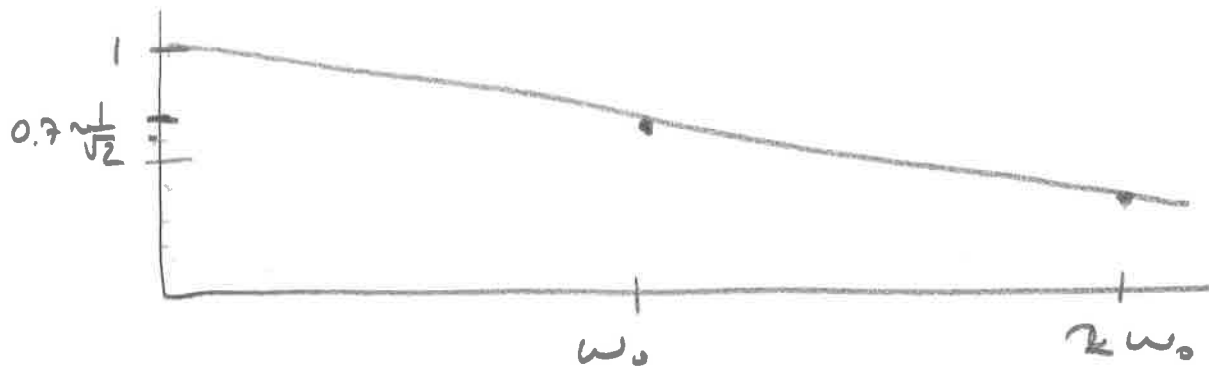
$$\frac{V_{out}}{V_{in}} = \frac{\sqrt{1 + (\omega/\omega_0)^2}}{1 + (\omega/\omega_0)^2} = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}$$




On log scale (in dB)


$$\begin{aligned} \frac{V_{out}}{V_{in}} [\text{dB}] &= 20 \log_{10} \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}} \\ &= -10 \log_{10} 1 + (\omega/\omega_0)^2 \end{aligned}$$

$$\omega = \omega_0 \Rightarrow -3 \text{ dB}$$

$$\omega = \omega_0 \times 10 \Rightarrow -20 \text{ dB}$$
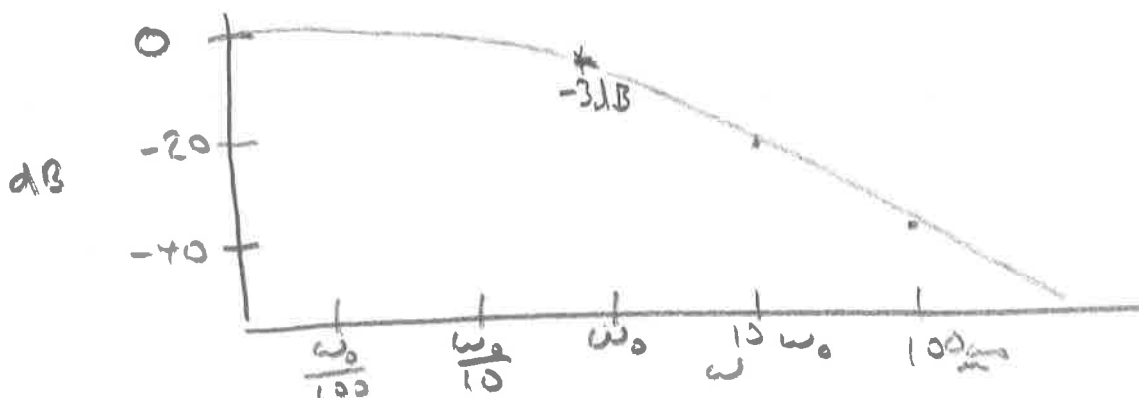
$$\omega = \omega_0 \times 100 \Rightarrow -40 \text{ dB}$$



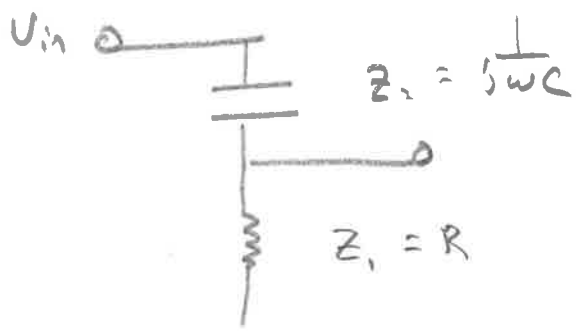


High pass Filter

$$H = \frac{Z_1}{Z_1 + Z_2} = \frac{R}{R + \frac{1}{j\omega C}}$$

$$= \frac{1}{1 - j \frac{1}{\omega RC}}$$

$$\frac{1}{1 - j \left( \frac{\omega_0}{\omega} \right)}$$


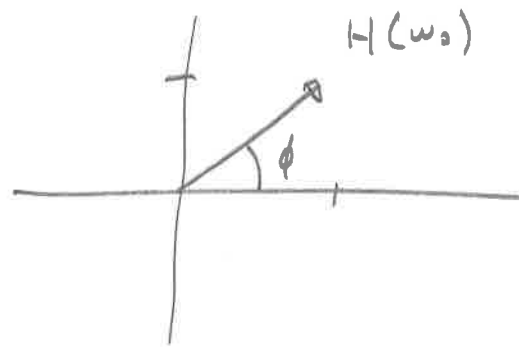
$$= \frac{1 + j \left( \frac{\omega_0}{\omega} \right)}{1 + \left( \frac{\omega_0}{\omega} \right)^2}$$



At  $\omega_0$

$$G = |H| = \frac{1}{\sqrt{2}}$$

$$\phi = +\frac{\pi}{4} = 45^\circ$$

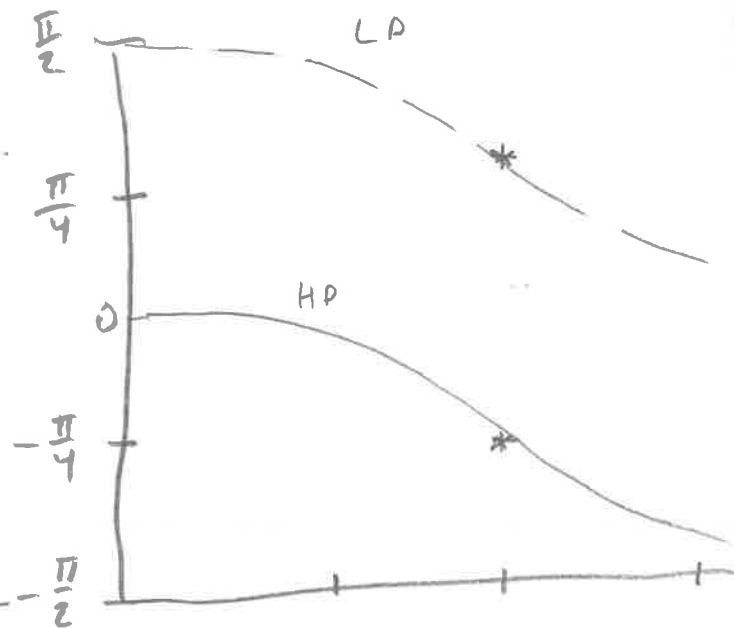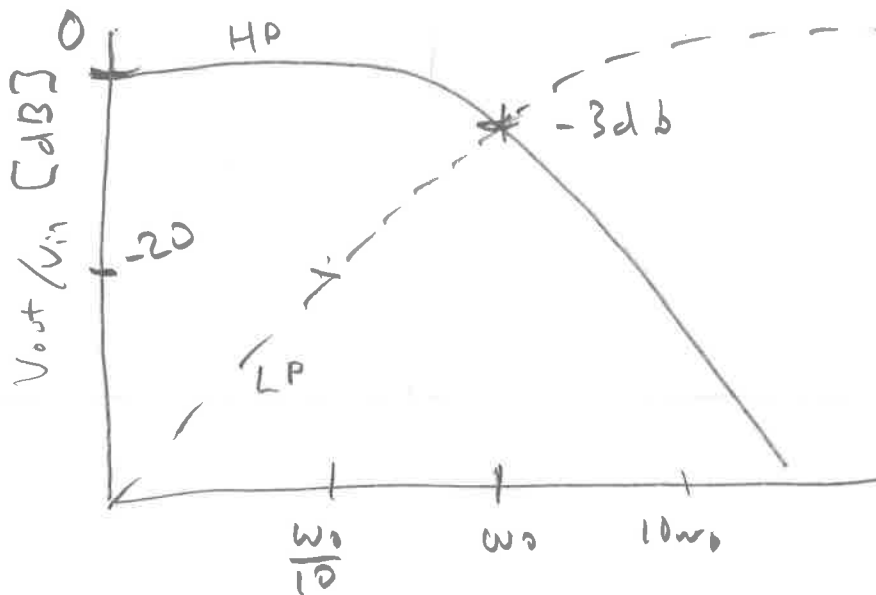




Not Included Yet. . .

→ Power in RLC systems?

→ Transformers ?

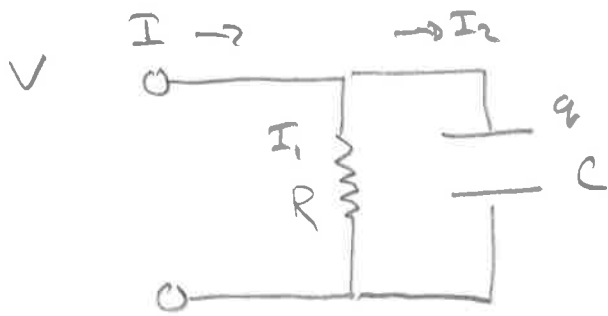DC  $I$ - $V$  curve for  $R+C$ : (steady state)



$$\frac{dq}{dt} = 0$$


$$\Rightarrow I_2 = 0$$

$$q = CV$$

$$I_2 = 0 \Rightarrow I = I_1$$

$$V = I_1 R = IR$$


Looks just like

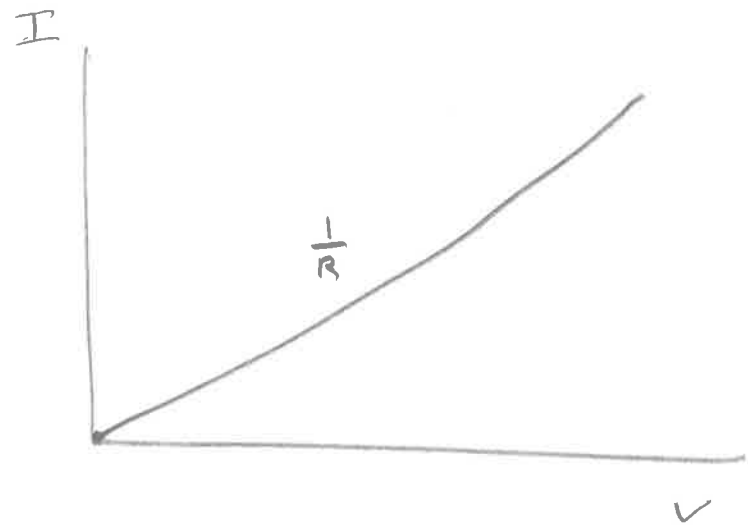

**\*\* DC steady-state only \*\***

Much more interesting behavior  
from AC sources and transients

(Leave For After Lab 1)

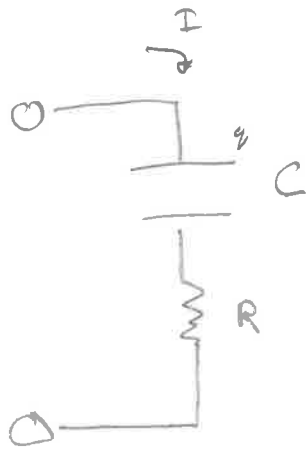

$$\frac{dq}{dt} = 0$$

$$I = 0$$


Looks like

$$R = \infty$$



\* For DC steady state, simply  
replace capacitors with  
an open circuit ( $R = \infty$ )

# RLC Band pass Filter

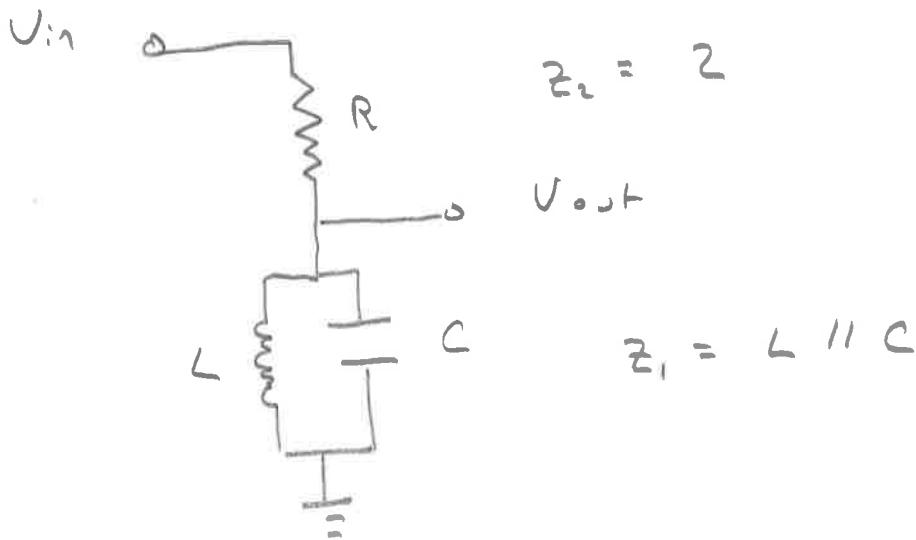

$$H = \frac{Z_1}{Z_1 + Z_2} = \frac{1}{1 + Z_2/Z_1}$$

$$\frac{1}{Z_1} = \frac{1}{Z_C} + \frac{1}{Z_L} = j\omega C + \frac{1}{j\omega L}$$

$$\begin{aligned} \frac{Z_2}{Z_1} &= j \frac{RC}{\omega} \left( \omega^2 - \frac{1}{LC} \right) \quad \gamma = RC \quad \omega_0 = \frac{1}{\sqrt{LC}} \\ &= j \frac{\gamma}{\omega} \left( \omega^2 - \omega_0^2 \right) = j (\gamma \omega_0) \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \end{aligned}$$

$$H(\omega = \omega_0) = \frac{1}{1+0} = 1 \quad \text{In phase, unit gain.}$$

$$H = \frac{1}{1 + j(\gamma \omega_0) \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)}$$

$$|H|^2 = \frac{1}{1 + (\gamma\omega_0)^2 \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}$$

At  $\omega_+$  and  $\omega_-$

$$|H|^2 = \frac{1}{2}$$

$$\Rightarrow (\gamma\omega_0)^2 \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2 = 1$$

$$\left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2 = \frac{1}{(\gamma\omega_0)^2}$$

$$\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} = \pm \frac{1}{\gamma\omega_0}$$


$$\left( \frac{\omega}{\omega_0} \right)^2 \pm \frac{1}{\gamma\omega_0} \left( \frac{\omega}{\omega_0} \right) = 1$$

$$\left( \frac{\omega}{\omega_0} \pm \frac{1}{2\gamma\omega_0} \right)^2 = 1 + \frac{1}{4(\gamma\omega_0)^2} = 1 + \varepsilon$$

$$\frac{\omega}{\omega_0} = \sqrt{1 + \varepsilon} \pm \frac{1}{2\gamma}$$


$$\omega_+ - \omega_- = \frac{1}{\gamma}$$
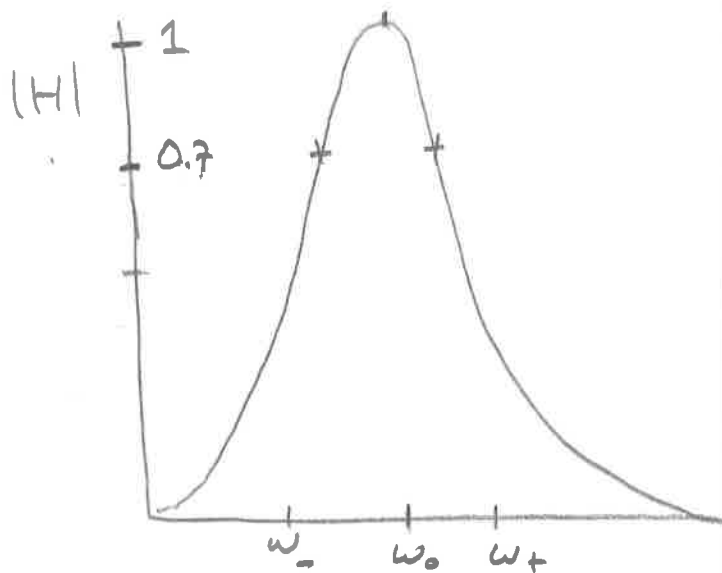
$$Q = \frac{\omega_0}{\omega_+ - \omega_-} = \boxed{\omega_0 \gamma}$$



$$Q = \frac{\omega_0}{\omega_+ - \omega_-}$$
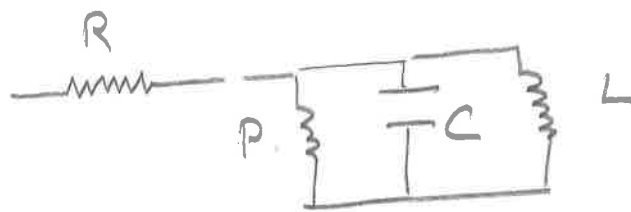
# Effect of Parasitic Parallel Resistance (Not for lecture)



$$G = \frac{1}{1 + Z_2/Z_1}$$

$$\frac{1}{Z_1} = \frac{1}{P} + j\omega C + \frac{1}{j\omega L}$$

$$\frac{Z_2}{Z_1} = \frac{R}{P} + j\omega RC \left(1 - \frac{1}{\omega^2 LC}\right)$$

$$= \frac{R}{P} + j\omega \cdot \tau \left(1 - \frac{\omega_0^2}{\omega^2}\right) \quad \tau = RC$$

$$\omega_0^2 = \frac{1}{LC}$$

$$= \frac{R}{P} + j\omega_0 \tau \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)$$

$$G = \frac{1}{1 + \frac{R}{P} + j(\omega_0 \tau) \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)}$$

$$|G|^2 = \frac{1}{\left(1 + \frac{R}{P}\right)^2 + (\omega_0 \tau)^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^2}$$


$$|G_{\max}|^2 = \frac{1}{1 + (R/P)^2}$$

$$Q = \frac{\omega_0 \tau}{1 + R/P}$$

$$\frac{|G|^2}{|G_{\max}|^2} = \frac{1}{1 + \left(\frac{\omega_0 \tau}{1 + R/P}\right)^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^2}$$

# Parallels with QFT

Feynman Diagrams

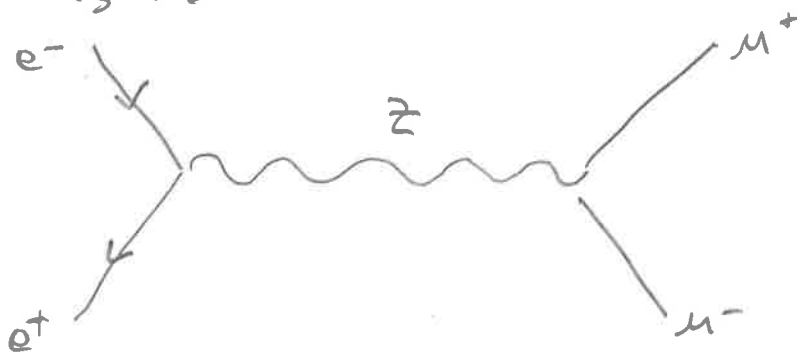

complicated  
many dimensional  
integrals

← (Feynman Diagram) →


Complex  
Numbers  
(Amplitudes)

Rate of Process  $\sim | \text{Amplitude} |^2$

Just a bit like


Diff Eq

$$V = \frac{dq}{dt} R + \frac{q}{C}$$

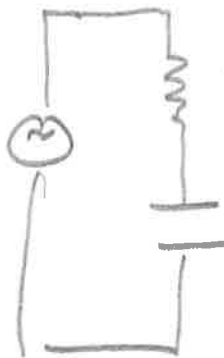

$$Z_R = R$$

$$Z_C = \frac{1}{j\omega C}$$

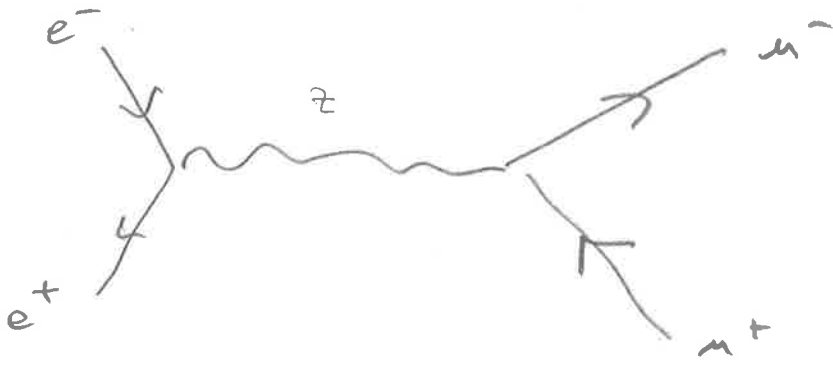


$$s = E_{\text{cm}}^2$$



$$M_Z \sim \frac{1}{(s - m_Z^2) + i\Gamma_Z}$$

$$|M_Z|^2 = \frac{1}{\Gamma_Z^2 + (s - m_Z^2)^2}$$

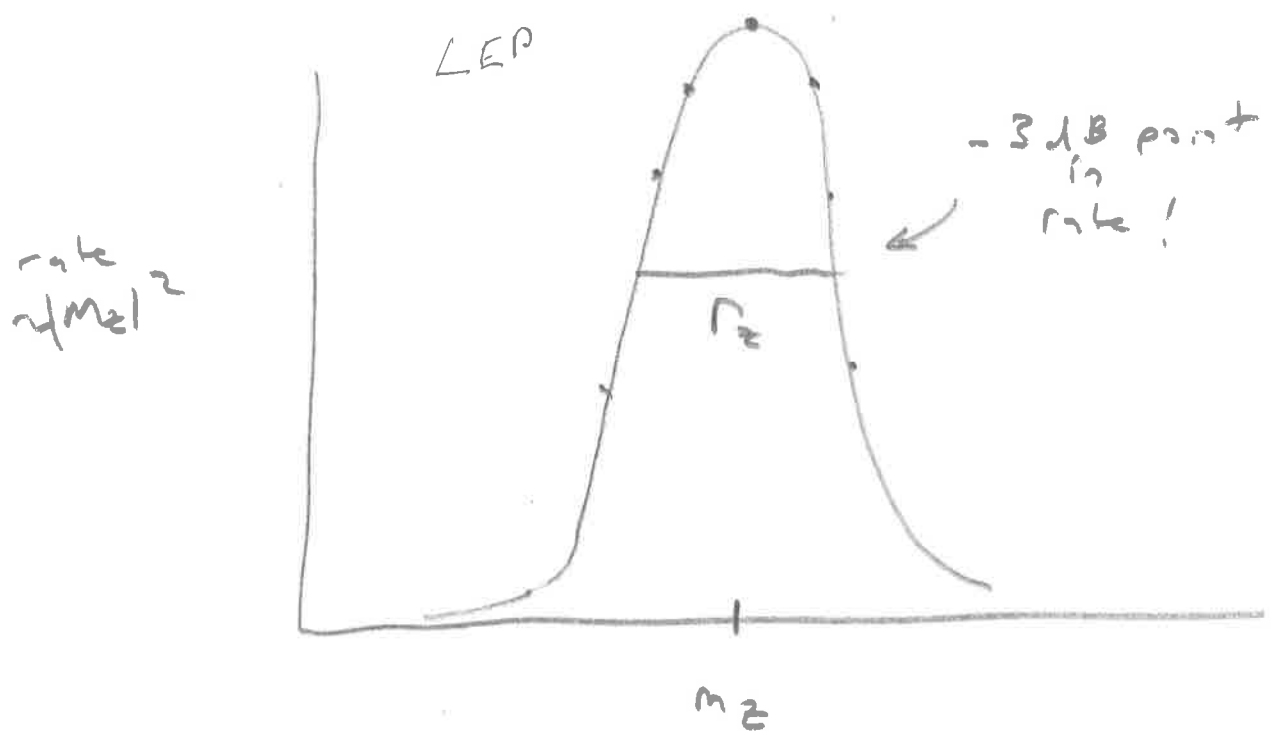

LEP measurement of  $m_Z$  and  $\Gamma_Z$   
 remains unbeatable today... Resonance!



## Interference

$$M_Z \sim \frac{1}{(s - m_Z^2) + i\Gamma_Z}$$


$$M_\gamma \sim \frac{1}{s}$$

In QFT, like QM, processes interfere:

$$\begin{aligned} |M_{\gamma Z}|^2 &= M_Z^* M_\gamma + M_Z M_\gamma^* \\ &= \frac{(s - m_Z^2)}{s [(s - m_Z^2)^2 + \Gamma_Z^2]} \end{aligned}$$

At  $s = m_Z^2$  interference goes to zero at  $s = m_Z^2$

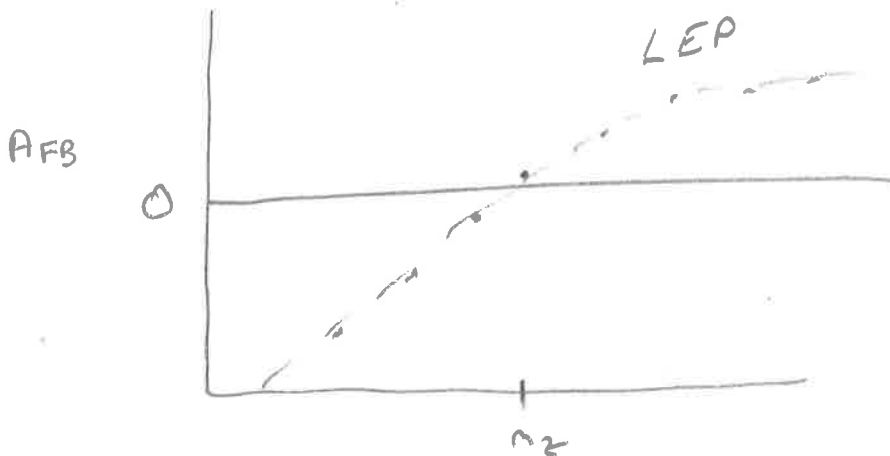(LC circuit, phase goes to zero  $\omega = \omega_0$ )



→ Double back:

⇒ Power in reactive circuits

→ Goes to zero


⇒ Power company story

(Different pricing for large  
reactive loads in capacitor  
banks at factories)

## Transformer

A transformer consists of two interlinked inductors, with different number of turns,

primary

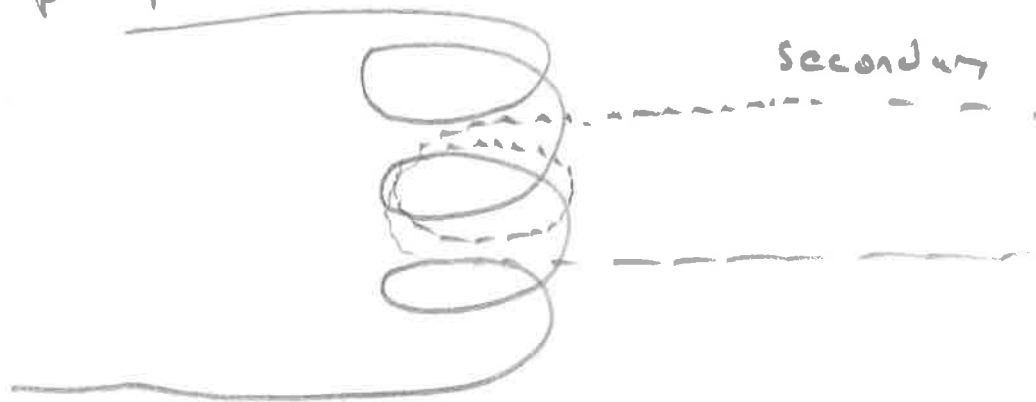

Trick is they share the same

flux!

$$\vec{\nabla} \times \vec{E} = - \frac{\partial \vec{B}}{\partial t}$$

$$\int \vec{\nabla} \times \vec{E} \cdot d\vec{A} = - \int \frac{\partial \vec{B}}{\partial t} \cdot d\vec{A}$$

$$\int \vec{E} \cdot d\vec{l} = - \frac{\partial}{\partial t} \int \vec{B} \cdot d\vec{A}$$


$$\frac{E \cdot l}{\text{per loop}} = - \frac{d}{dt} B A = E \cdot l /_s = V_{\text{loop}}$$

$$V_p = n_p V_{\text{loop}}$$

$$V_s = n_s V_{\text{loop}}$$

$\Rightarrow$
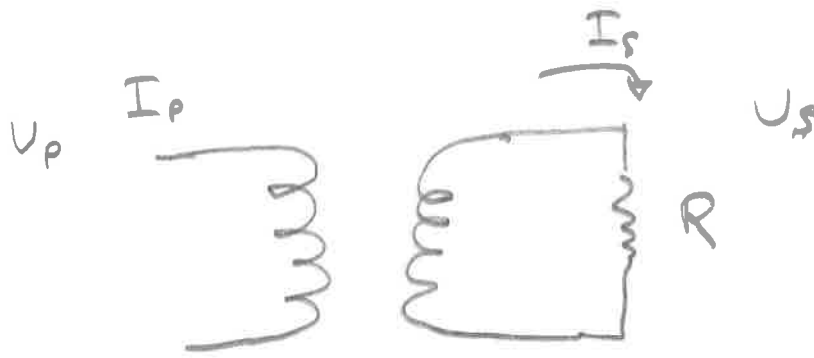
$$\boxed{\frac{V_p}{V_s} = \frac{n_p}{n_s} = a}$$




Apparent Load

$$R_a = \frac{V_p}{I_p} = \frac{a V_s}{I_s / a} = a^2 \frac{V_s}{I_s} = a^2 R$$

$$R_a = a^2 R$$

Step - Up

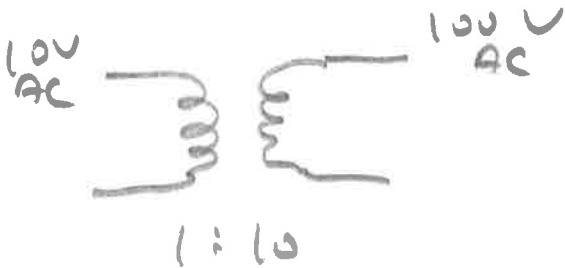

Step Down



Ideal Transformer:

Power In = Power Out

$$\frac{V_p}{V_s} = \frac{n_p}{n_s} = a$$

$$P_{in} = V_p I_p = P_{out} = V_s I_s$$

$$\Rightarrow \frac{I_p}{I_s} = \frac{V_s}{V_p} = \frac{1}{a}$$