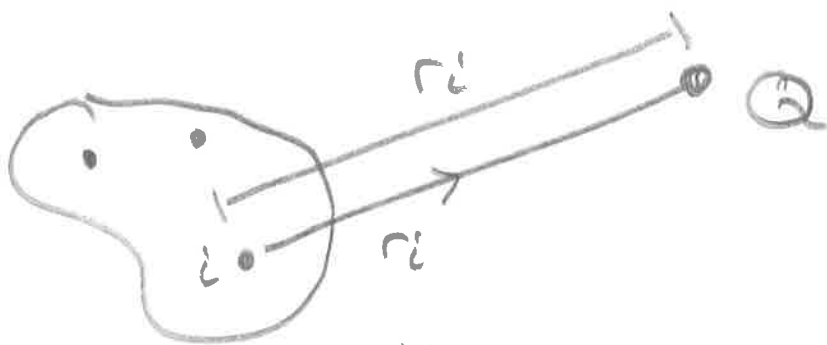


RLC

Circuits

Chapter 1 : DC Circuits
and Resistance

Electric Field:



$$\vec{F} = Q k_e \sum_{i=1}^N \frac{q_i}{r_i^2} \hat{r}_i$$

$$\vec{E} = \frac{\vec{F}}{Q} \text{ is independent of } Q,$$

$$\vec{F} = \vec{E} Q$$

Electric Potential

Electric Force is conservative


$$U_{ab} = -W_{esu} = - \int_a^b F_x dx$$

"Change in potential energy going from $a \rightarrow b$,"

$$V_{ab} = \frac{U_{ab}}{Q} = - \int_a^b E_x dx$$

"Change in electric potential going from $a \rightarrow b$."

$$V = - \int_a^b E \, dx$$

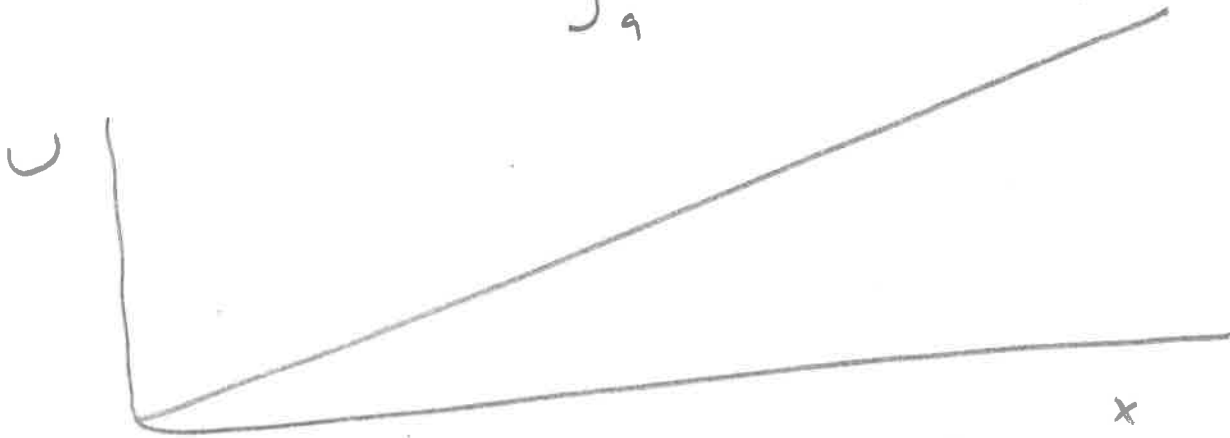


⊖ "Fall" toward high V

⊕ "Fall" toward low V

Unit of Electrical Potential is

Volt (V)

$$1 \text{ V} = 1 \text{ J/C}$$

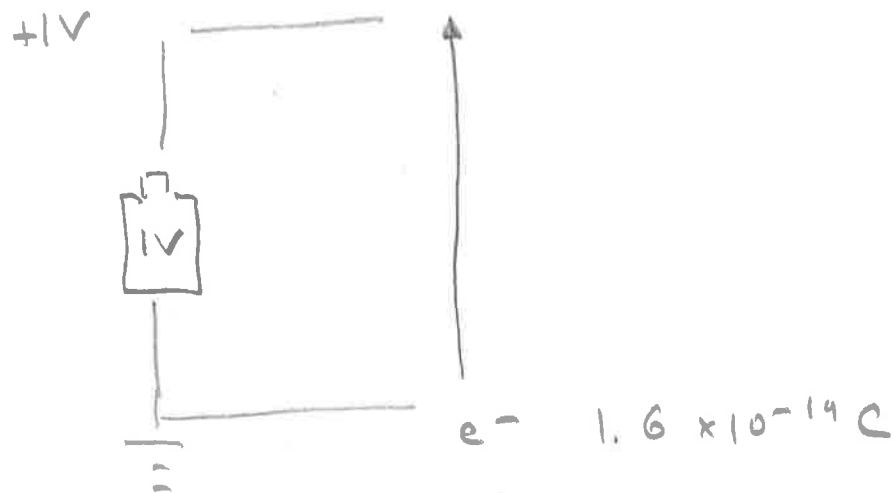


$$K = 1.6 \times 10^{-19} \text{ J} \equiv 1 \text{ eV}$$

Volt is at useful scale in many contexts.

- your car battery (12), tower (120V)
- Kinetic energy of photo-electron ($\sim 1 \text{ eV}$)
- CMB energy density 0.25 eV/cm^3

Circuit Diagrams

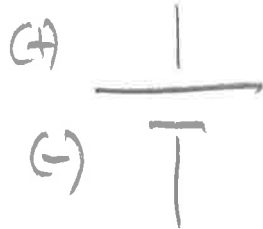

Cell




Battery



Voltage Source

$$U_D = 5$$

eg.

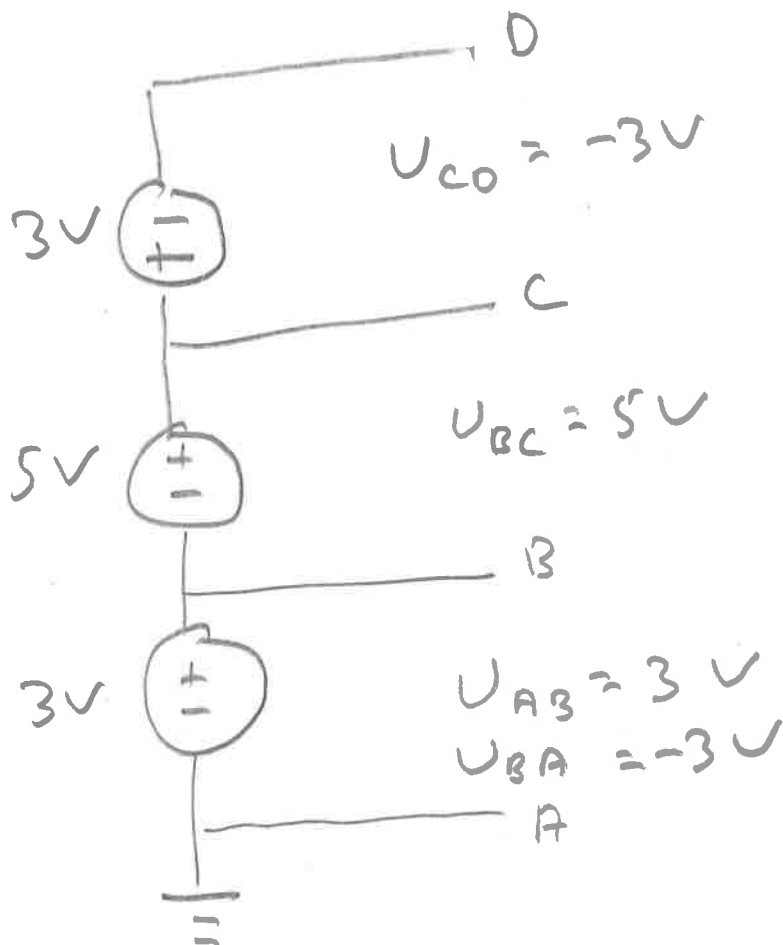

$$U_C = 8$$


$$U_B = 3$$

$$U_A = 0$$

$$U_{AC} = 8V$$

$$U_{CA} = -8V$$

Conductors and Insulators

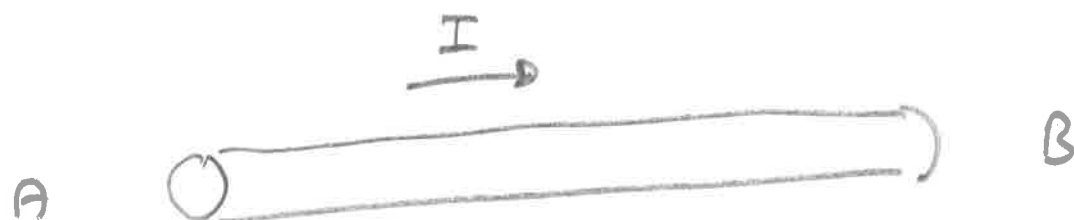

$$I = dQ/dt$$

Conductors have mobile charge carriers which readily conduct.

$\Rightarrow E = 0$ inside conductor
(else, charges rearrange)


$\Rightarrow \Delta V$ across conductor is 0.

$V_{AB} = 0 \Leftrightarrow$ short circuit

symbol:  wire

* Treat good conductors as if ideal *

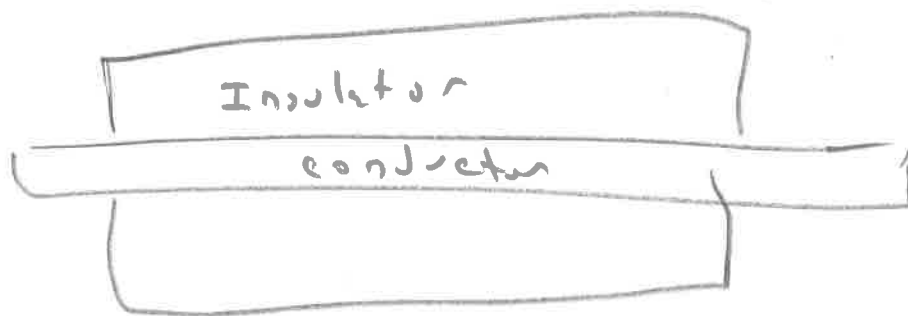
Insulators: Do not readily conduct,
Implicit in diagrams,



Resistors

Mix graphite (conductor) and ceramic dust (insulator) held together with resin, build

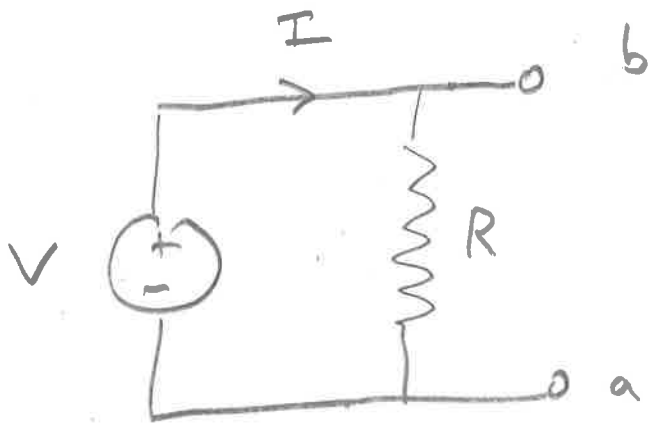resistor \rightarrow mobile charges that do not readily conduct



Ohm's Law

$$V = I R$$

$$1 \Omega = 1 \frac{V}{A}$$

Note sign:

$$V_{ab} = I R$$

$a \rightarrow b$ free current

$$V_{ba} = -I R$$

$b \rightarrow a$ with current

Conductors

$$R \sim 0$$


Insulators

$$R \rightarrow \infty$$


All materials break down and conduct at some V ,

Kirchhoff's Laws

Conservation of charge (KCL)

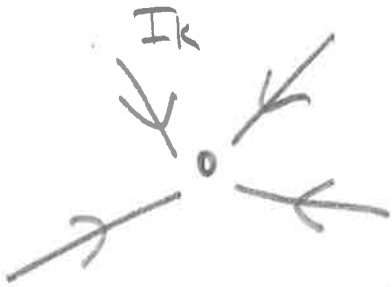

$$\sum_k I_k = 0$$

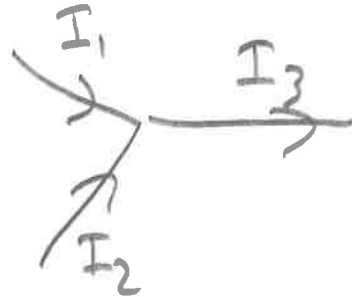

$$I_1 + I_2 = I_3$$

Electric Field is conservative (KVL):

$$\sum_k V_k = 0$$




$$I_1 = I_2 + I_3$$

$$0 = -I_1 R_1 + V_1 - I_2 R_2 - I_1 R_4$$

$$0 = R_2 I_2 - R_3 I_3 - V_2 - I_3 R_5$$

$$0 = -I_1 R_1 + V_1 - I_3 R_3 - V_2 - I_3 R_5 - I_1 R_4$$

Exercise 2

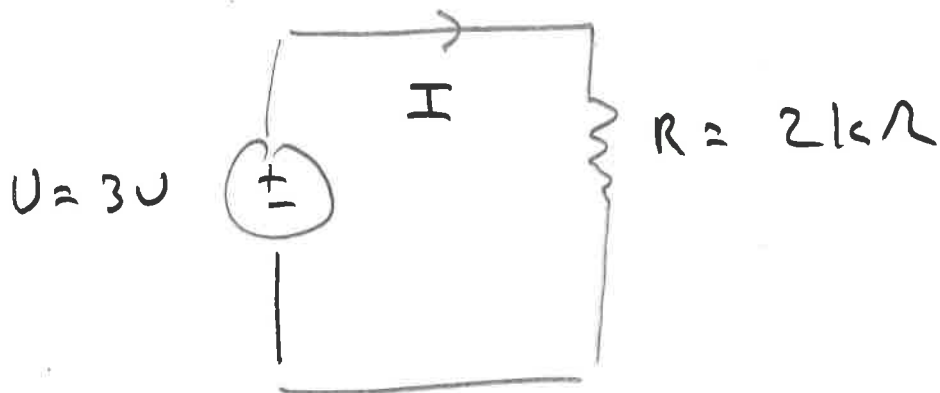

$$0 = U - IR$$

$$I = U/R = \frac{3V}{2k\Omega} = \boxed{\frac{3}{2} \text{ mA}}$$

Loop in other direction

$$0 = (-U) + IR \Rightarrow I = \frac{U}{R} = \frac{3}{2} \text{ mA}$$

"I" in other direction




$$0 = U + IR$$

$$I = -\frac{U}{R} = \boxed{-\frac{3}{2} \text{ mA}}$$

* Always draw current directions and note the signs *

Exercise 2:

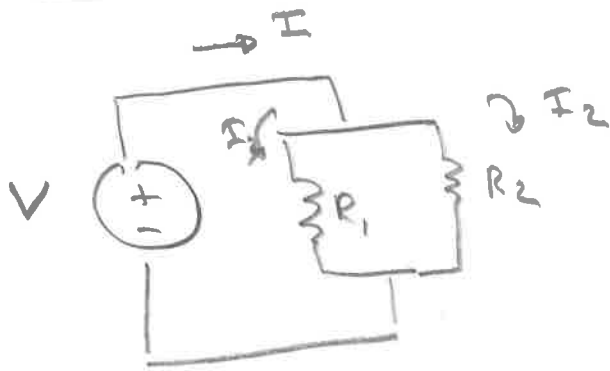

$$I = I_1 + I_2$$

$$U = I_1 R_1$$

$$U = I_2 R_2$$

$$I = \frac{U}{R_1} + \frac{U}{R_2}$$



$$I = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) U$$

As if


$$I = \frac{1}{R_{eq}} U$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

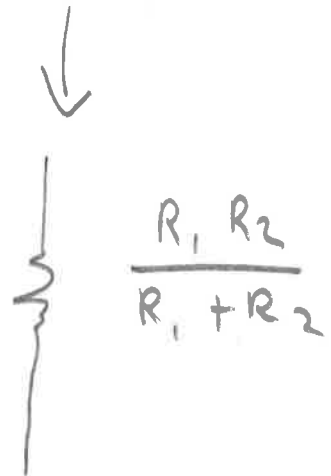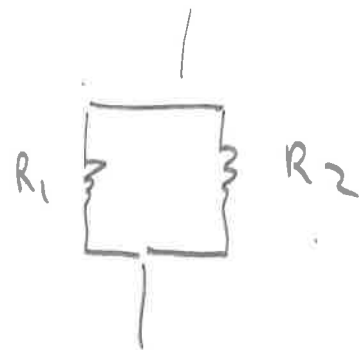

Example 3

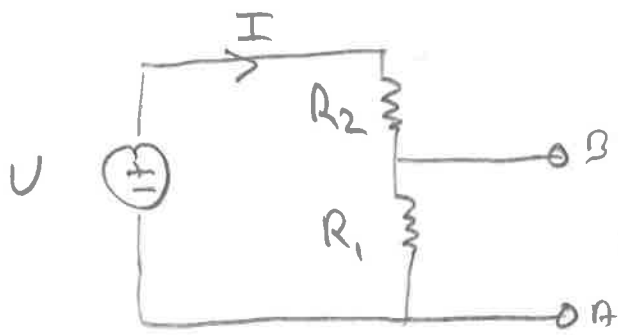

$$I = ?$$


$$V_{AB} = ?$$

$$0 = U - IR_2 - IR_2$$

$$U = IR_2 + IR_1$$
$$= (R_1 + R_2) I$$

$$I = \frac{U}{R_1 + R_2} = \frac{U}{R_{eq}}$$

$$R_{eq} = R_1 + R_2$$

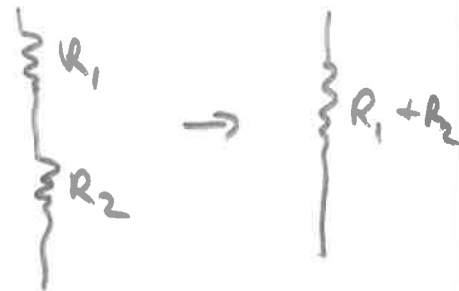


$$V_{AB} = IR_1 = \frac{R_1}{R_1 + R_2} U$$

"Take a share R_1 from the voltage across $R_1 + R_2$."


**** Ready for DC circuits Lab ****

Sources and Loads

Start simple:

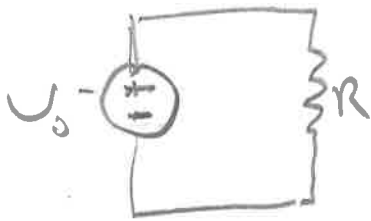





closed circuit


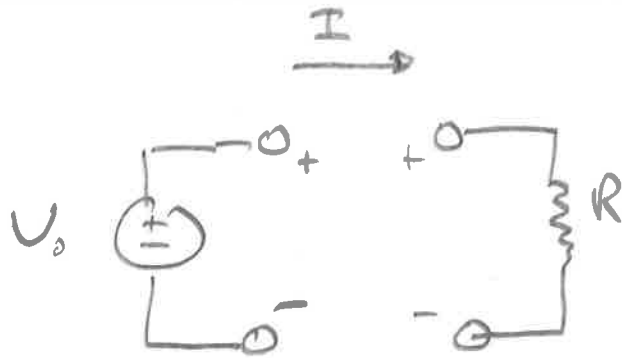


source
network
(open circuit)

load
network
(open circuit)

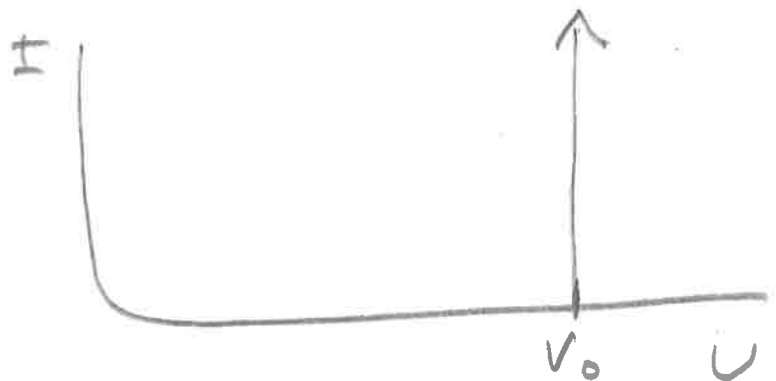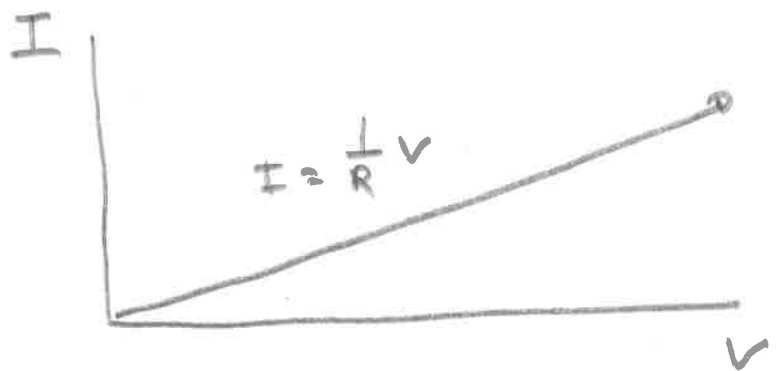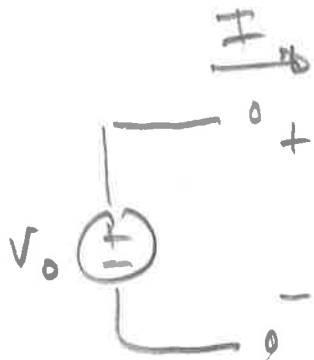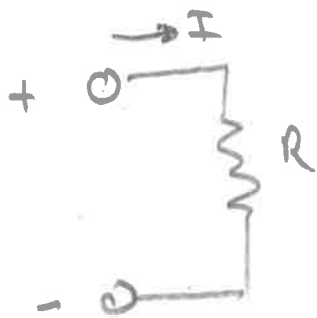Source / Load differ only in direction of current: source $+I$ is out of positive terminal, load $+I$ is into positive terminal.
(Ohm's Law defined for R in load).



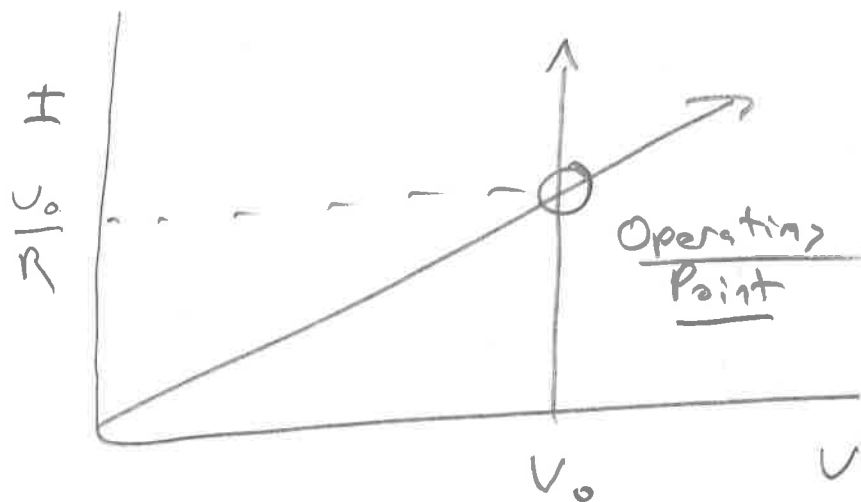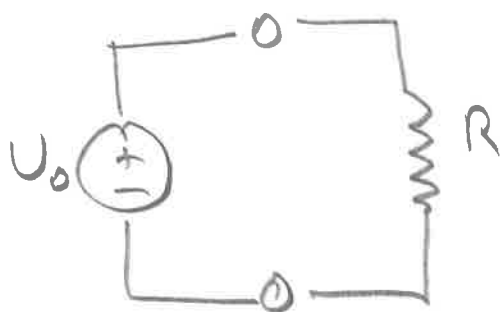

Power :




$$P \equiv \frac{dU}{dt} = \frac{V dQ}{dt} = V \frac{dQ}{dt} = VI$$

Source provides power VI

Load consumes power VI

In this case $P = VI = U_0 \left(\frac{U_0}{R} \right)$

$$P = \frac{U_0^2}{R}$$

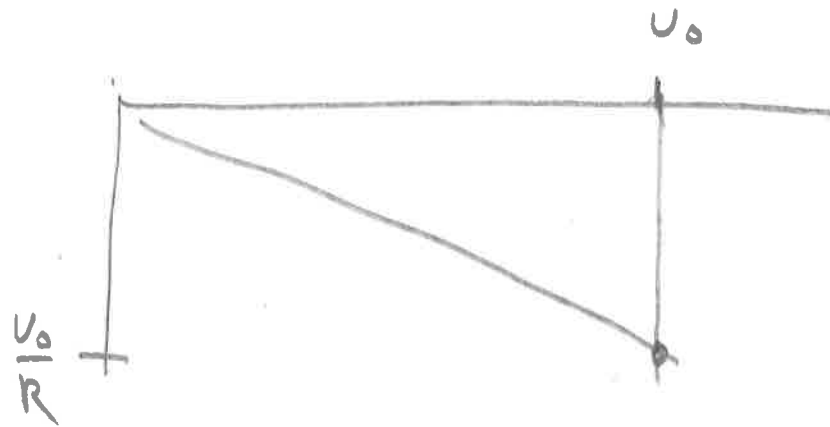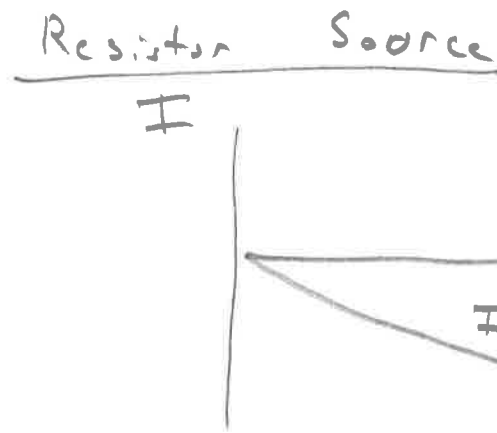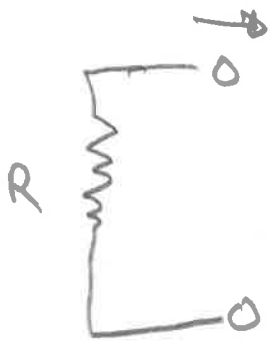


$$P = -\frac{(U_0)^2}{R}$$

source provides
negative power
load consumes
negative power,

(Maths polite way of saying
you choose source and load
wrong.)

* R in source has negative
slope *

Realistic Source

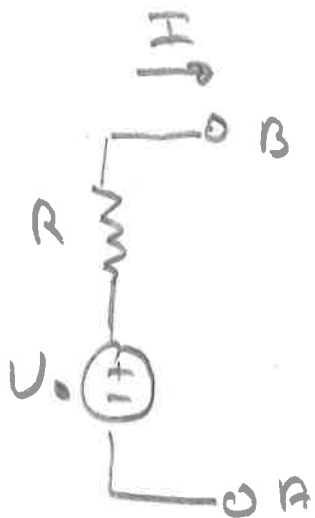

* Expect slope $-\frac{1}{R}$ *

Leave AB open:

$$I = 0$$


$$V_{AB} = U_0 = U_{oc}$$

Short AB:

$$V_{AB} = 0$$




$$I_{sc} = \frac{U_0}{R}$$

$$I_{sc} = U_0/R$$

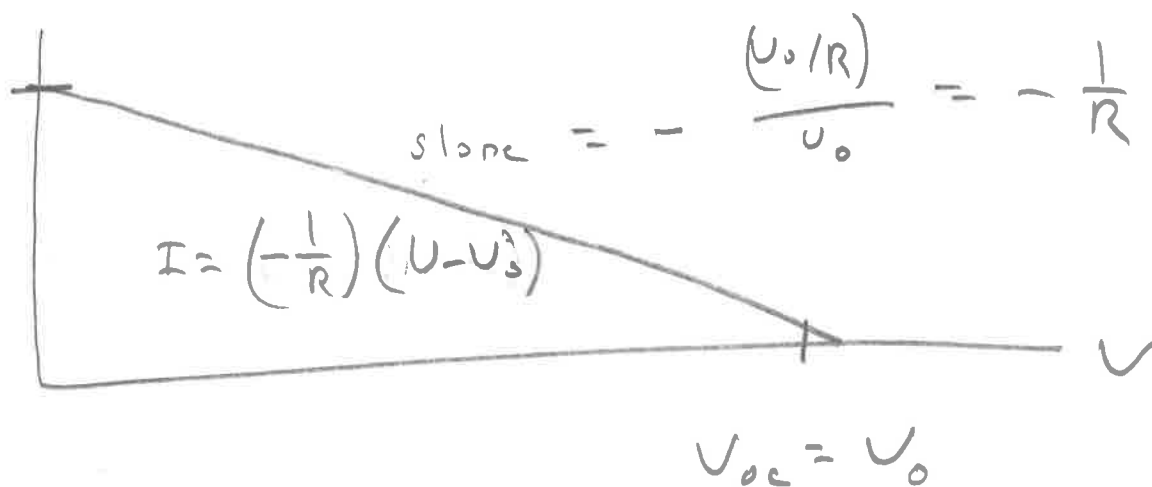

Thevenin Equivalent Circuits

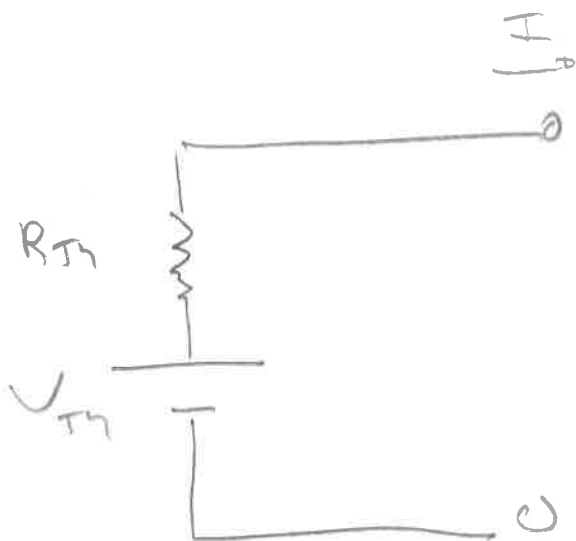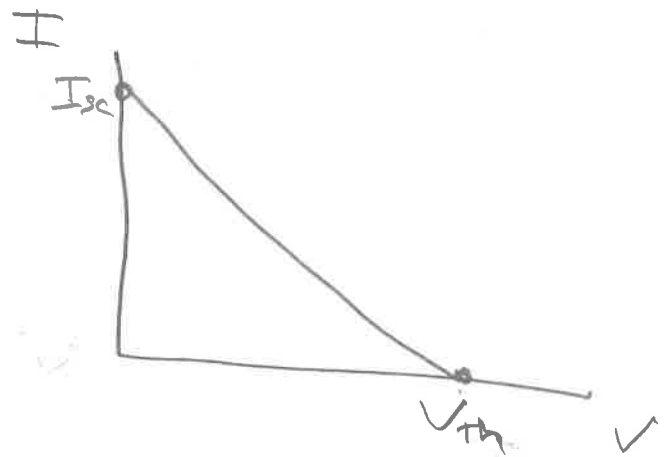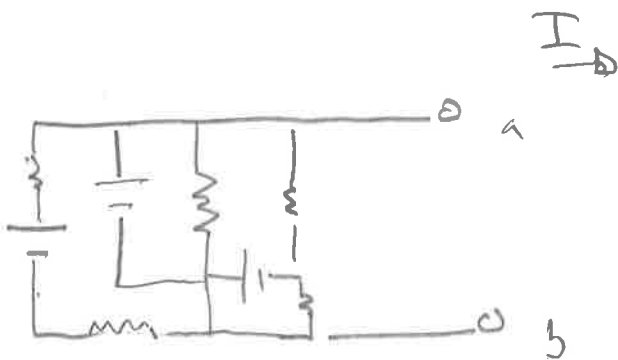Because of superposition principle of $E + M$, combining linear components always has a linear response... all circuits consisting of R , V , and I -sources have a linear I U curve.




U_{th} is open circuit voltage


I_{sc} is short circuit current

$$R_{th} = U_{th} / I_{sc}$$

Original Circuit: (Thevenin Lab)

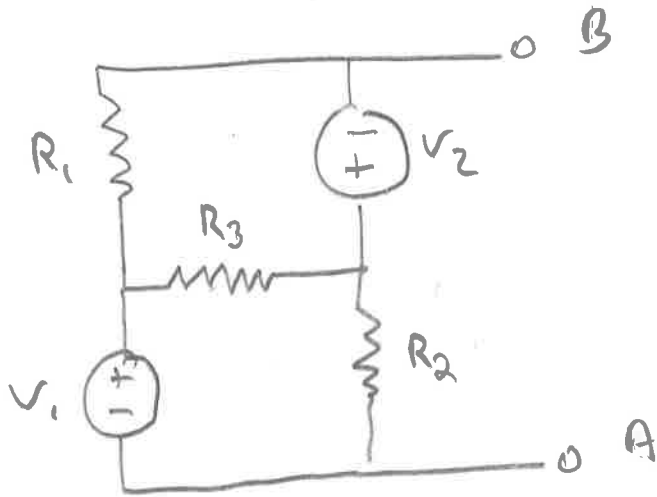


For R_{th} set $V_1 = V_2 = 0$

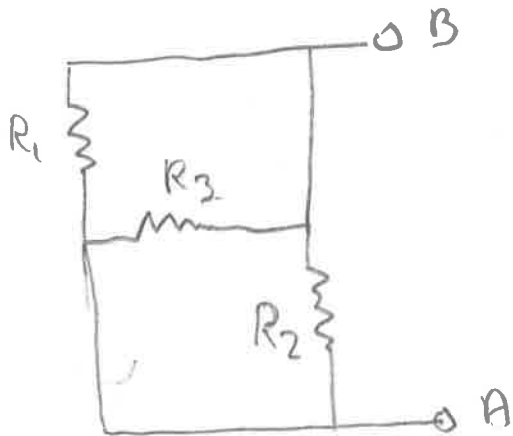

Looks complicated but
don't be fooled!

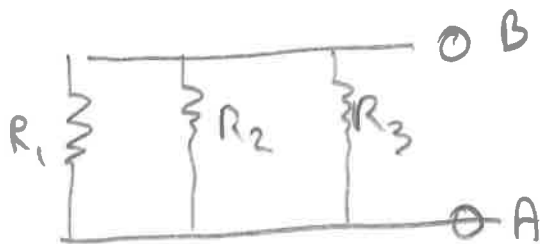Each resistor connects
to point a and
b directly




$$R_{th} = R_1 \parallel R_2 \parallel R_3$$


$$R_{th} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

For V_{th} , use superposition. First set

$$\underline{U_2 = 0}$$

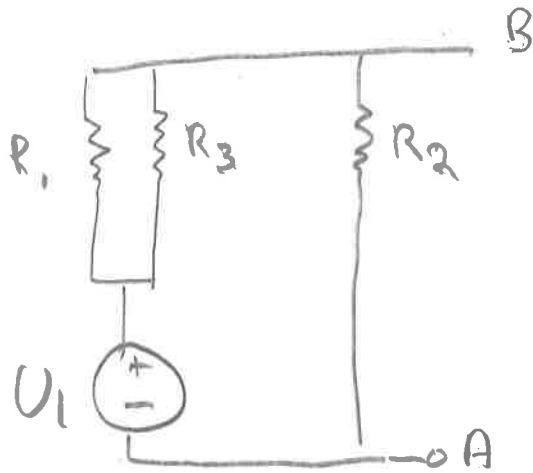


→

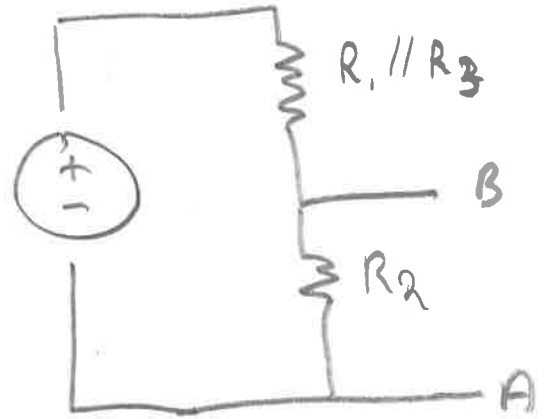


$$U_{Th}^{(1)} = U_{AB} = \frac{R_2}{R_2 + R_1 \parallel R_3} U_1$$

$$\underline{U_1 = 0}$$

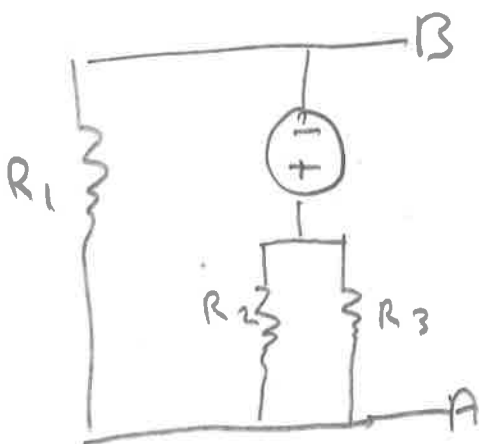

→

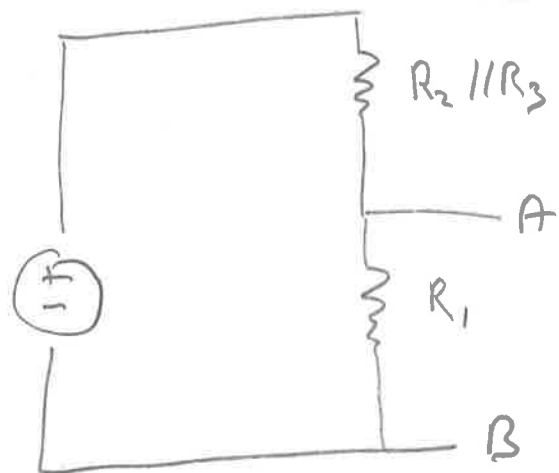

$$U_{Th}^{(2)} = U_{AB} = -U_{BA} = -\left(\frac{R_1}{R_1 + R_2 \parallel R_3}\right) U_2$$

* Ready for Thevenin Lab *

$$U_{Th} = U_{Th}^{(1)} + U_{Th}^{(2)}$$

$$= \frac{R_2}{R_2 + R_1 // R_3} U_1 - \frac{R_1}{R_1 + R_2 // R_3} U_2$$

$$= \frac{R_2}{R_2 + \frac{R_1 R_3}{R_1 + R_3}} U_1 - \frac{R_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} U_2$$

$$(R_1 = 33 \text{ k}\Omega, R_2 = 3.9 \text{ k}\Omega, R_3 = 4.7 \text{ k}\Omega)$$