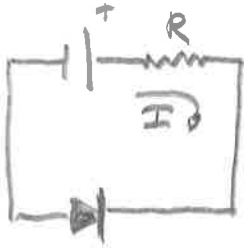





The Diode




Basic Operation





Reverse Bias

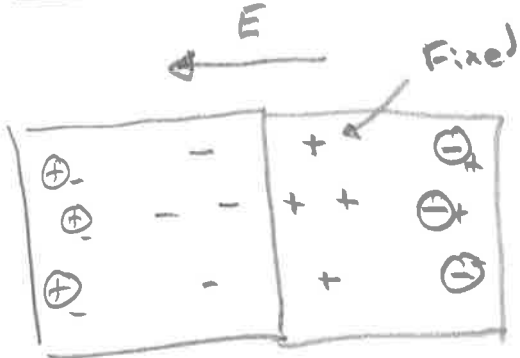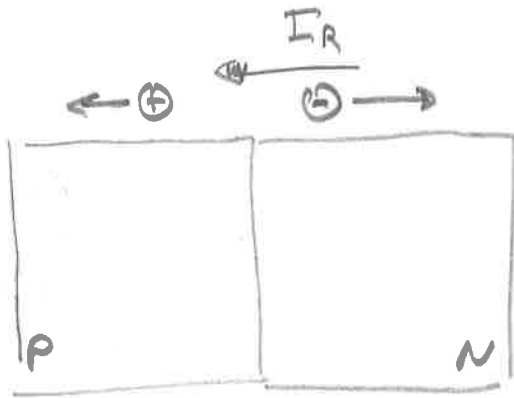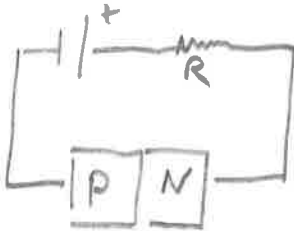

No Current

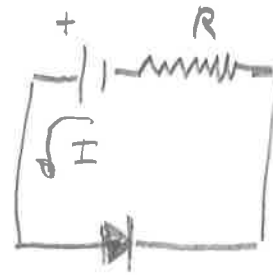


Forward Bias

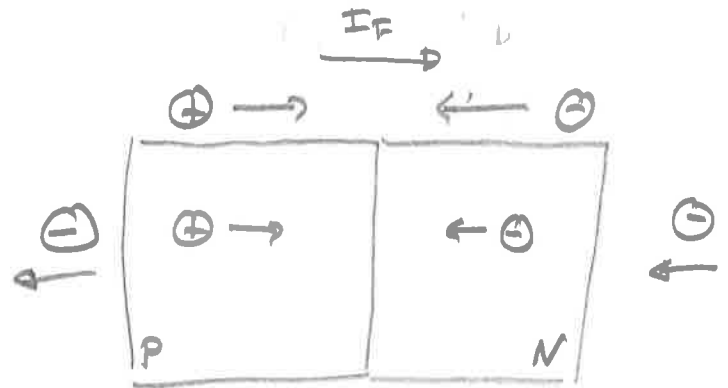
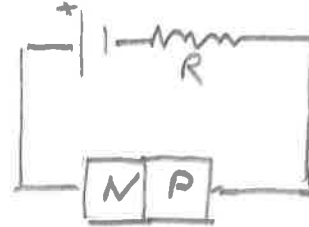


Current!

Basic Operating Model

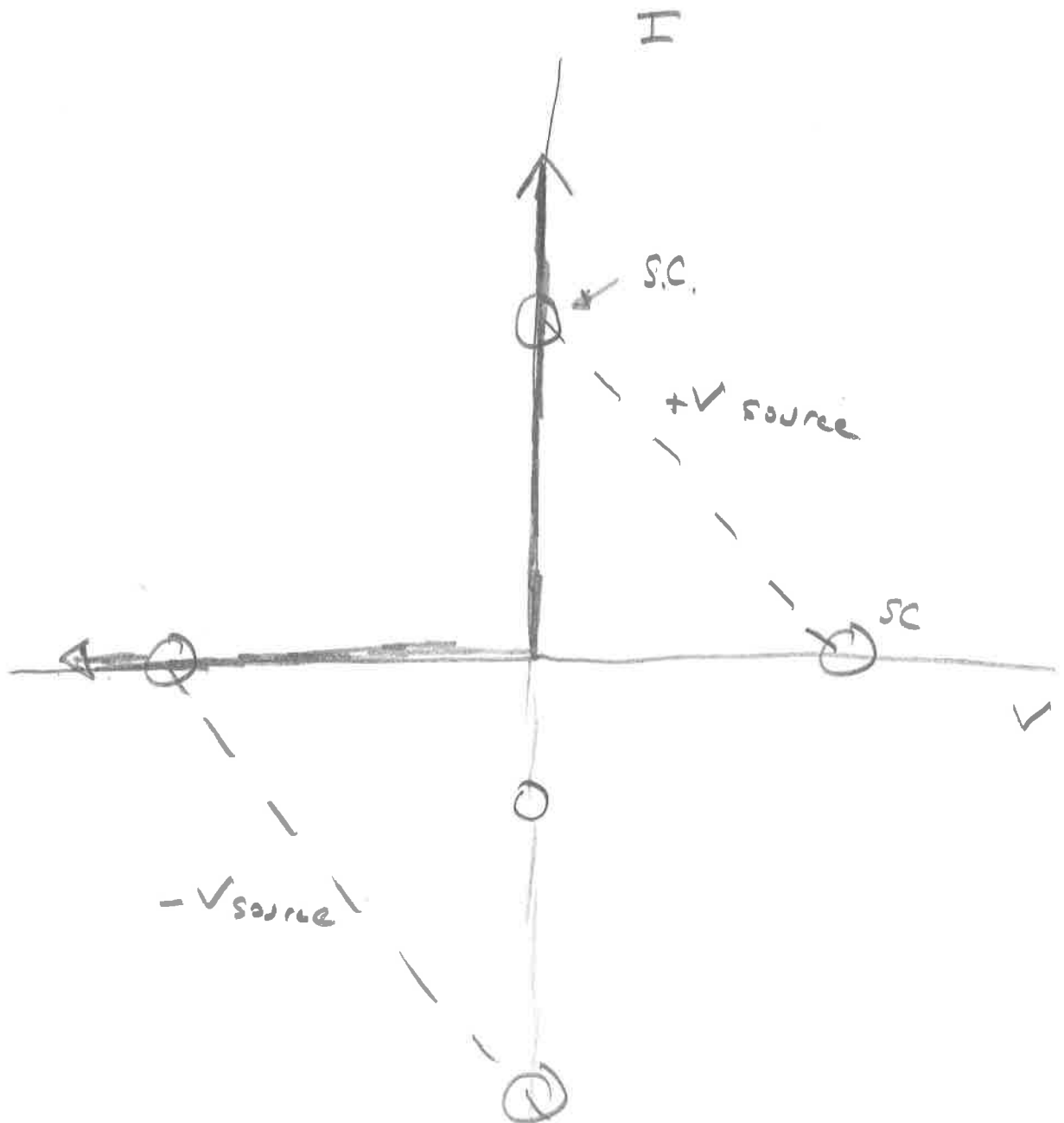



Slightly Better Model

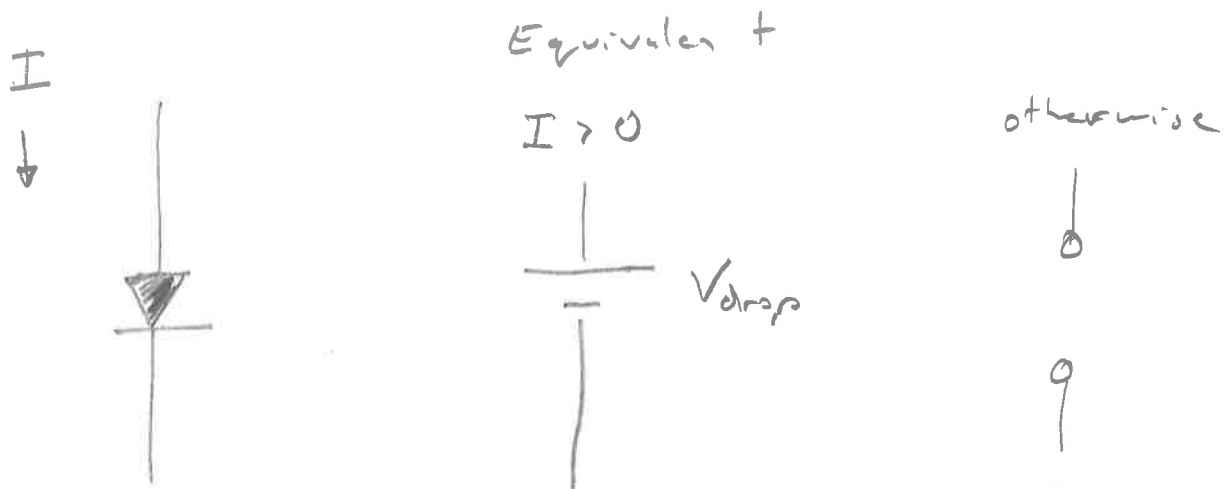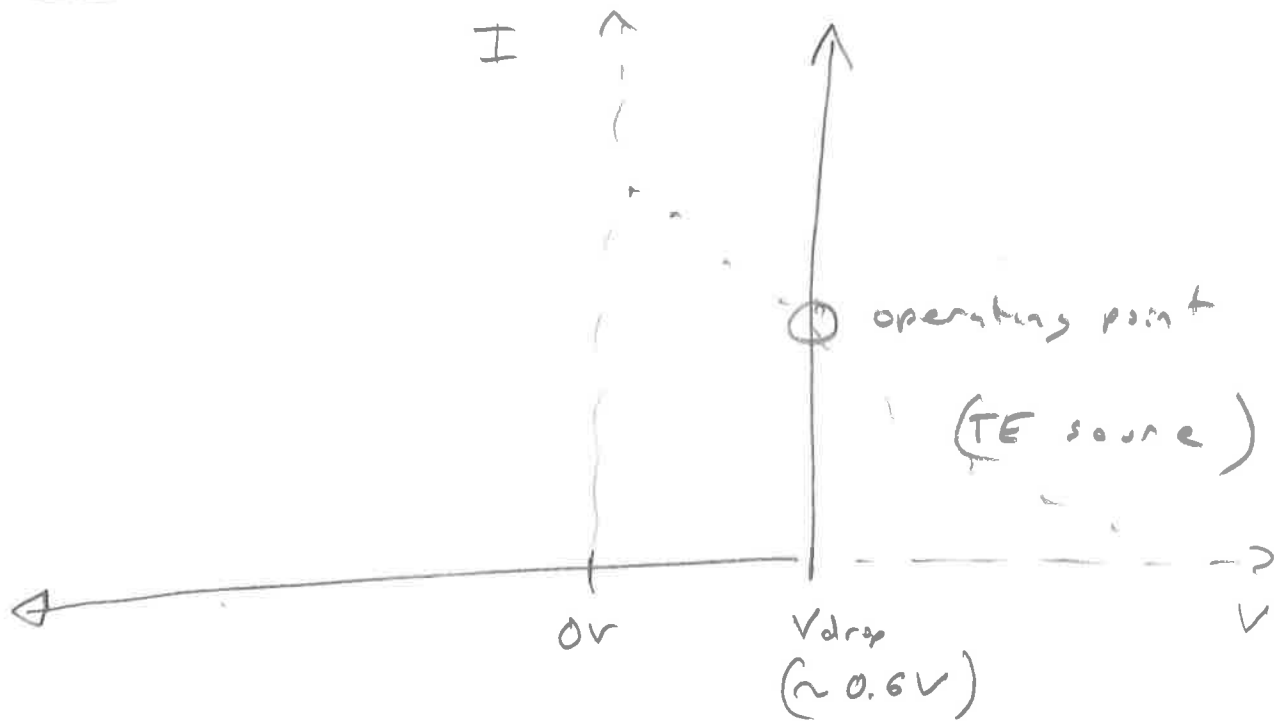



Diode allows current to flow in direction of arrow, but at a "fall" of one diode drop...





This is usually enough to understand basic diode circuits.




Diode Example Circuits;

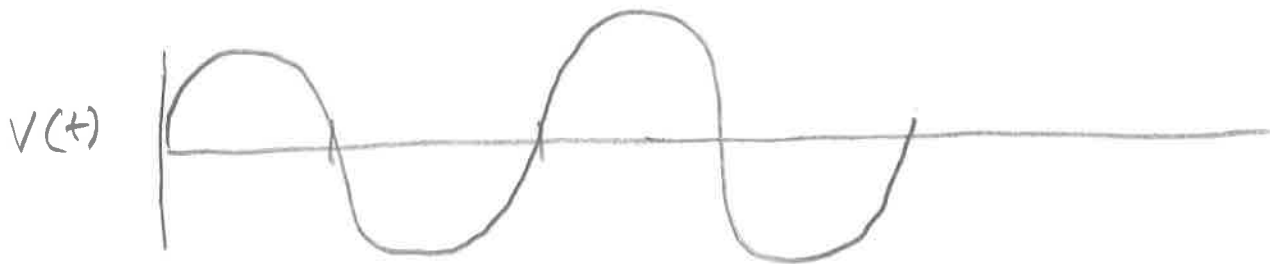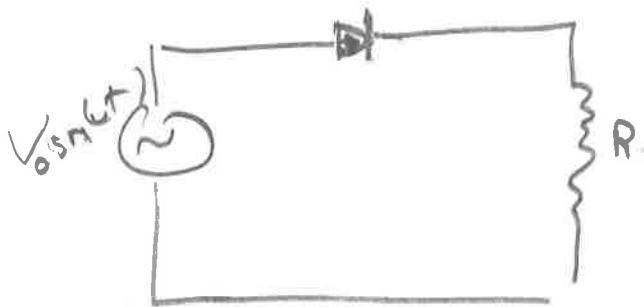

(neglecting V_{FO})

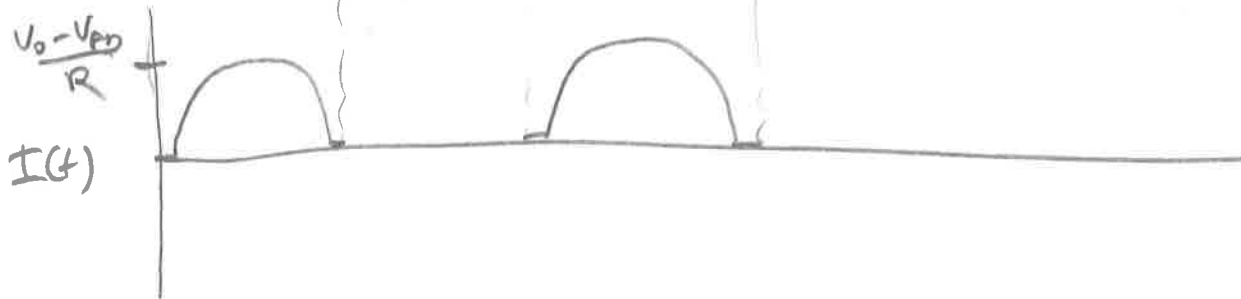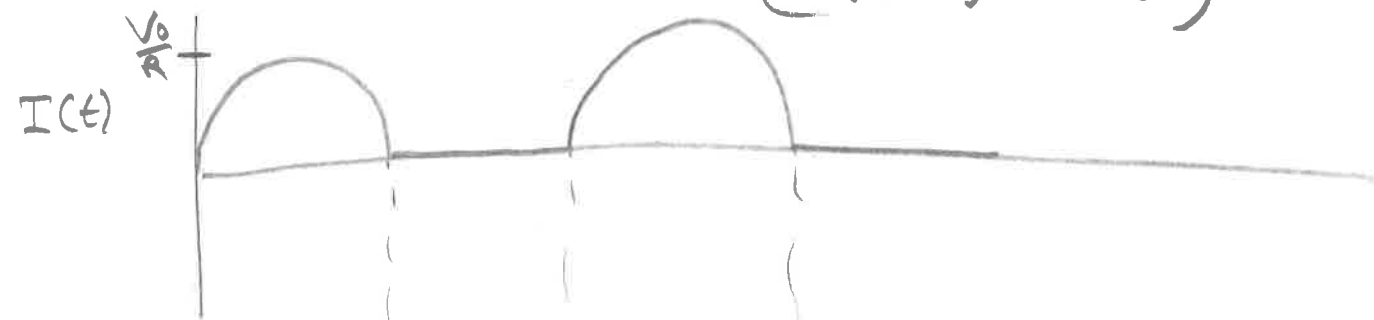

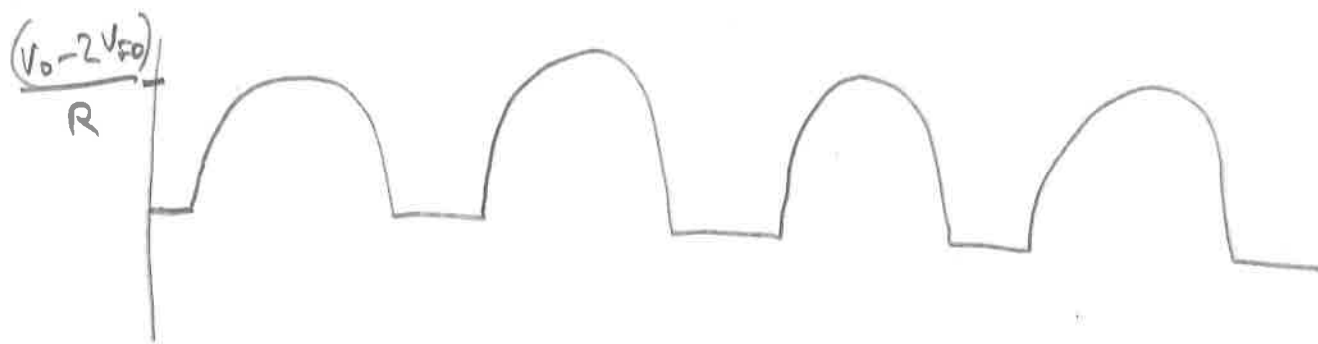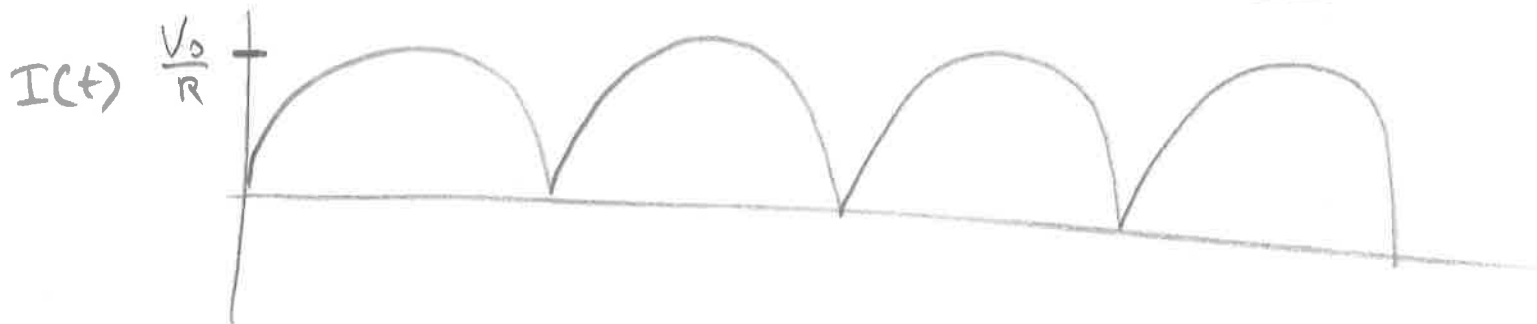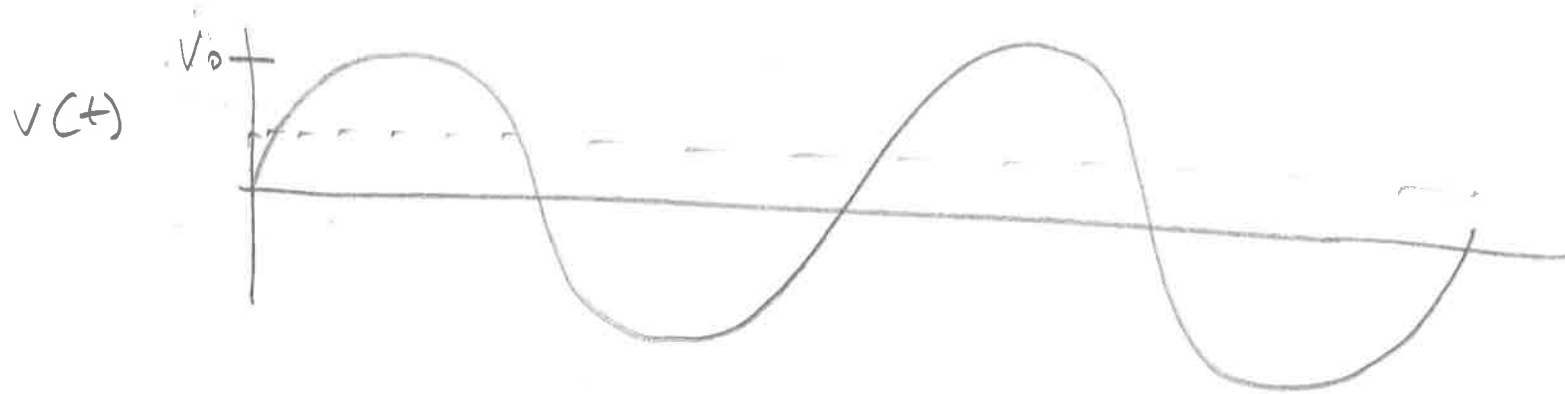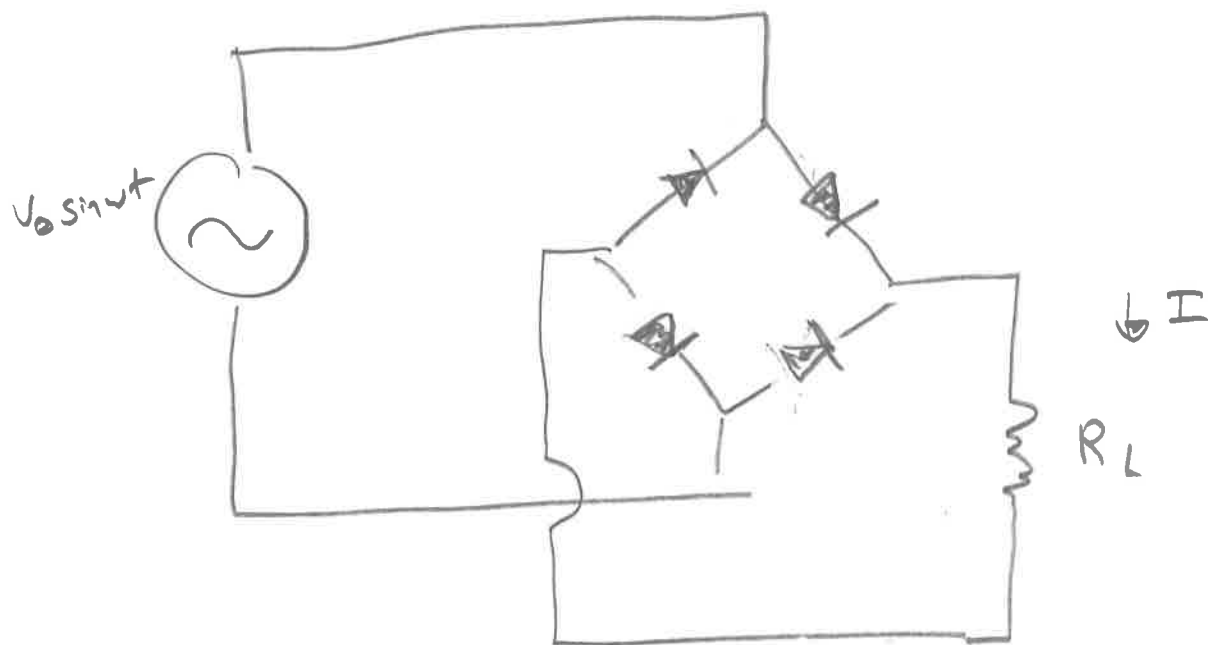

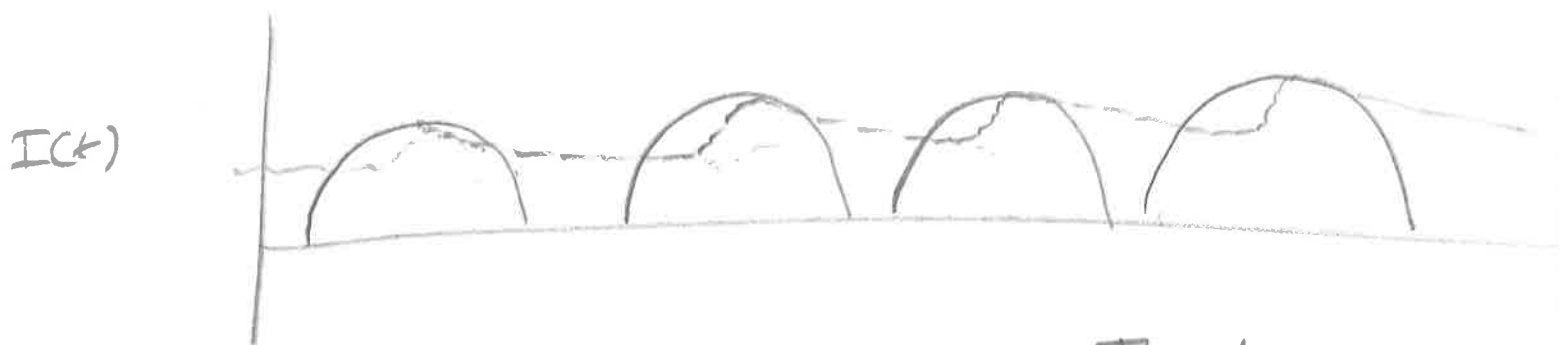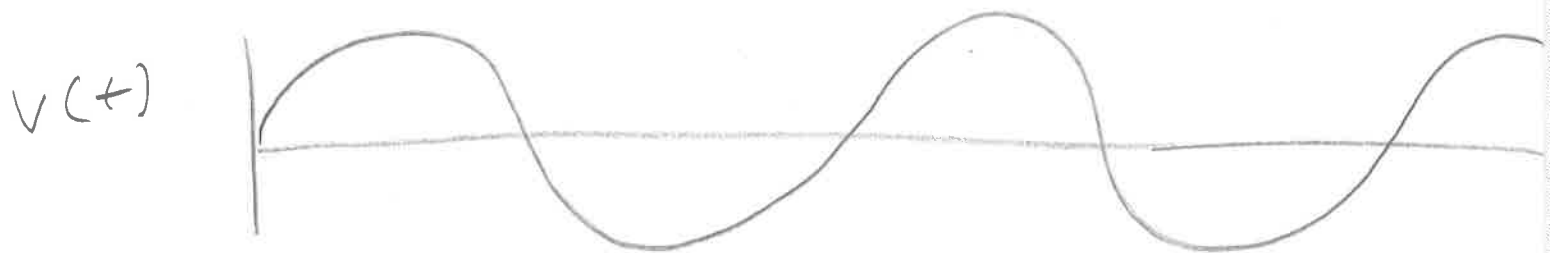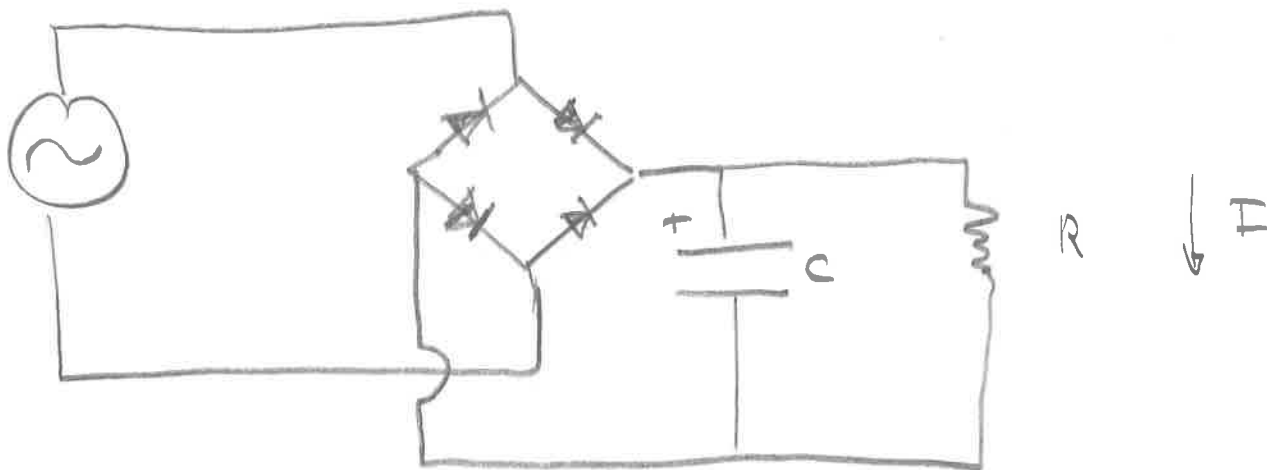

Ripple Voltage:

$$\Delta V \approx \frac{\Delta q}{C} \sim \frac{I_{max} \Delta t}{C}$$

$$f \sim \frac{1}{2\Delta t}$$

(Full-wave)

$$f \sim \frac{1}{\Delta t}$$

(half-wave)


$$\Delta V \sim \frac{I}{2fC}$$

full-wave

$$\frac{I}{fC}$$

half-wave

Diodes in Inductive Loads

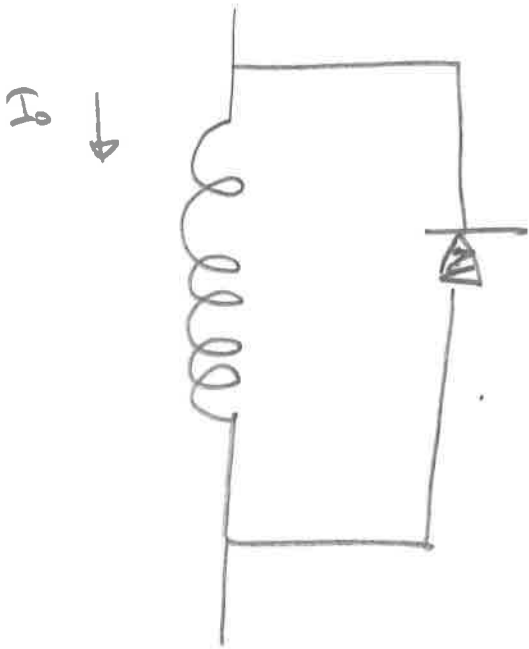


→ Diode must not break down when switch closed

→ Diode must be rated to handle

I_0 current,

Saturation Current

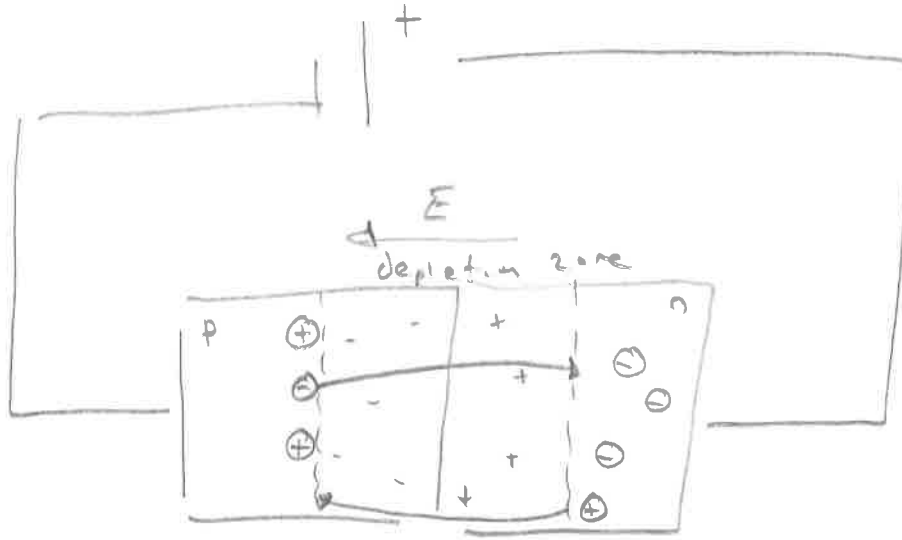

* Minority carriers, p in n -type, n in p -type, have no trouble crossing depletion zone (it's forward bias for them!)


- Thermal fluctuations near depletion zone result in a small reverse bias current

- Since field propels minority carriers across the depletion zone, rate of this current is constant.

\Rightarrow Diodes have small, nearly constant current under reverse bias.


Model of Diode in Forward Bias

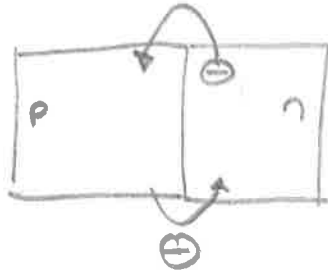At $V_{FB} = 0$, $I = 0$, system is in equilibrium. So rate of thermal generation of electron-hole pairs equals rate of recombination:



In forward-bias

$$V = V_{FB} > 0$$

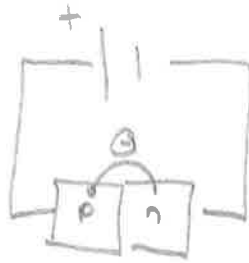

p side is at higher electric potential, so electrons in n side that combine with holes on p side now gain additional energy

$$\Delta E = q V_{FB}$$

This disturbs equilibrium ... assume generation rate is same (T hasn't changed!) so recombination increases by

$$r \sim \exp\left(\frac{\Delta E}{kT}\right) = \exp\left(\frac{q V_{FB}}{kT}\right)$$

But

$$I \sim r \sim \exp\left(\frac{V_{FB}}{V_T}\right) \quad V_T \equiv \frac{kT}{q}$$

Recap:

- 1) $V = 0$ $I = 0$
- 2) $V < 0$ $I \sim \text{const} = -I_0$
- 3) $V > 0$ $I \sim \exp(V/V_T)$

So try:


$$I = A \exp(V/V_T) + B$$

$$I(V=0) = A + B = 0 \Rightarrow A = -B$$

For $V < 0$, $|V| \gg V_T$, $\exp(V/V_T) \rightarrow 0$


$$I = B = -I_0$$

$$I = I_0 (\exp(V/V_T) - 1)$$

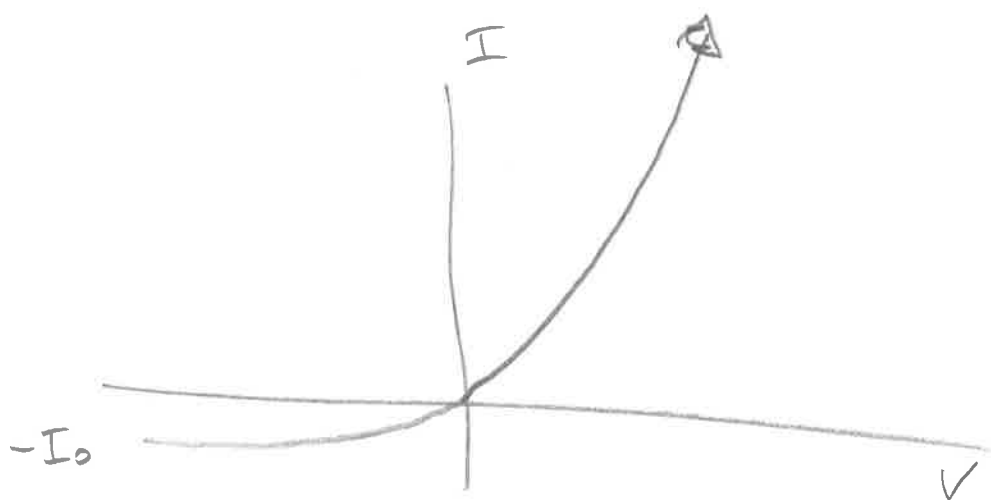


Avalanche Breakdown

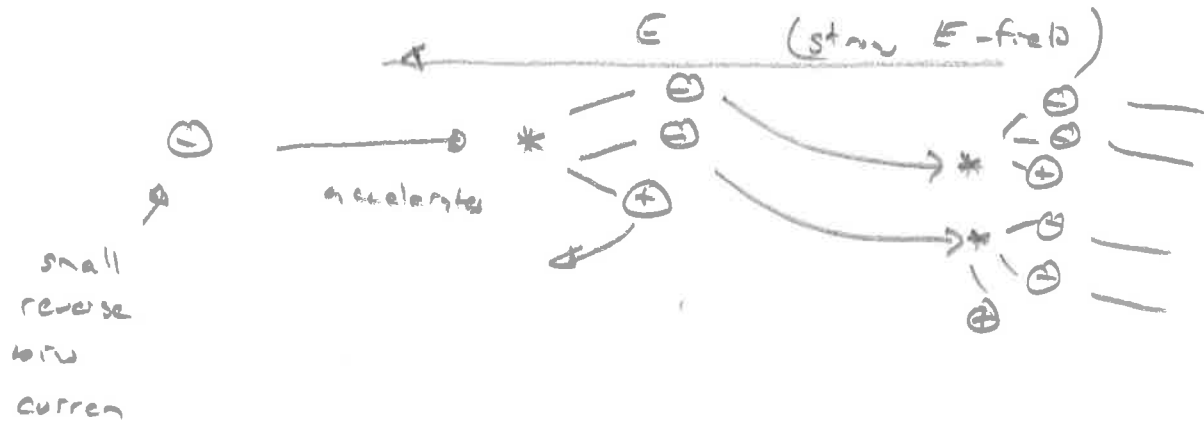IF we put large enough reverse bias voltage,




small reverse bias current is exponentially multiplied due to pair production from high energy collisions!


Zener Breakdown

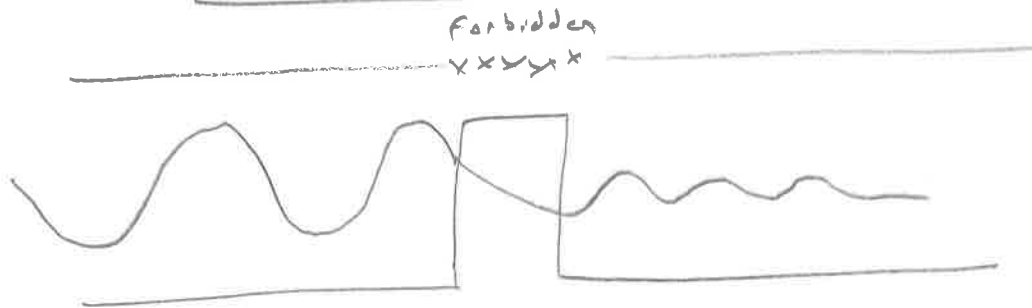

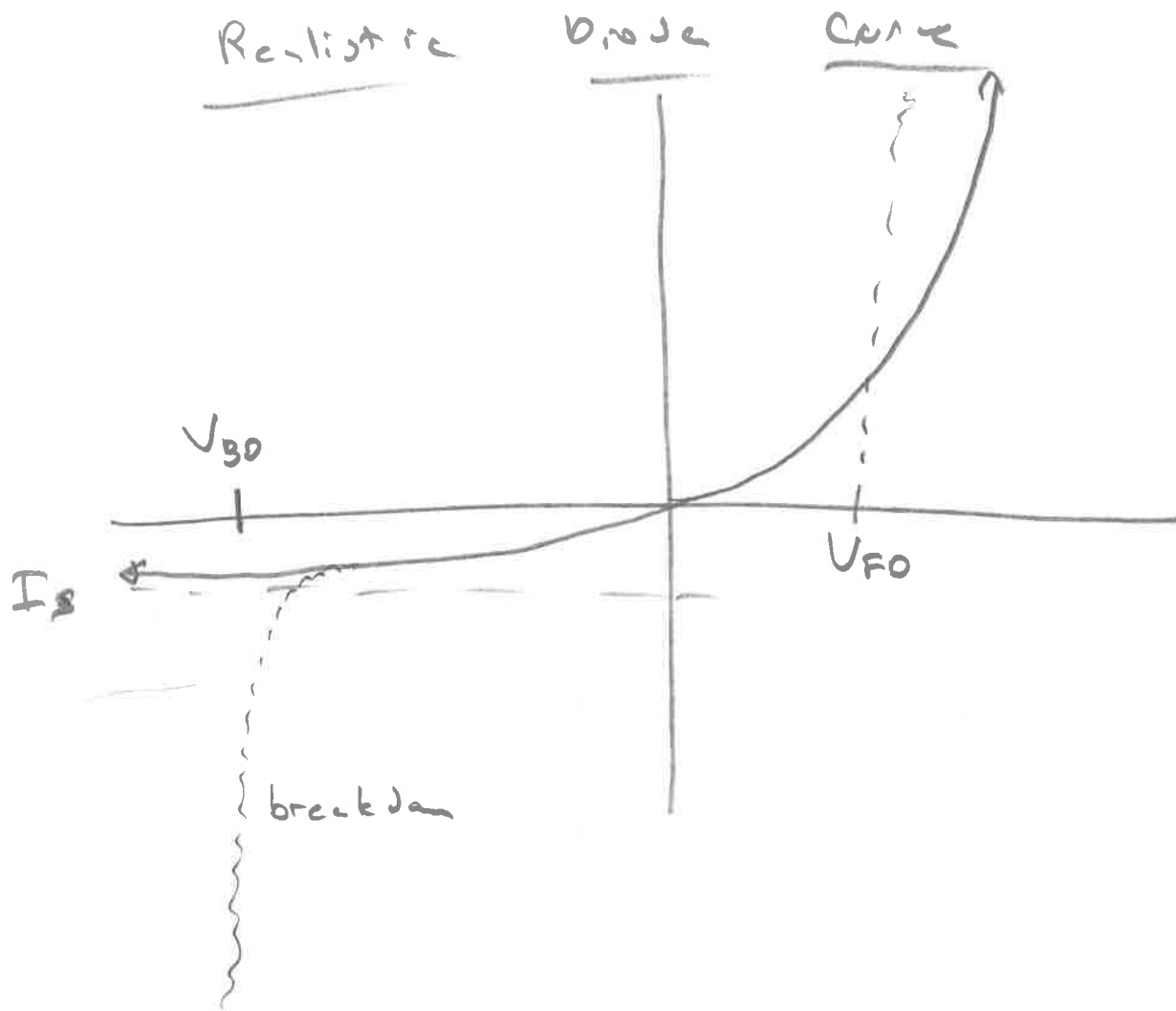Quantum tunnelling effects can allow a current to flow through the depletion region, just as a quantum mechanical particle can tunnel through a classically forbidden region.



Piece-wise Linear Approximation

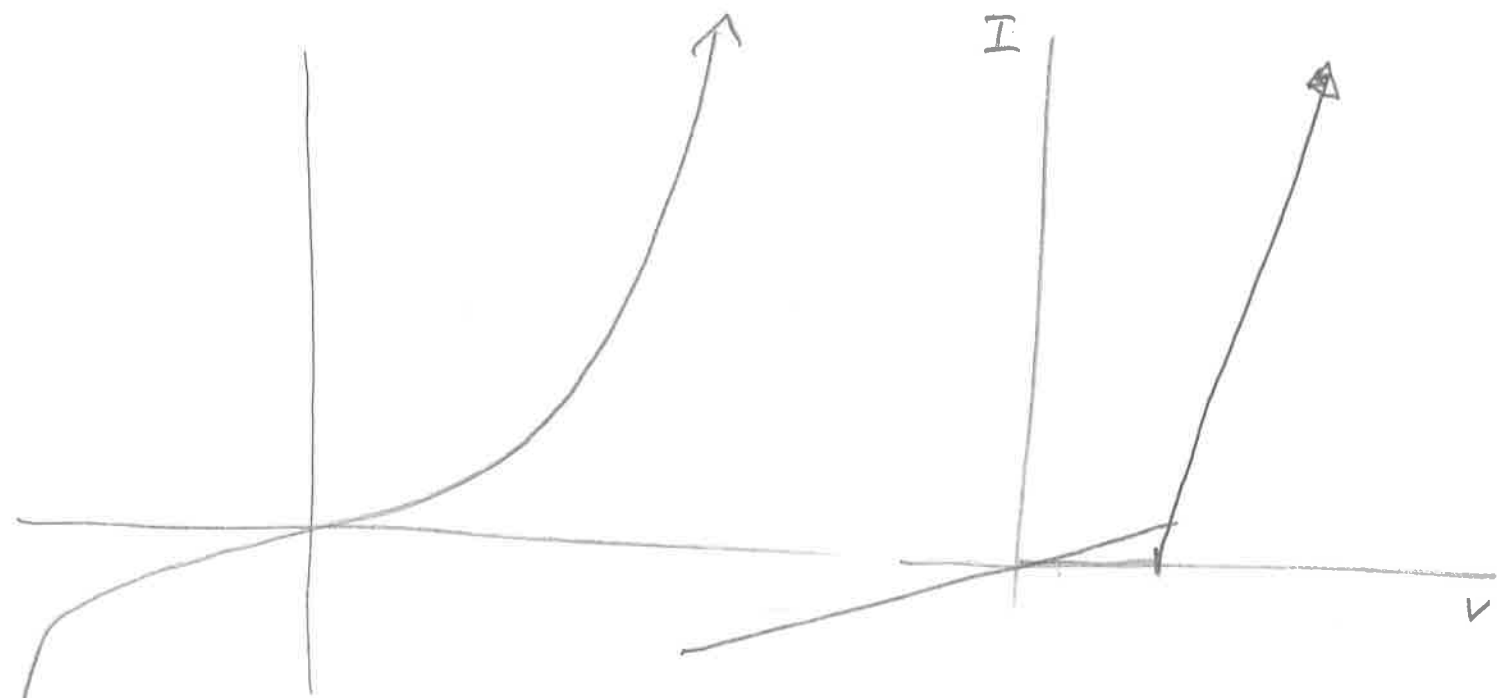

"DC load line" = T.E. for non-diode

