
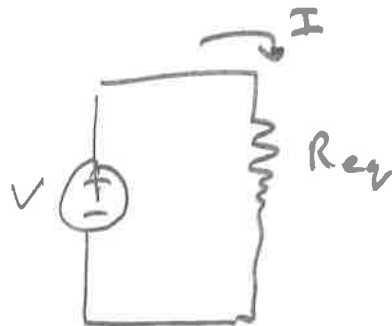


HW 1

Solution 2



1)

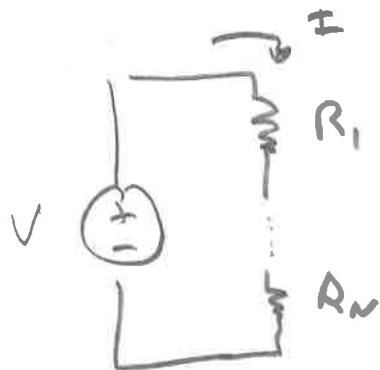

From KVL:

$$V = \sum_i R_i \cdot I = R_{eq} \cdot I$$

$$\Rightarrow R_{eq} = \sum_i R_i$$

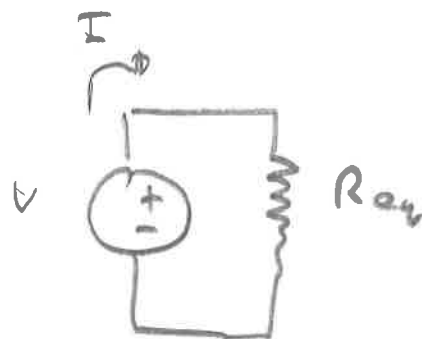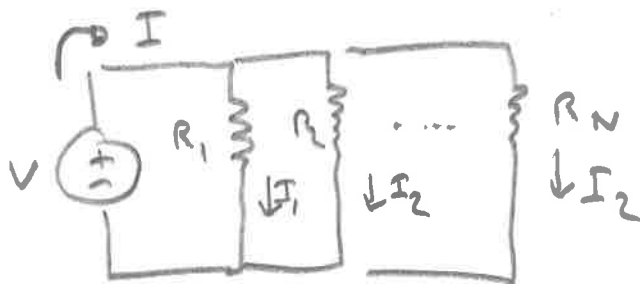

From KCL: $I = \sum_i I_i$


From KVL: $V = I R_{eq} = I_i R_i$

$$\Rightarrow I_i = \frac{V}{R_i} \quad , \quad I = \frac{V}{R_{eq}}$$

$$\Rightarrow \frac{V}{R_{eq}} = \sum_i \frac{V}{R_i}$$

\Rightarrow
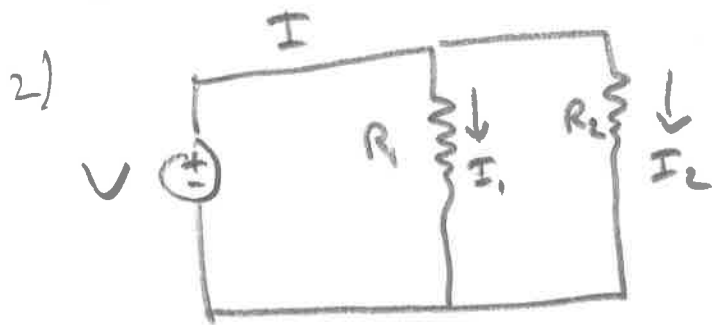
$$\boxed{\frac{1}{R_{eq}} = \sum_i \frac{1}{R_i}}$$




From KVL: $V = I_1 R_1 = I_2 R_2$

$$\Rightarrow \frac{I_1}{I_2} = \frac{R_2}{R_1}$$

3) $P = VI$, but $V = IR$ for resistor
 $\Rightarrow P = I^2 R$

4) $P = VI$, but $I = V/R$
 $\Rightarrow P = V^2 / R$

5)

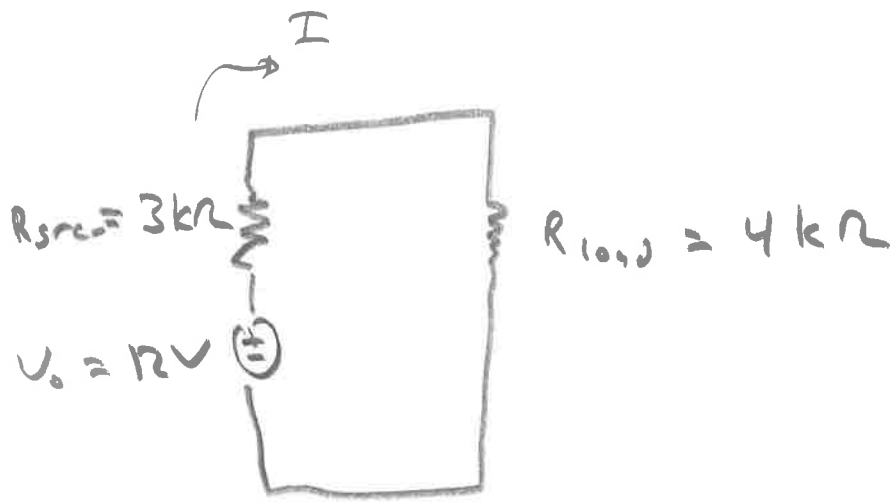

$$I = \frac{V_o}{R_{src} + R_{load}} = \frac{12V}{(3 + 4)k\Omega}$$


$$= \frac{12}{7} \text{ mA} \approx \boxed{1.7 \text{ mA}}$$

$$V = R_{load} \cdot I = 4k\Omega \cdot 1.7 \text{ mA}$$

$$= \boxed{6.8 \text{ V}}$$

These values agree well with the indicated Q point.


6)

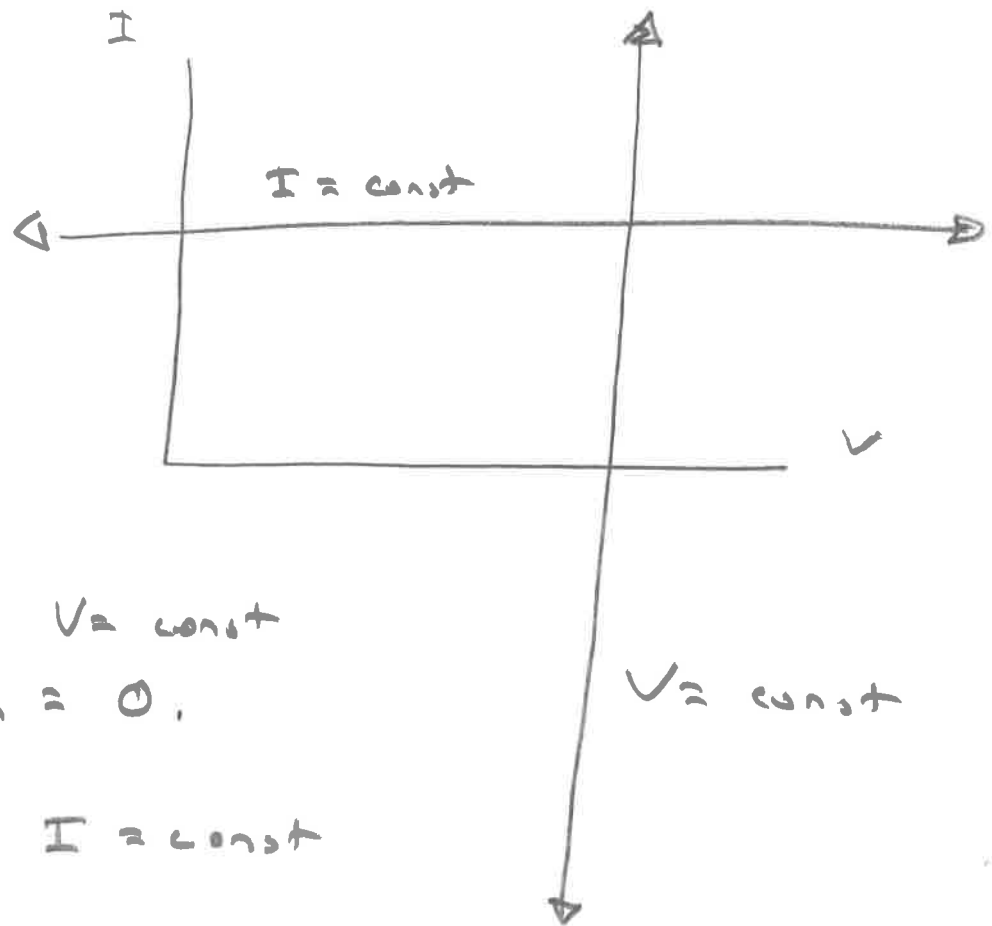

Slope of $V = \text{const}$
is ∞ , $R = 0$.

Slope of $I = \text{const}$
is 0, $R = \infty$.

Current supply:

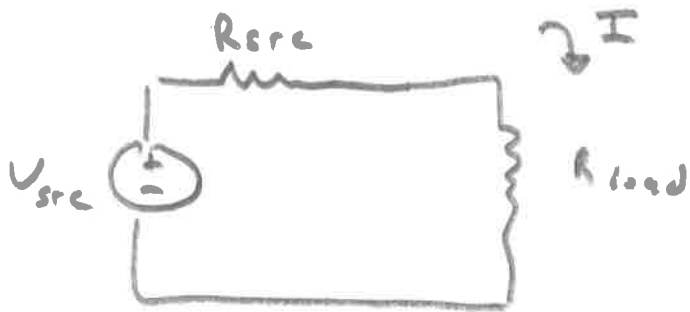


IF $R_{src} \gg R_{load}$,

$$I \approx \frac{V_{src}}{R_{src}}$$

independent of
 R_{load} . I_n

this case $R_{src} \rightarrow \infty$,
as expected by slope.

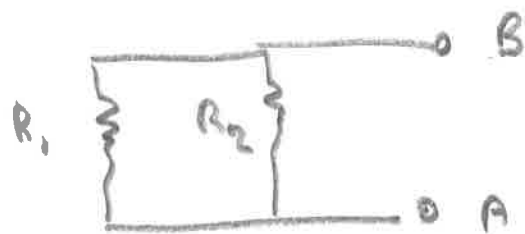
7) To find R_{TH} , set $V_1 = 0$
and find R_{eq} :



$$R_{TH} = R_{eq} = R_1 // R_2 =$$

$$\boxed{\frac{R_1 R_2}{R_1 + R_2} = R_{TH}}$$

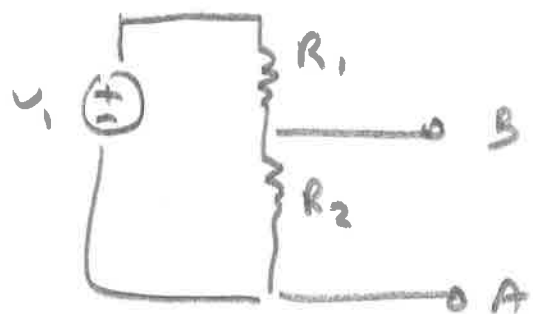The T.E. voltage is simply the
output of the voltage divider:



$$\boxed{V_{TH} = \frac{R_2}{R_1 + R_2} V_1}$$

The short-circuit current is


$$I_{sc} = \frac{V_{TH}}{R_{TH}} = \frac{\frac{R_2}{R_1 + R_2} V_1}{\frac{R_1 R_2}{R_1 + R_2}}$$

$$\boxed{I_{sc} = \frac{V_1}{R_1}}$$

Makes sense:



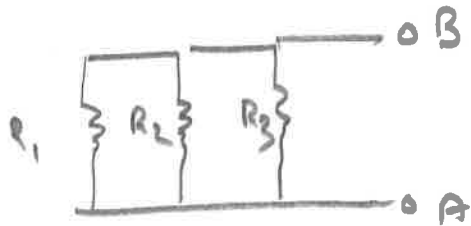8) Calculate R_{Th} by setting
 $V_1 = V_2 = V_3 = 0$ and finding
 equivalent resistance:




$$R_{Th} = R_{eq} = R_1 // R_2 // R_3$$

$$R_{Th} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

For V_{Th} , use superposition principle
 and calculate partial solutions:

Set $V_2 = V_3 = 0$
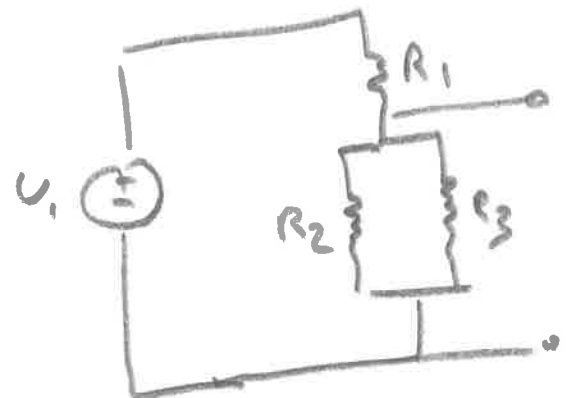
$$V_{Th}^{(1)} = \frac{R_2 // R_3}{R_1 + R_2 // R_3} V_1$$



Similarly:

$$V_{Th}^{(2)} = \frac{R_1 // R_3}{R_2 + R_1 // R_3} U_2$$


$$V_{Th}^{(3)} = \frac{R_2 // R_3}{R_3 + R_1 // R_2} U_3$$

$$V_{Th} = V_{Th}^{(1)} + V_{Th}^{(2)} + V_{Th}^{(3)}$$

$$= \frac{R_2 // R_3}{R_1 + R_2 // R_3} U_1 + \frac{R_1 // R_3}{R_2 + R_1 // R_3} U_2 + \frac{R_1 // R_2}{R_3 + R_1 // R_2} U_3$$

$$V_{Th} = \frac{R_2 R_3 U_1 + R_1 R_3 U_2 + R_1 R_2 U_3}{R_2 R_3 + R_1 R_3 + R_1 R_2}$$

9)

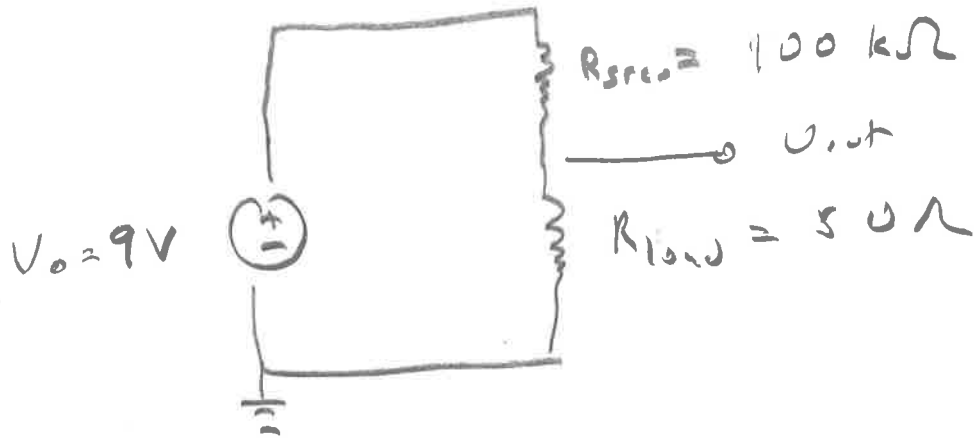

$$U_{out} = \frac{R_{load}}{R_{src} + R_{load}} V_o$$

$$= \frac{50 \Omega}{100 k\Omega + 50 \Omega} 9V$$

$$\sim 0.5 mV \ll 1V$$