

# Lab 7: Combinatorics

Physics 116B

January 5, 2022

## Introduction

In this lab, you will construct a 2-bit decoder and a 2-bit adder circuit using discrete logic gates. The parts you will need and their pin-outs are shown in the Appendix.

## 2-bit Decoder

Using AND gates and inverters, construct the two-bit digital decoder shown in Figure 1; that is, a device for which the numerical binary input  $i = (A_1 A_0)_2$  will cause output  $Q_i$ , and only that output, to be TRUE (e.g.  $A_1 = 1, A_0 = 0 \rightarrow Q_2 = 1$ ). Use as few devices as possible.

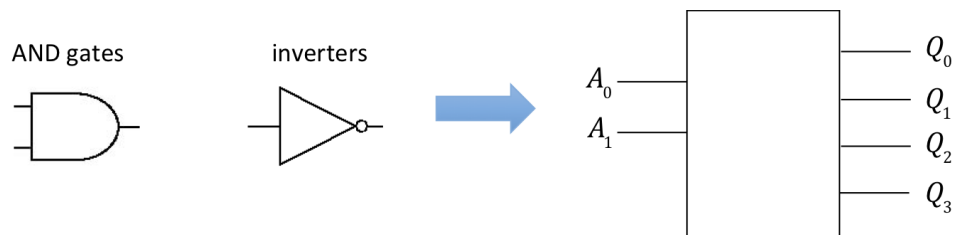


Figure 1: Two-bit decoder

Connect the inputs to the logic switches on the proto-boards and the outputs to the LED indicators.

Verify that the outputs behave as expected for all combinations of the input bits and fill out a truth table with the state of the four outputs for all possible states of  $A_0$  and  $A_1$ .

## 2-bit Adder with Carry Out

Wire up the following 2-bit adder circuit shown in Figure 2. Connect the inputs to the logic switches on the proto-board and the outputs to the LED indicators.

Fill out a truth table for all 16 combinations of the input switches, and verify that the circuit behaves as expected.

Disconnect the  $A_0$  bit from the switch and connect it to the TTL function generator. Set bit  $A_1$  to 0 and  $B_0$  and  $B_1$  to 1. Measure the propagation delay from  $A_0$  changing state (both high and low) to  $Q_0$ ,  $Q_1$ , and  $CO$

