

Microprocessors

and

Assembly

Little Man Computer



Input → user input

Output → e.g. to screen

Acc → accumulator (for addition + subtraction)

Program Counter → starts at zero, increments prior to each instruction, but may be overwritten by the instruction, (Next instruction taken from address in PC)

Mail boxes: Stores data and program.

LMC Instruction Set

1XX	ADD	Add value in mailbox XX to accumulator
2XX	SUB	Subtract value "
3XX	STA	Store contents of Acc into mailbox XX.
5XX	LOA	Load contents of XX into the accumulator
6XX	BRA	Set PC to mailbox XX
7XX	BRZ	Set PC mailbox XX if Acc is zero
8XX	BRP	Set PC mailbox XX if Acc is zero or positive
901	INP	load input to Acc
902	OUT	Send Acc to Out
000	COB	Coffee Break

Example : Adder $(A+B)$

901	INP
350	STA FIRST
901	INP
150	ADD FIRST
902	OUT
000	COB
	FIRST DAT

Example Subtractor $(A-B)$

901	INP
350	STA FIRST
901	INP
351	STA SECOND
550	LDA FIRST
251	SUB SECOND
902	OUT
000	COB

Example Multiplier

00	901	INP	input "a"
01	350	STA A	store "a"
02	901	INP	input "a"
03	351	STA B	store "b"
04	711	LOOP ORZ DONE	
05	552	LOA SUM	
06	150	ADD A	
07	352	STA SUM	
08	551	LOA B	
09	253	SUB ONE	
10	604	BRA LOOP	
11	552	DONE LOA SUM	
12	902	OUT	
13	000	COB	
---	---		
50	---	A DAT	
51	---	B DAT	
52	0	SUM DAT	0
53	1	ONE DAT	1

* HW LMZ to integer divide A/B

6	3	→	2
5	3	→	1
7	3	→	2

Computer

A > B

AND



AB

A	B	O
0	0	0
0	1	0
1	0	0
1	1	1


NAND



\overline{AB}

0	0	1
0	1	1
1	0	1
1	1	0

OR

 

$A + B$


0	0	0
0	1	1
1	0	1
1	1	1

NOR




0	0	1
0	1	0
1	0	0
1	1	0

XOR

 

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

XNOR

 



0	0	1
0	1	0
1	0	0
1	1	0 1

For the minimalists...


NAND and NOR are each functionally complete... you can construct all logic from enough of either,

Man tricks, invert:


Ignore!

  

AND:

 


OR:

 


Half Adder

0	1	1	1
0	0	1	1
0	0	0	1
00	0	10	11

 


Full Adder

 

"Trick" to understanding is that
 $1 + 1 + (1) = 11 = 3$ is biggest number possible
 $(\Leftrightarrow 2 = 1 \Rightarrow x = 0)$

Buffer

 

A	O
0	0
1	1

Inverter



A	O
1	0
0	1

Buffer from Inverter



Inverter from Buffer



Tri-State Buffer




A	C	O
0	0	Z
1	0	Z
0	1	0
1	1	1

Multiplexing




1-bit Mux

 

A	Q
0	I_0
1	I_1

1-bit Demux

 

A	O_0	O_1
0	I	0
1	0	I

MUX, DEMUX, Tri-State Buffer

MUX


A	B	S	O
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

DEMUX

A	S	C	D
0	0	0	0
1	0	1	0
0	1	0	0
1	1	0	1


S	O
0	A
1	B

S	C	D
0	in	0
1	0	in

 

S	O
0	Z
1	in



De coder

 


3-bit;




A_0	A_1	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

  

2^n inputs

 

A	O
0	I_0
1	I_1
2	I_2
...	...
(2^n-1)	$I_{(2^n-1)}$

 

A	O_0	O_1	O_2, \dots	O_{2^n-1}
0	H	O	O	O
1	O	H	O	O
2	O	O	H	O
...
2^n-1	O	O	O	H

Multiplexer

Number of inputs: N_i


Number of outputs: $N_o \geq 1$

Number of address bits: N_A

$$2^{N_A} = N_i / N_o$$



eg.

4:1

 


$$2^2 = 4/1$$

4:2

  

$$2^1 = 4/2$$

Mux \leftrightarrow Generic Logic

 

a	b	Q
0	0	A
0	1	B
1	0	C
1	1	D

Configurable Logic!


Set to
which we
want

Width:


Often, we might want to associate m -bits with a particular address,

(Accumulator in LMC requires 10 bits ≤ 1024)
and Mailboxes

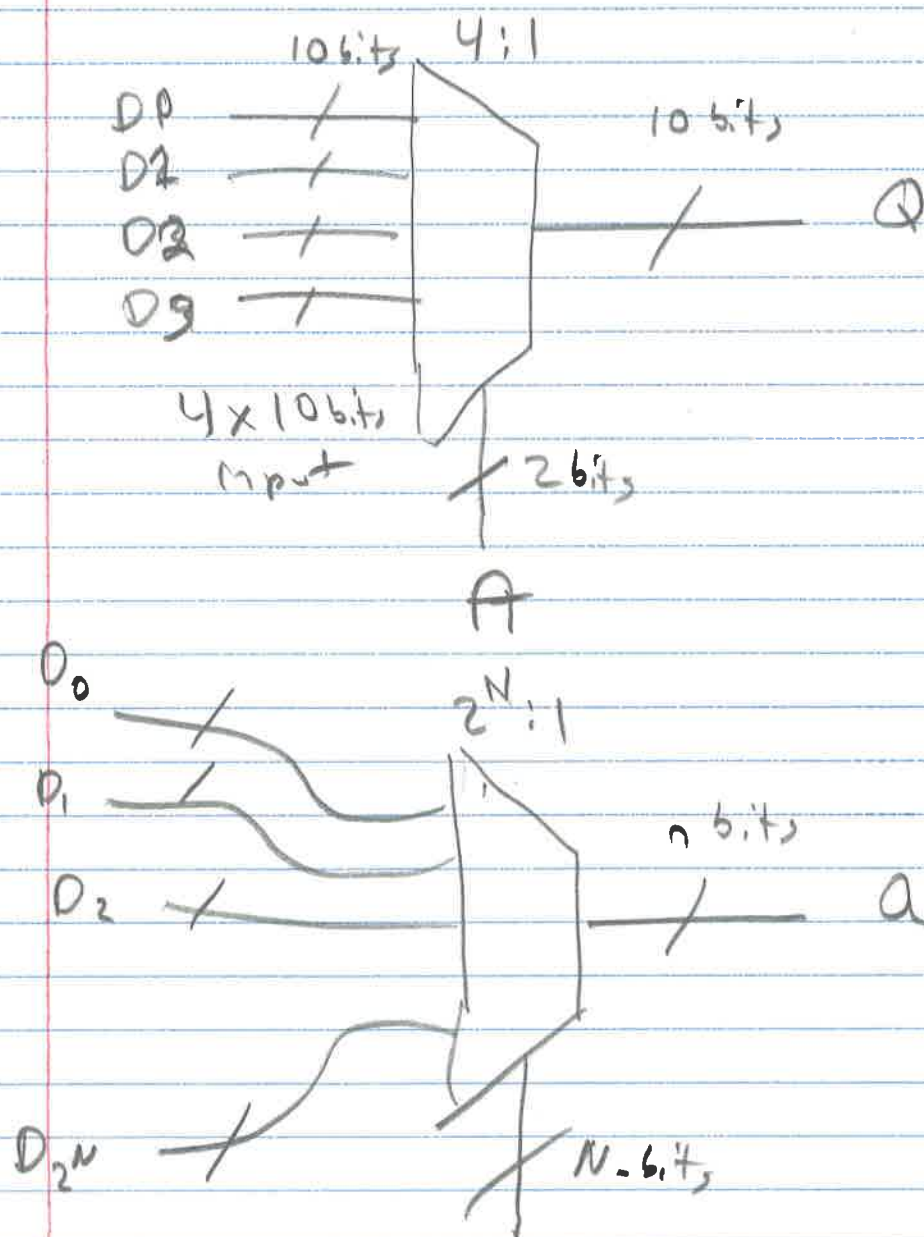→ 10 bits at address 0x3
10 bits at address 0x2



RS latch

 


RS both high $Q = 0$ $\bar{Q} = 1$ stable
 $Q = 1$ $\bar{Q} = 0$ stable
 ($Q = \bar{Q}$ not stable)

$R = 1$ $S = 0$, $S = 0$ forces $\bar{Q} = 1$ (not)
 $\bar{Q} = 1$ and $R = 1$ forces $Q = 0$

$R = 0$ $S = 1$ $R = 0$ forces $Q = 1$
 $Q = 1$ and $S = 1$ forces $\bar{Q} = 0$

RS both 0 \rightarrow $Q = \bar{Q} = 0$ invalid state

D-type Flip-Flop

 


$$E = 0 \Rightarrow R = S = 1 \Rightarrow Q \text{ constant}$$

$$E = 1 \Rightarrow R = \bar{D} \quad S = D \Rightarrow Q = D \quad \bar{Q} = \bar{D}$$


Note: $R = S = 0$ is not possible
due to NOT at (*)

(Btw: that $0 = \neg 0$ for NAND
construction... 5 NANDs per D ff)

Symbol

 


Memory


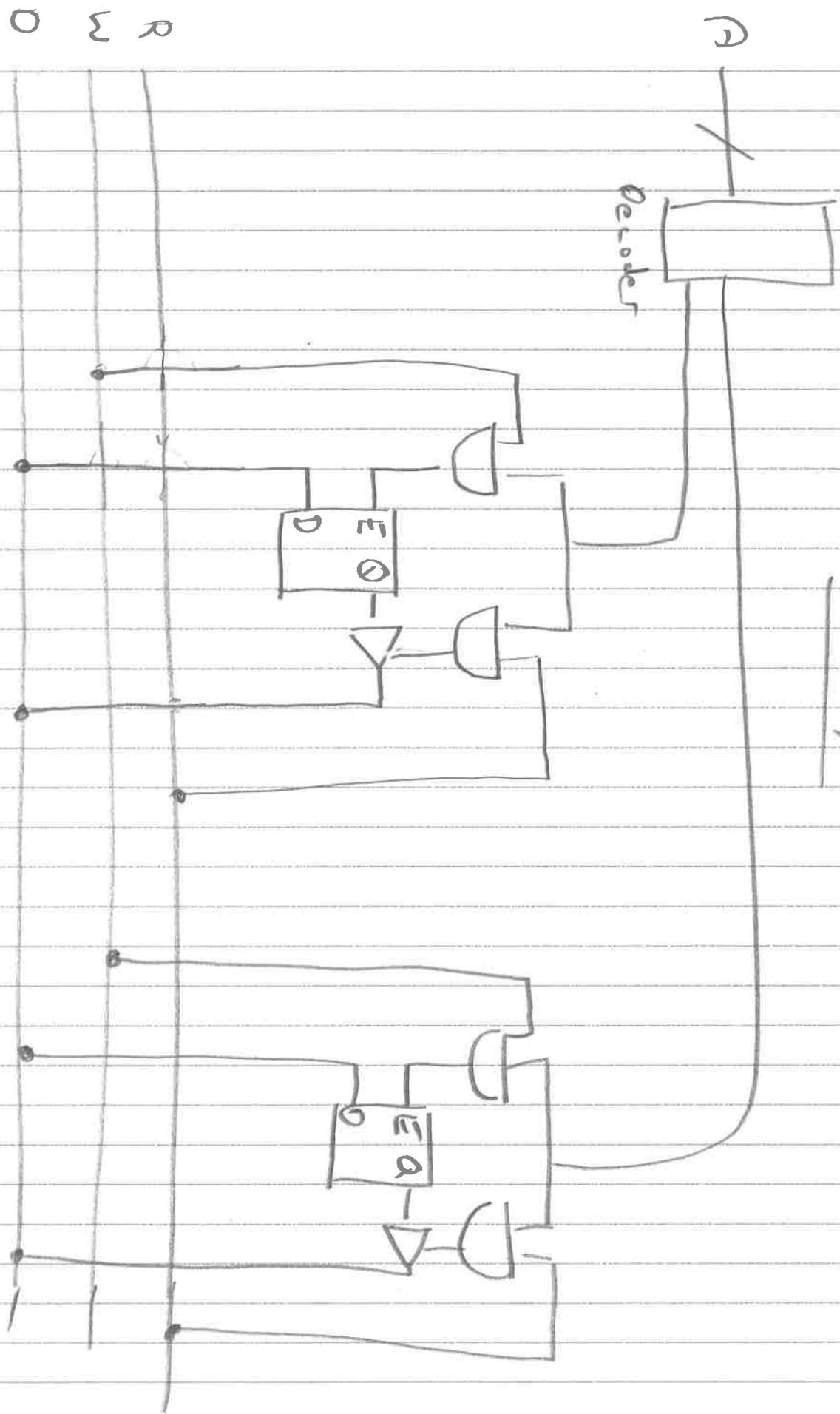


Any 0-ff can be set with W, or feed

Memory Symbol

 



Synchronous Accumulator

  

As long as we feed B $\frac{1}{2}$ cycle ahead, accumulator handles one new input per cycle.

Register

 

 



1-bit asynchronous, NAND computer

X X X
 604 514 424

1) 2)

66	0	1	0	0
65	1	0	1	0
64	0	0	0	1
63	0	0	1	0
62	0	1	0	0
61	1	0	0	1
60	X	X	X	1



Edge - Triggered D - Flip Flop

  


* Won't see new value until after falling edge, i.e.,

Next Clock Cycle

Symbols

  

CPU: Central Processing Unit

 

By now understood workings of
ALU for each assembly command
w a fixed set of steps:

- moving data into registers
- digital synchronous logic

all driven by control signals (C_i)

Fixed Program Computer

Early computers applied a fixed set of steps to variable input data

C_1 0 0 1
 C_2 0 1 0
:
 C_N 0 0 1

} Known
by
Designer

R_1 ? ? ?
 R_2 ? ? ?
 R_3 ? ? ?

} Computed
at run
time.

First computers had a hard-wired CU, no easy way to change it.

Turing / Von Neumann / Euse

developed idea to

Store Instructions in Memory,

Incredibly powerful:

→ General Purpose Computer

* ~~New Algorithms Possible
based on recursion & goto
and branching (conditional)~~ *

Control Unit


- fetch instruction word from memory at current address in program counter (IR)
- increment program counter (PC++)
- IR contains both OP code and address.
- For each operation, there are a fixed set of steps that take place.

CLK 

Counter	1	2	3	4	5	6	0	1	2	3	4	5
OP code	0	0	0	0	0	0	3	3	3	3	3	3
C1	1	1	0	0	1	1	1	1	0	0	1	0
C2	0	0	1	1	0	0	1	1	0	1	1	1
C3	1	0	1	0	1	1	1	1	0	1	1	1
C4	1	1	1	0	1	1	1	1	0	0	1	1

Key point: the control operations can, eg. change program counter, providing flow control, and conditional execution.

CU m ROM

 

That's really it....

except for literally Trillions
of \$ invested to improve
performance!

Microsoft	—	\$500 B
Apple	—	\$700 B
Google	—	\$534 B
Amazon	—	\$373 B