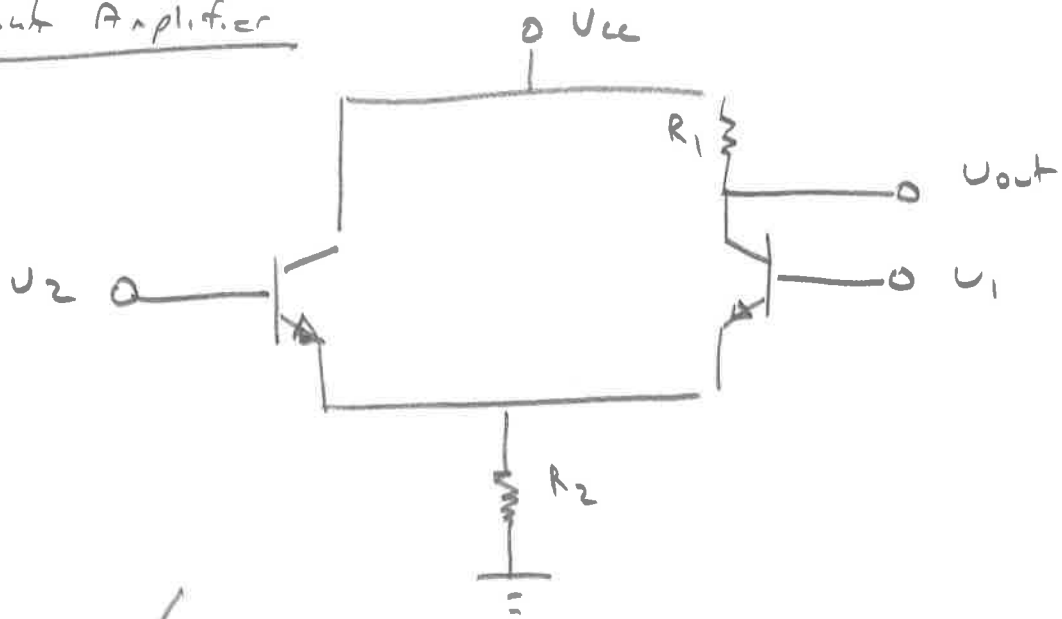


Feed back !


and

Op Amps

# Differential Amplifier



AC  
model

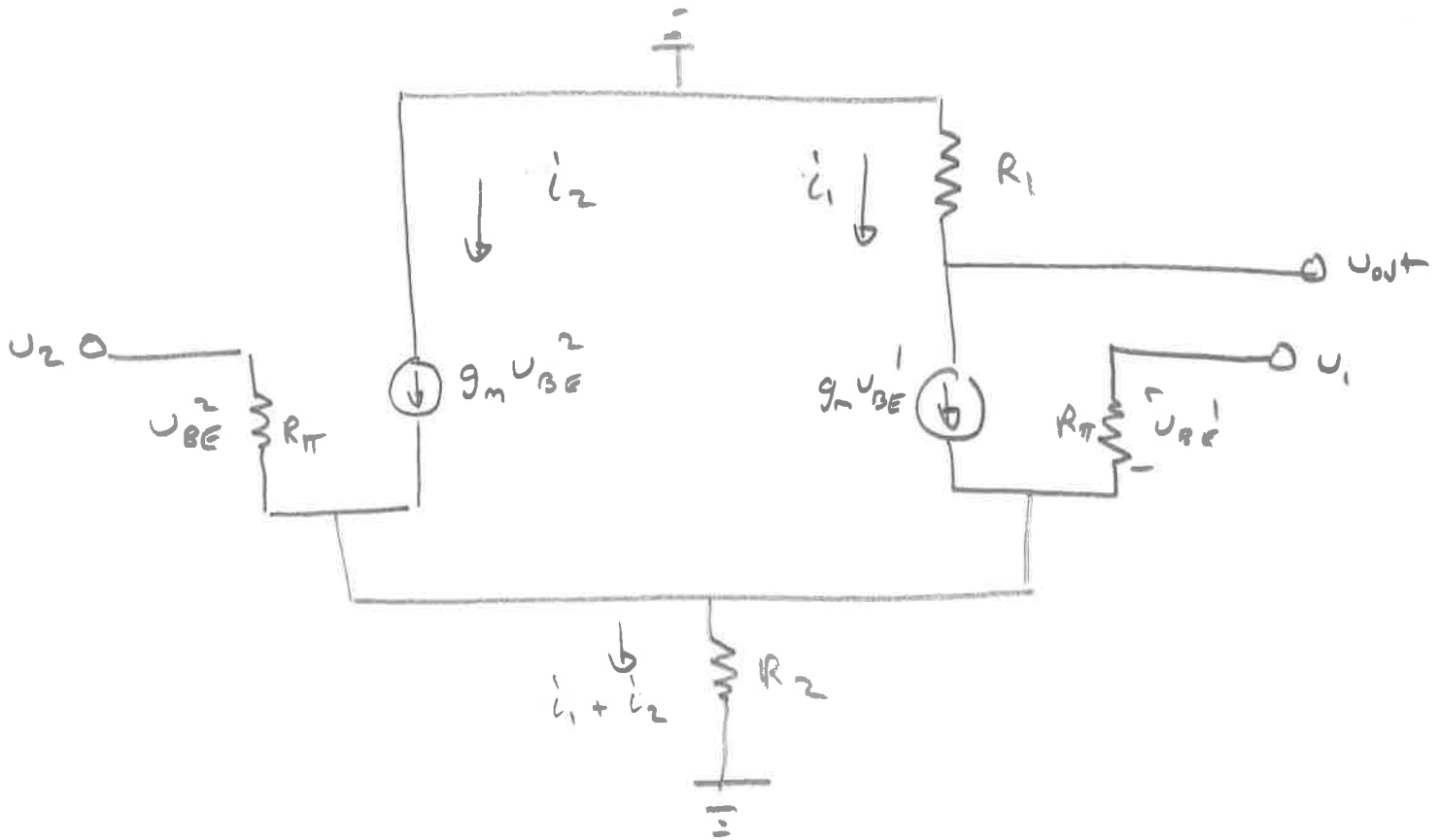

Case:  $U_1 = U_2 = U_0 \Rightarrow i_1 = i_2$

$$U_{BE}^1 = U_{BE}^2 = U_0 - R_2 (i_1 + i_2)$$

$$U_{BE}^1 = U_0 - 2R_2 (g_m U_{BE}^1)$$

$$(1 + g_m 2R_2) U_{BE}^1 = U_0$$

$$U_{BE}^1 = \frac{U_0}{1 + g_m 2R_2}$$

$$U_{out} = -i_1 R_1 = -g_m U_{BE}^1 R_1$$

$$= \frac{-g_m R_1}{1 + g_m 2R_2} U_0$$

$$= -\left(\frac{R_1}{r_E + 2R_2}\right) U_0 = -\left(\frac{R_1}{r_E + 2R_2}\right) \left(\frac{U_1 + U_2}{2}\right)$$

Case:  $V_1 = -V_2 = V_0$

$$i_2 = -i_1 \Rightarrow \text{current in } R_2 \text{ is zero}$$

$$\Rightarrow V_E = 0$$

$$V_{BE} = V_1$$

$$i_1 = g_m V_1$$

$$V_{out} = -i_1 R_1 = -g_m R_1 i_1$$

$$V_{out} = \frac{R_1}{r_E} \left( \frac{V_2 - V_1}{2} \right)$$



Generally:

$$V_{out} = \left( \frac{R_1}{r_E + 2R_2} \right) \frac{(V_1 + V_2)}{2} + \left( \frac{R_1}{r_E} \right) \frac{(V_2 - V_1)}{2}$$

↑  
Common  
Mode  
Rejection

↑  
Differential  
Gain

# The Follower and Feedback

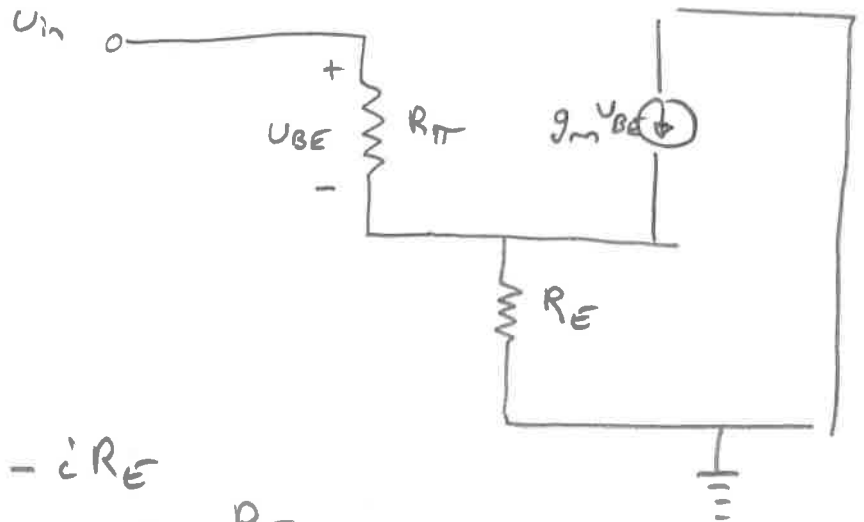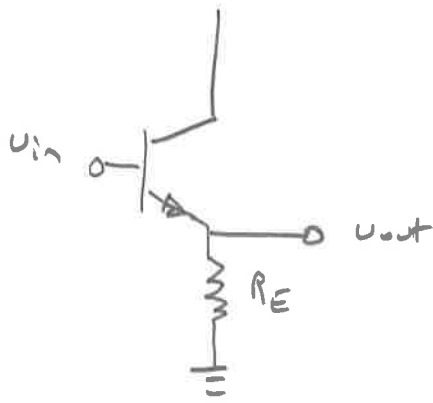

$$\textcircled{1} \quad U_{BE} = U_B - U_E = U_{in} - i R_E \\ = U_{in} - g_m U_{BE} R_E$$

$$(1 + g_m R_E) U_{BE} = U_{in}$$

$$U_{BE} = \frac{U_{in}}{1 + g_m R_E}$$

$$U_{out} = i R_E = g_m U_{BE} R_E = \frac{g_m R_E}{1 + g_m R_E} U_{in}$$

$$U_{out} = \frac{A}{A+1} U_{in}$$

$$A = g_m R_E \gg 1$$

$$U_{out} \rightarrow U_{in} \quad \text{as } A \rightarrow \infty$$

$$\textcircled{2} \quad U_{BE} = U_B - U_E \Rightarrow U_{BE} = U_{in} - U_{out}$$

$\uparrow$  gain device input       $\uparrow$  input       $\uparrow$  negative feedback

$$U_{BE} \rightarrow 0$$



or,

$$U_{BE} = U_{in} - U_{out} = U_{in} - \frac{A}{A+1} U_{in}$$

$$U_{BE} = \frac{U_{in}}{1+A}$$

Negative feedback drives  $U_{BE}$  very close to zero, just near enough that large factor  $A$  puts  $U_{out} \sim U_{in}$

# Common Emitter Amplifier and Feedback

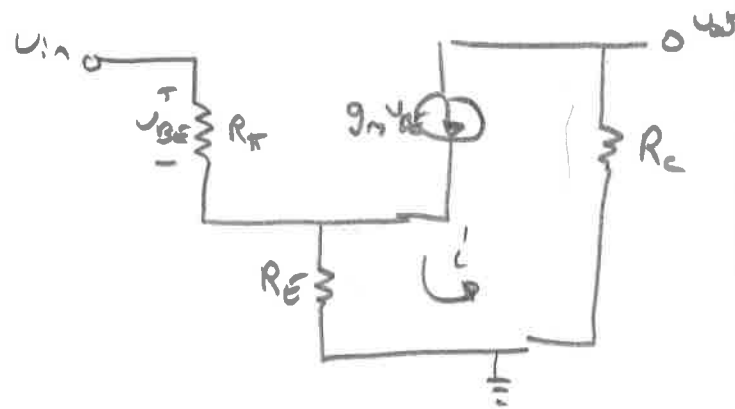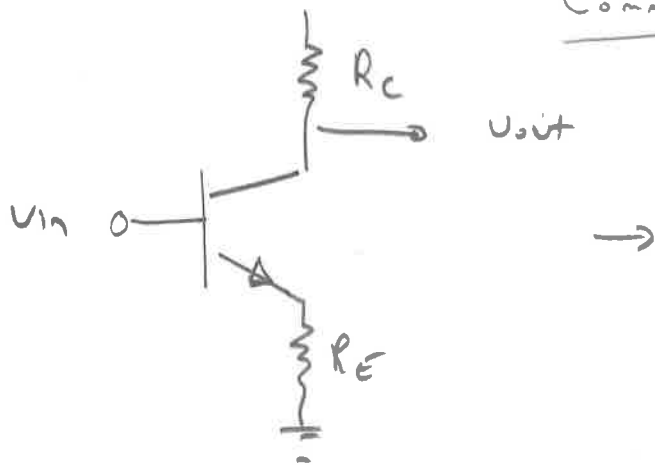

$$\textcircled{1} \quad V_{BE} = V_B - V_E = V_{in} - i R_E$$

$$= V_{in} - g_m V_{BE} R_E$$

$$(1 + g_m R_E) V_{BE} = V_{in}$$

$$V_{BE} = \frac{V_{in}}{1 + g_m R_E}$$

$$V_{out} = -R_C i = -R_C g_m V_{BE}$$

$$= - \frac{g_m R_C}{1 + g_m R_E} V_{in}$$

$$= \left( - \frac{R_C}{R_E} \right) \frac{g_m R_E}{1 + g_m R_E} V_{in} = \left( - \frac{R_C}{R_E} \right) \frac{A}{1 + A} V_{in}$$

$$V_{out} \rightarrow - \frac{R_C}{R_E} V_{in}$$

$$\textcircled{2} \quad V_{BE} = V_B - V_E \Rightarrow V_{BE} = V_{in} - i R_E$$

$$= V_{in} - \left( - \frac{V_{out}}{R_C} \right) R_E$$


$$V_{BE} = V_{in} - \left( - \frac{R_E}{R_C} \right) V_{out}$$

$\uparrow$  gain device input       $\uparrow$  input       $\uparrow$  negative feedback.

$$V_{BE} \rightarrow \frac{V_{in}}{A + 1}$$

$$V_{out} \rightarrow \left( - \frac{R_C}{R_E} \right) \frac{A}{A + 1} V_{in}$$

# Op - Amp

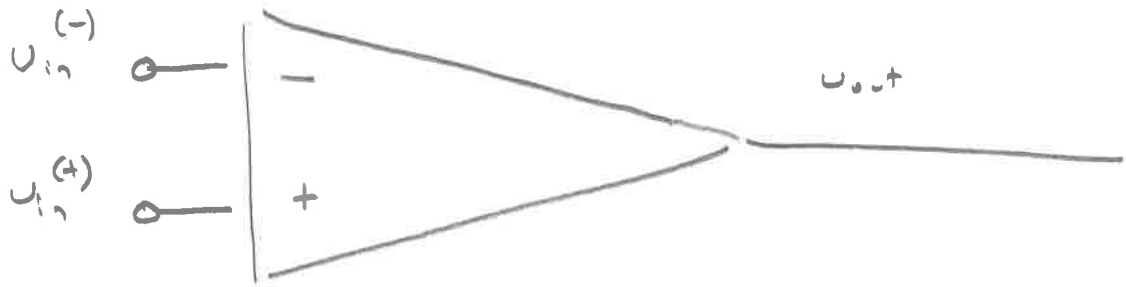

$$U_{out} = A (U_{in}^{(+)} - U_{in}^{(-)})$$


$$A \rightarrow \infty$$

~ Infinite input impedance

With  $A \rightarrow \infty$ , nearly useless device

until tuned by negative feedback ....

## Follower

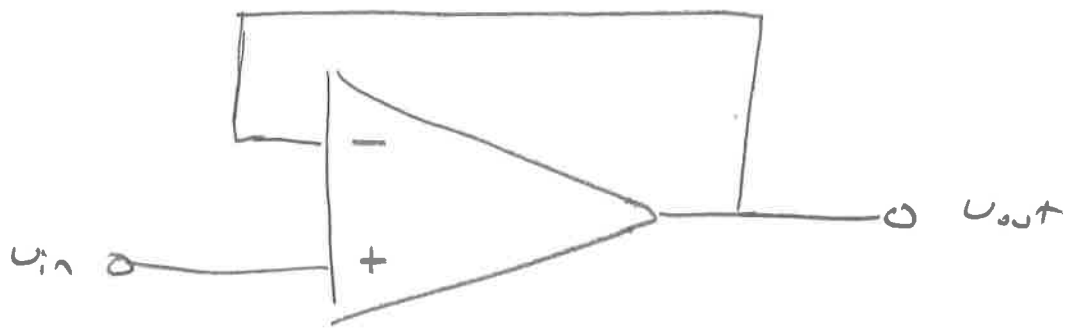

$$\begin{aligned} U_{out} &= A (U_{in}^{(+)} - U_{in}^{(-)}) \\ &= A (U_{in} - U_{out}) \end{aligned}$$

$$(A+1) U_{out} = A U_{in}$$

$$U_{out} = \frac{A}{A+1} U_{in}$$


$$U_{out} \rightarrow U_{in} \quad \text{when} \quad A \rightarrow \infty$$

Notice:

$$\begin{aligned} U_{in}^{+} - U_{in}^{-} &= U_{in} - \left( \frac{A}{A+1} \right) U_{in} \\ &= \frac{U_{in}}{A+1} \rightarrow 0, \dots \end{aligned}$$



## Non-inverting Amplifier

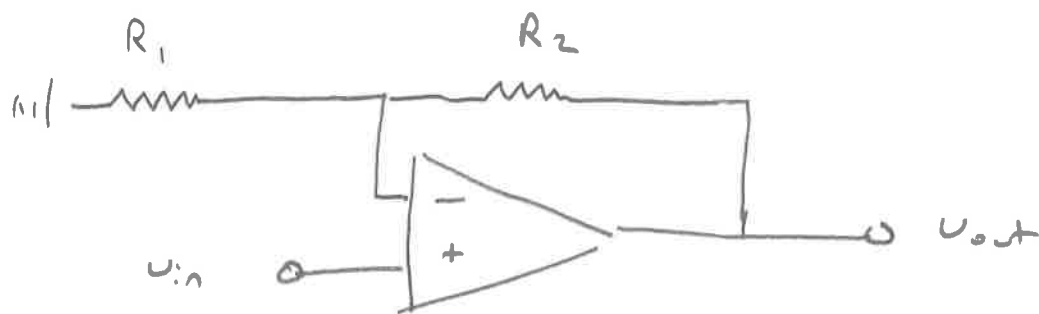

$$U_{out} = A (U_{in}^{(+)} - U_{in}^{(-)})$$

$$= A \left( U_{in} - \frac{R_1}{R_1 + R_2} U_{out} \right)$$

$$U_{out} = \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{A}{A + 1 + \frac{R_2}{R_1}} \right) U_{in}$$

$$U_{out} \rightarrow \left( 1 + \frac{R_2}{R_1} \right) U_{in}$$

Notice:

$$U_{in}^{(+)} - U_{in}^{(-)} = U_{in} - \frac{R_1}{R_1 + R_2} U_{out}$$


$$= \left( 1 - \frac{A}{A + 1 + R_2/R_1} \right) U_{in}$$

$$\rightarrow 0$$

as


$$A \rightarrow \infty$$

# Op - Amp      Rules

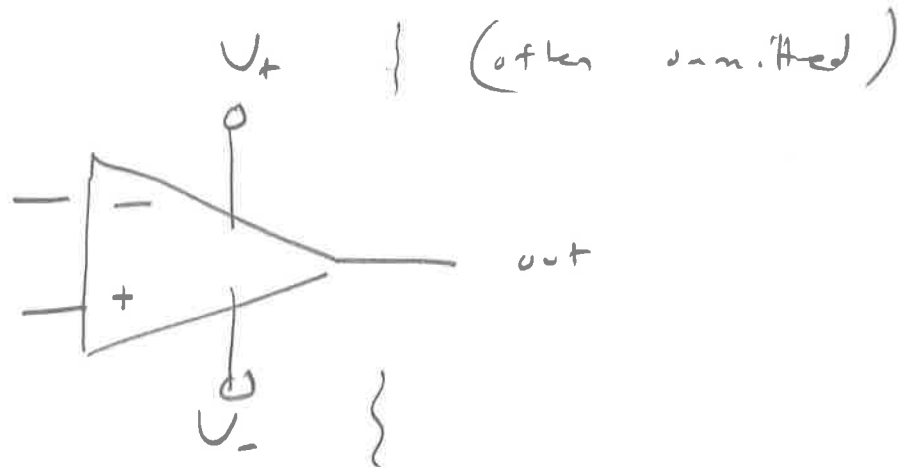

When negative feedback is present:

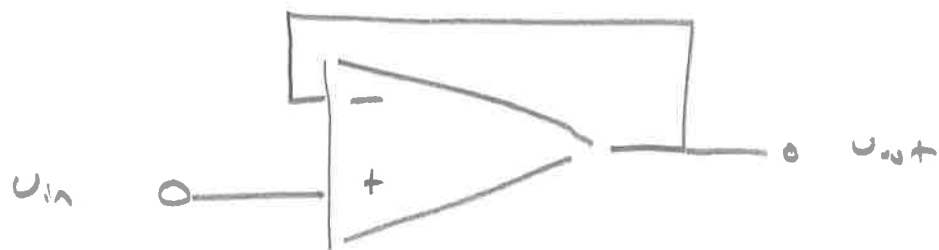
- ① output does whatever possible  
to put  $V_{in}^{(-)} = V_{in}^{(+)}$ ,
- ② input terminals are  $\sim$  infinite  
impedance  $\Rightarrow$  no current into  
terminals.



$$U_{in}^{(+)} = U_{in}^{(-)}$$

$$U_{in} = U_{out}$$

$$R_{in} = \infty$$

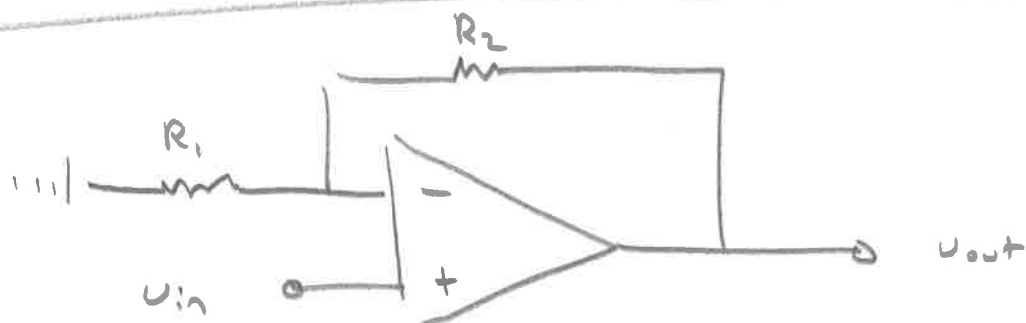


$$U_{in}^{(+)} = U_{in}^{(-)}$$

$$U_{in} = \frac{R_1}{R_1 + R_2} U_{out}$$

$$U_{out} = \left( 1 + \frac{R_2}{R_1} \right) U_{in}$$

$$R_{in} = \infty$$

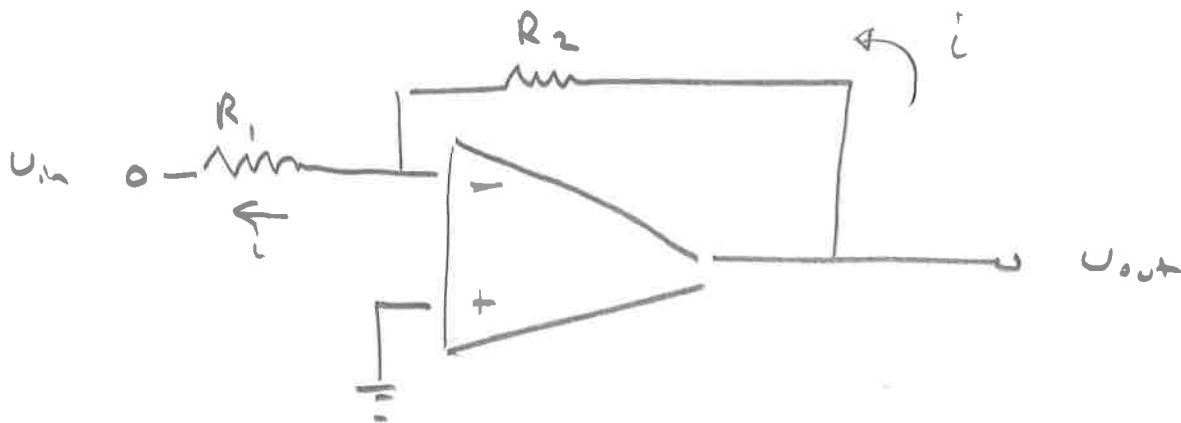

Since  $U_{in}^{(-)} = U_{in}^{(+)} = 0$ , we say

$U_{in}^{(-)}$  is a virtual ground.


$$i = -\frac{U_{in}}{R_1} = \frac{U_{out}}{R_2} \Rightarrow$$

$$U_{out} = \left(-\frac{R_2}{R_1}\right) U_{in}$$

$$R_{in} = R_1 !!!$$

Why ever do this?

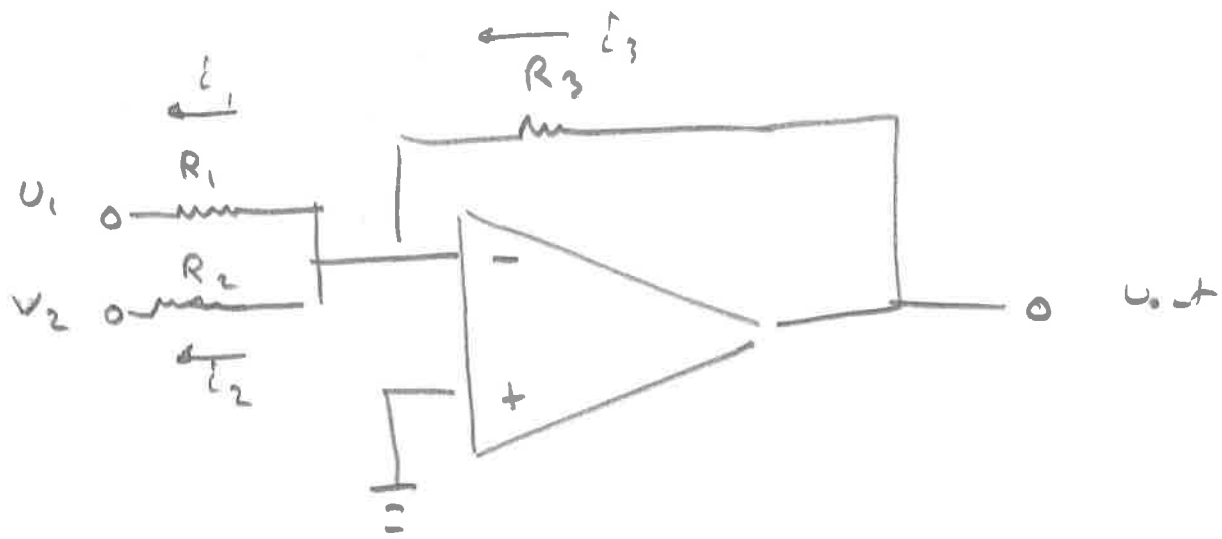- ① Current sources like low  $R_{in}$  and hate high  $R_{in}$ . High quality amps use current sources...
- ②  $G < 1$  possible.
- ③ See next...




$$i_3 = i_1 + i_2$$

$$\frac{U_{out}}{R_3} = \left( -\frac{U_1}{R_1} \right) + \left( -\frac{U_2}{R_2} \right)$$

$$U_{out} = \left( -\frac{R_3}{R_1} \right) U_1 + \left( -\frac{R_3}{R_2} \right) U_2$$


Addition (Mixer)

## Problematic Circuits

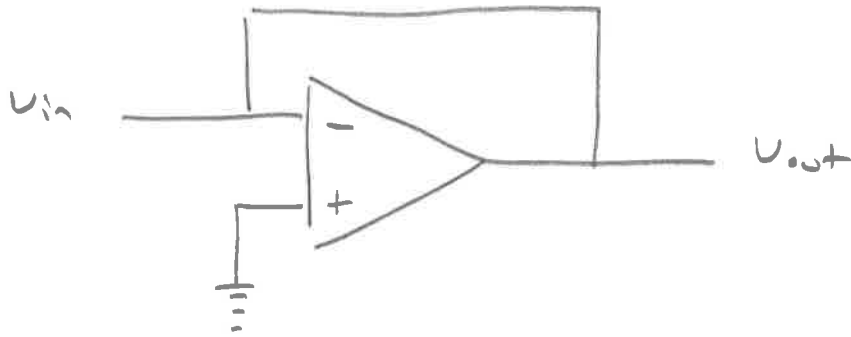

$V_{in} = V_{out}$ , but both are shorted  
to ground.

## Problematic Circuits

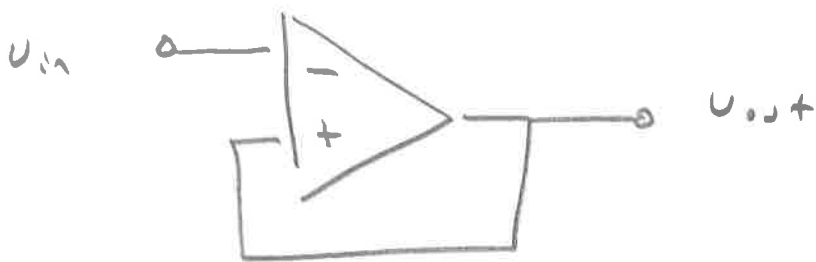

Blindly following rules predicts  $U_{in} = U_{out}$ ...

Not what happens... rules apply when  
negative feedback is present.


Check by putting  $U_{out}$  initially at  
 $\pm \infty$  (or  $\pm V_{cc}$ ) and see if  
it moves toward zero...

In this case

$$U_{out} = \infty \Rightarrow U_{out} \rightarrow A \cdot \infty$$

$$U_{out} = -\infty \Rightarrow U_{out} \rightarrow A(-\infty)$$


Compare with Follower!

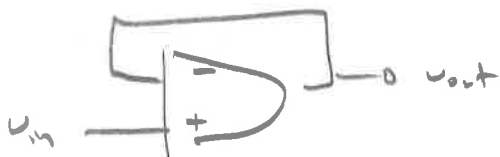

$$U_{out} = +\infty \Rightarrow U_{out} \rightarrow -\infty \quad (U_{out} \downarrow)$$


$$U_{out} = -\infty \Rightarrow U_{out} \rightarrow +\infty \quad (U_{out} \uparrow)$$

## log / "anti log" amplifiers

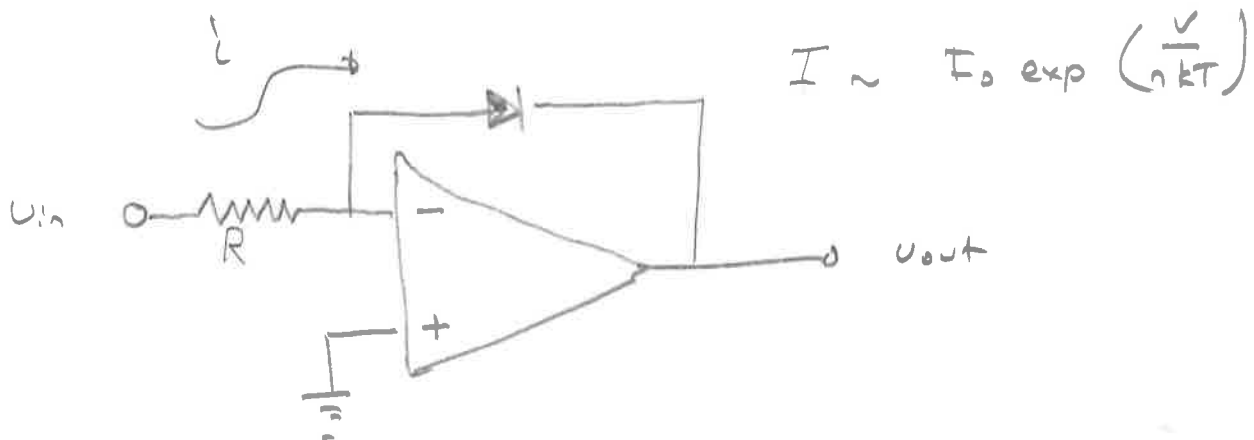

$$i = \frac{U_{in}}{R} = I_0 \exp\left(-\frac{U_{out}}{n k T}\right)$$

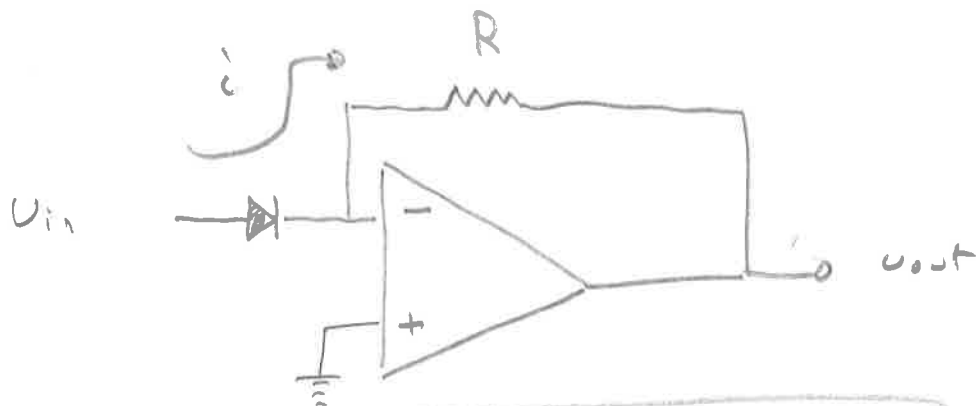
$$U_{out} = -n k T \log\left(\frac{U_{in}}{I_0 R}\right)$$



$$U_{out} = -I_0 R \exp\left(\frac{U_{in}}{n k T}\right)$$




## Multiplicier

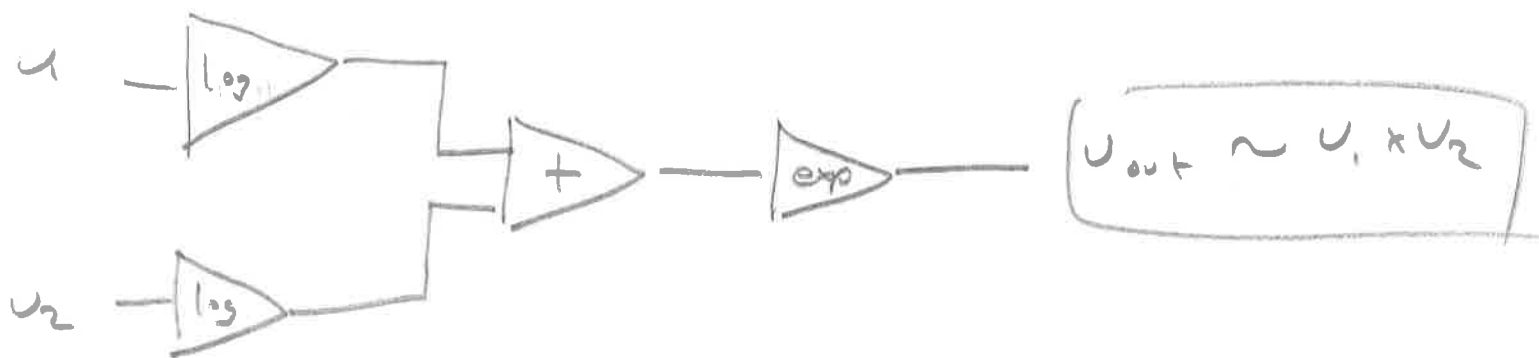


- Programmable Gain
- (AM modulation)

(Harder to make "4-quadrant" multiplier,  
w/ inputs and outputs allowed negative)

## Current Sources

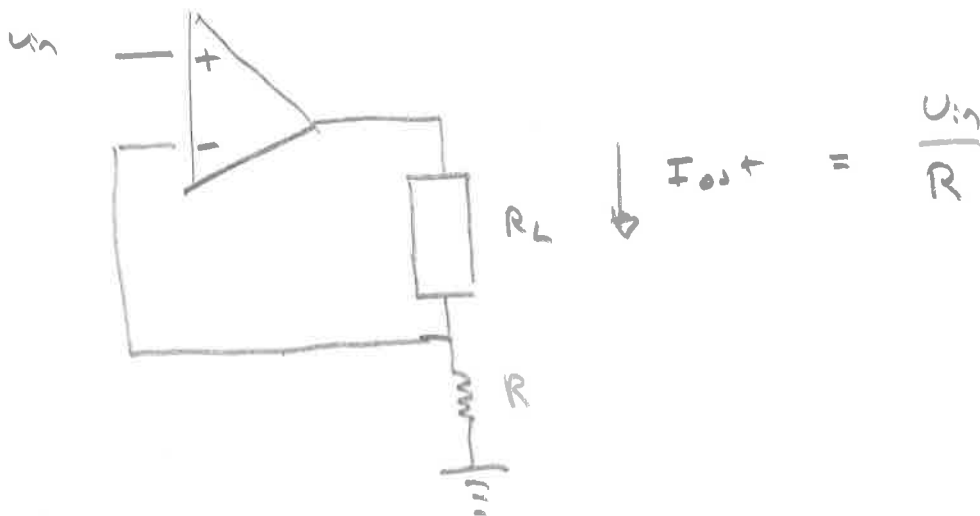

Ground connected;

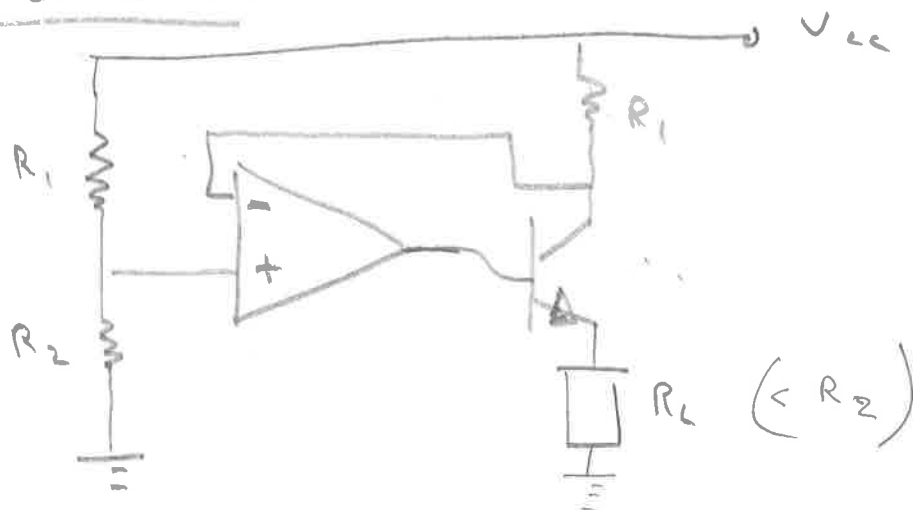

$$I_L = \frac{V_{cc}}{R_1 + R_2}$$