




Transconductance

Model


for

Transistor

Transistor Curves

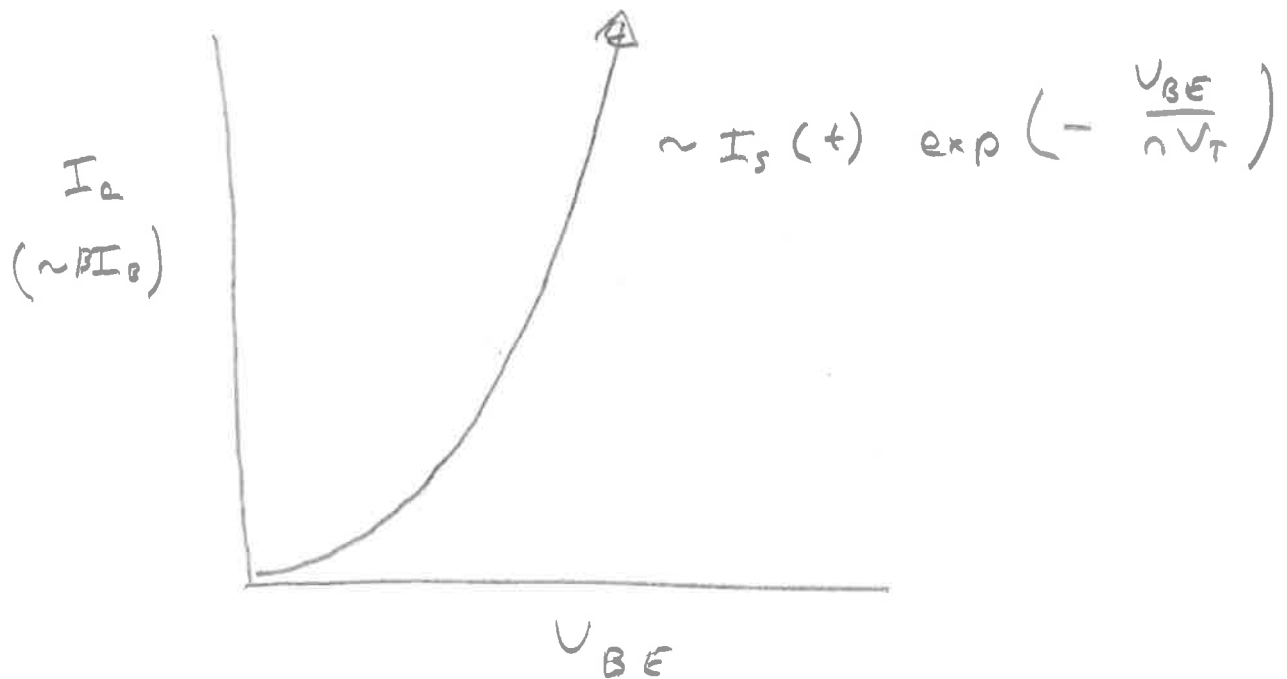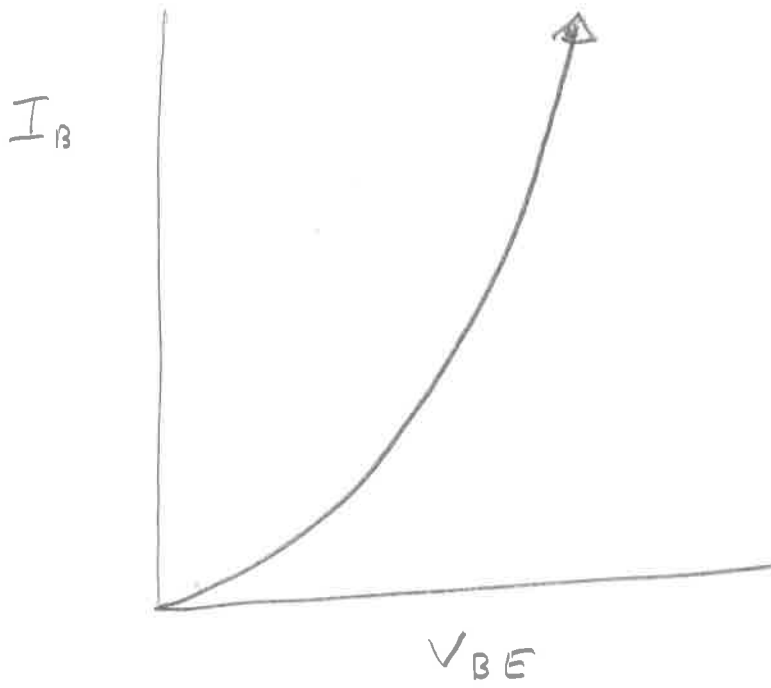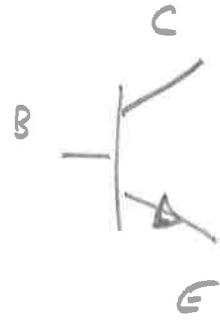

Current Mirror

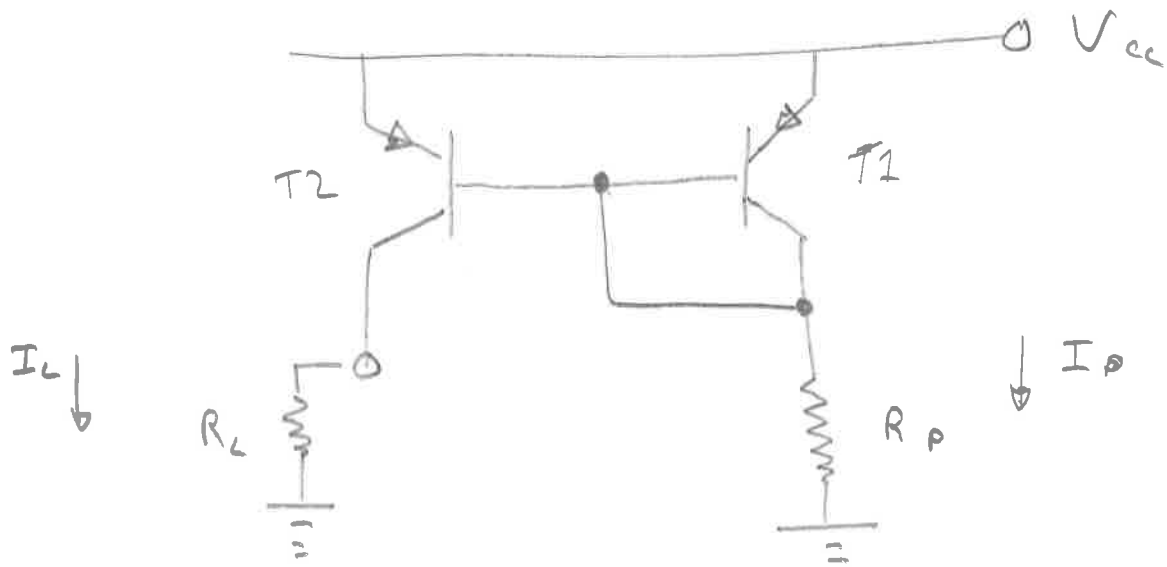

The short-circuit between E and B keeps V_E^1 about one diode drop below V_{cc} .

So, the "programming resistance" R_p causes current

$$I_p = \frac{V_{cc} - V_D}{R_p} \quad \text{to flow.}$$

E-M relates I_c to V_{BE} , and

both T1 and T2 have the same

V_{BE} . As a result, a current


$$I_L \sim I_p \quad (\text{match } T_1 \text{ and } T_2)$$

flows *independent* of R_L ($R_L < R_p$)

A current source.

(Note: large resistance hard for current source
easy for voltage source)

Large-Signal Model

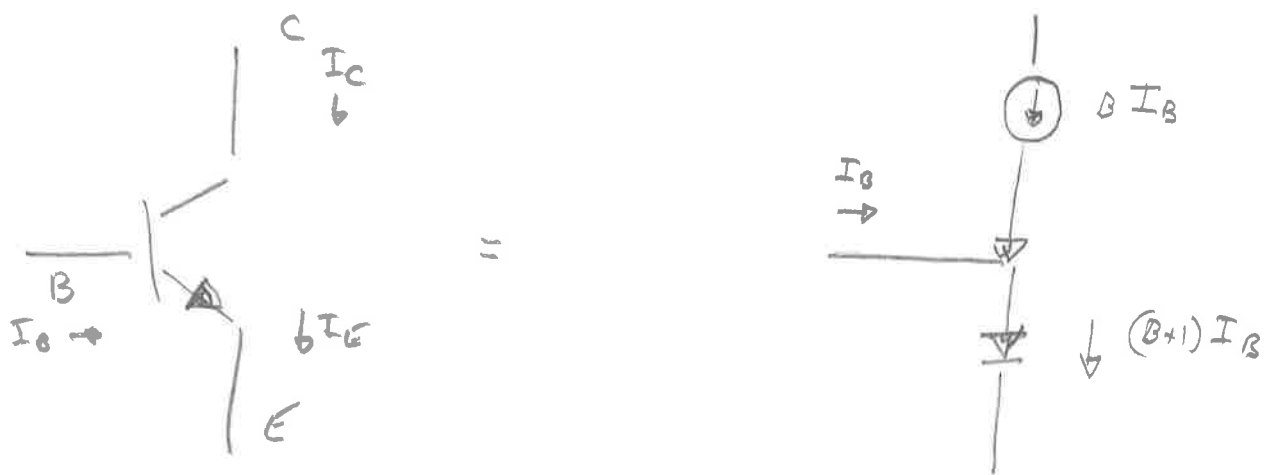

(*) In literature, you'll see $\alpha \approx \frac{I_C}{I_E} = \frac{\beta}{\beta + 1}$

This is known as "Approximate Ebers-Moll" model, and it's sufficient to find DC operating point for circuit in active mode.

The B-E junction is a diode, so

$$I_B = I_0 \left(\exp\left(\frac{V_{BE}}{nV_T}\right) - 1 \right)$$

and the current source (βI_B) results in

$$I_C = \beta I_0 \left(\exp\left(\frac{V_{BE}}{nV_T}\right) - 1 \right)$$

We lump βI_0 into one T-dependent, material dependent factor:


$$I_C = I_S(T) \left(\exp\left(\frac{V_{BE}}{nV_T}\right) - 1 \right)$$

Trans conductance

The Eber's Moll result:

$$I_C = I_S(T) \left(\exp\left(\frac{V_{BE}}{n V_T}\right) - 1 \right)$$

relates I_C to V_{BE} not $I_B \dots$

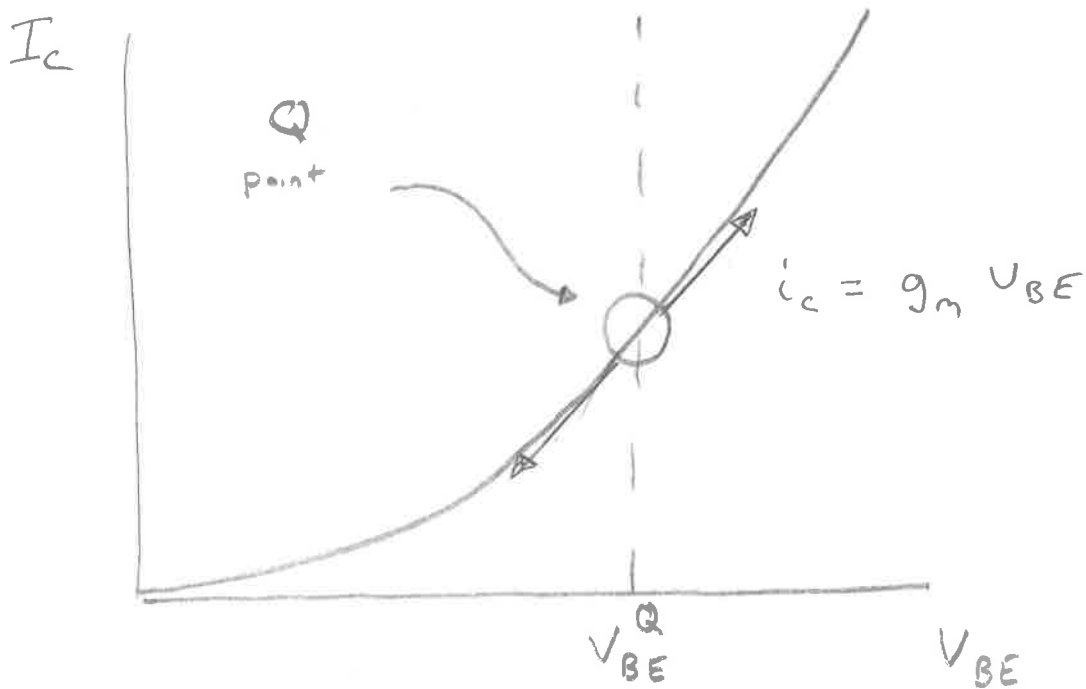

So after determining Q-point, we can approximate small AC signal as linear relationship between i_c and v_{BE}

$$i_c = g_m v_{BE} \quad [g_m] = \left[\frac{1}{R} \right]$$

g_m is called "trans conductance":

$$g_m \equiv \left. \frac{d I_C}{d V_{BE}} \right|_Q$$

Trans conductance

In active region

$$I_c = I_s(T) \left(\exp\left(\frac{V_{BE}}{n V_T}\right) - 1 \right) \\ \sim I_s \exp\left(\frac{V_{BE}}{n V_T}\right)$$


So

$$g_m \equiv \left. \frac{d I_c}{d V_{BE}} \right|_Q = \frac{1}{n V_T} I_s \exp\left(\frac{V_{BE}}{n V_T}\right) \Big|_Q \\ = \left. \frac{I_c}{n V_T} \right|_Q = \frac{I_c^Q}{n V_T}$$

Trans conductance g_m is "set" by I_c^Q ,


Unlike B , we control I_c^Q to reasonable accuracy, and so g_m is a "good" parameter.

Infinite Gain Problem Resolved

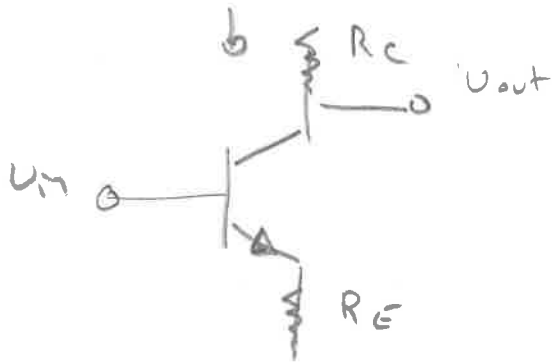

$$G \sim -\frac{R_C}{R_E}$$
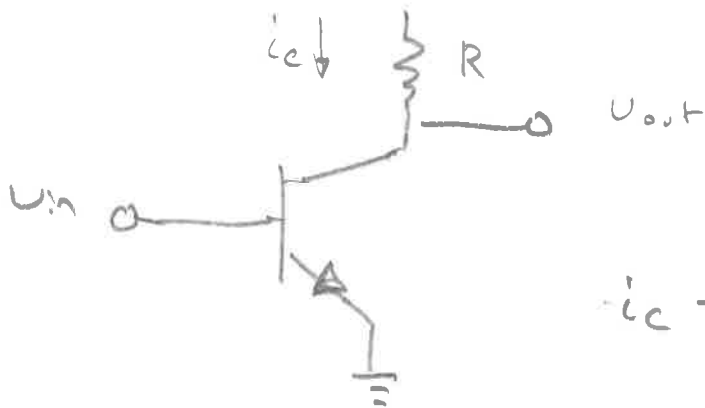
$$G \rightarrow -\infty \quad \text{as } R_E \rightarrow 0$$



$$i_c = g_m V_{in}$$


$$V_{out} \sim - (g_m R) V_{in}$$

$$G \sim -g_m R$$

g_m takes role of $\frac{1}{R_E}$,

As if R_E has $r_E = \frac{1}{g_m}$ in series.

Input Impedance:

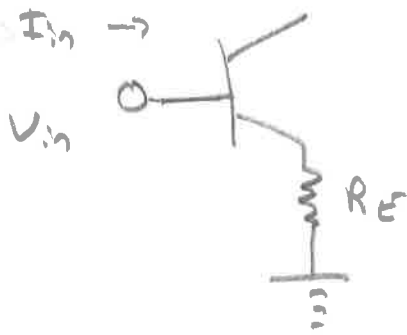

$$R_{in} = \frac{\Delta V_{in}}{\Delta I_{in}} = \beta R_E$$



$$R_{in} = \left. \frac{d V_{in}}{d I_{in}} \right|_Q$$



$$= \left. \frac{d V_{BE}}{d I_B} \right|_Q = \beta \left. \frac{d V_{BE}}{d I_C} \right|_Q$$

$$= \beta \left(\frac{1}{g_m} \right)$$

$$= \beta r_E$$


Again, as if R_E has small resistance

r_E in series...

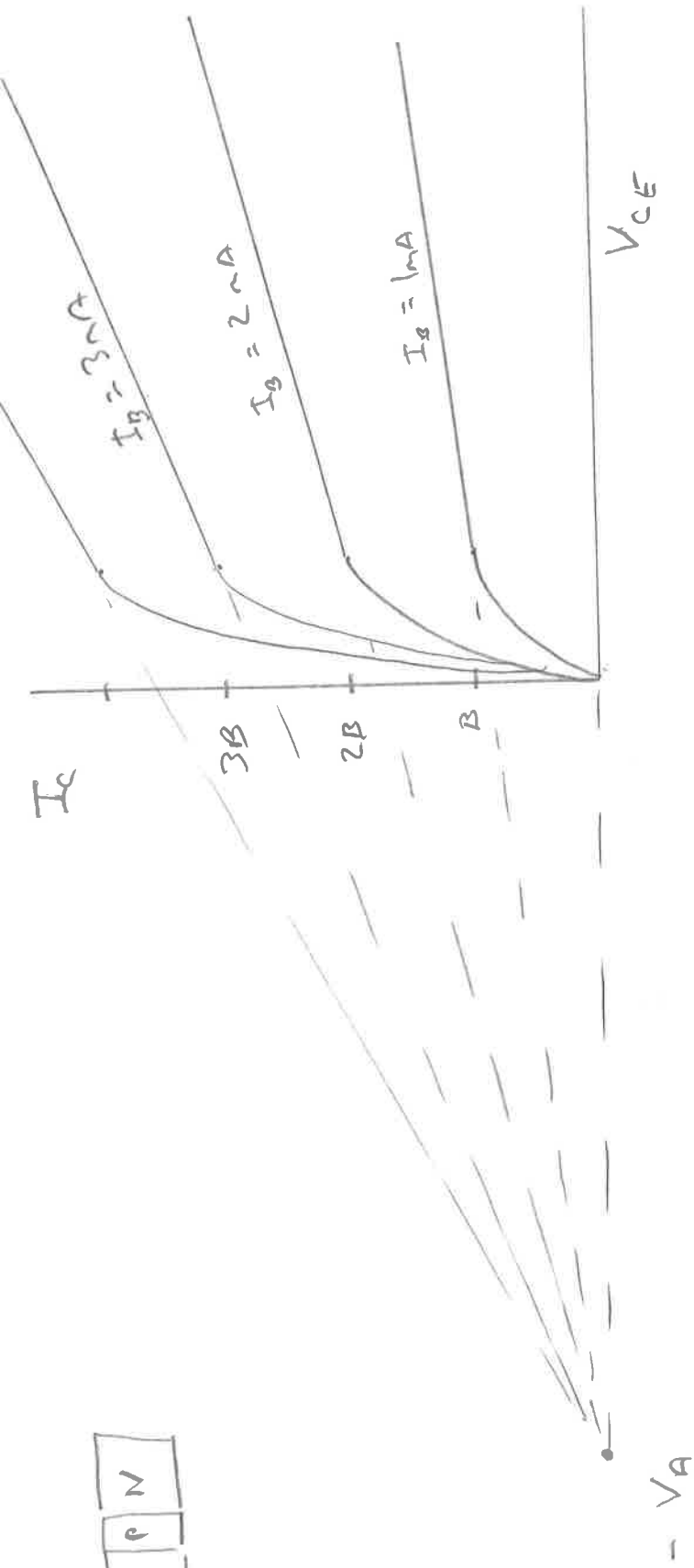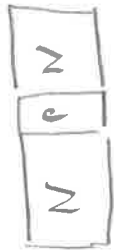

Increasing V_{BC} widens depletion zone, making "thin" P layer effectively much thinner, ... more current
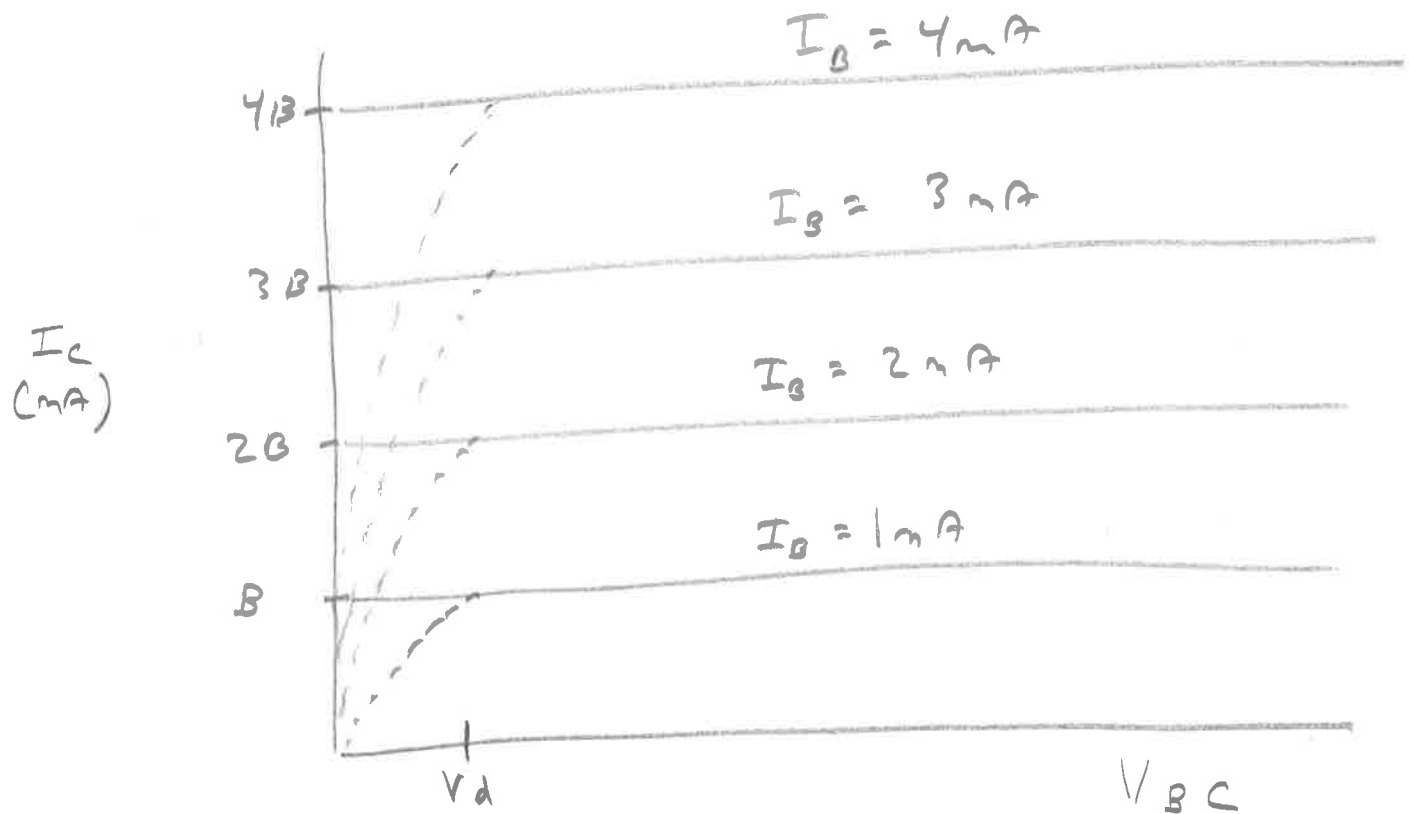
$$R_o = \frac{\Delta V}{\Delta I} = \frac{V_A + V_{CE}^Q}{I_C^Q}$$



Transistor "B" Model,



Recalls in active region,


B-E is forward biased

B-C is reverse-biased ... which is "good" because amplified current is due to minority carriers.

When $V_{BC} \lesssim V_d$, B-C is no longer reverse biased, becoming forward biased ... halts minority carriers ... current I_C goes to zero!

Hybrid- π Model

Small change v_{be} from Q-point:

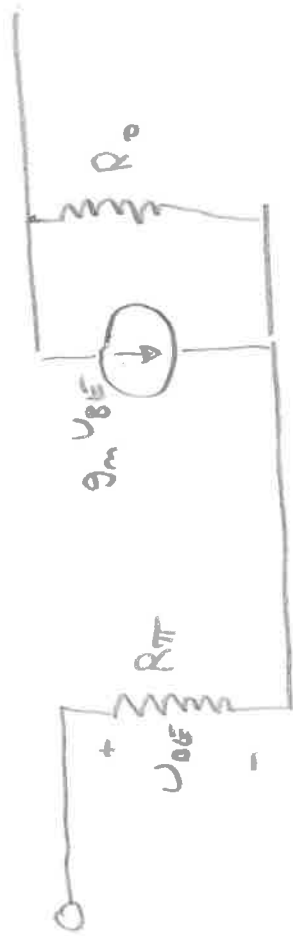

$$\frac{I_c}{V_T}$$

$$\frac{1}{r_e} = g_m = \frac{dI_c}{dV_{BE}} \bigg|_Q$$

$$R_{\pi} = \beta r_e$$

$$R_o = \frac{V_A + V_{CE}}{I_c}$$

Hybrid π Example


Follower

Total

$$V_{out}^Q = \frac{1}{2} V_{CC}$$

$$R_1 || R_2 \ll \beta R_E$$

$$\beta = 100$$

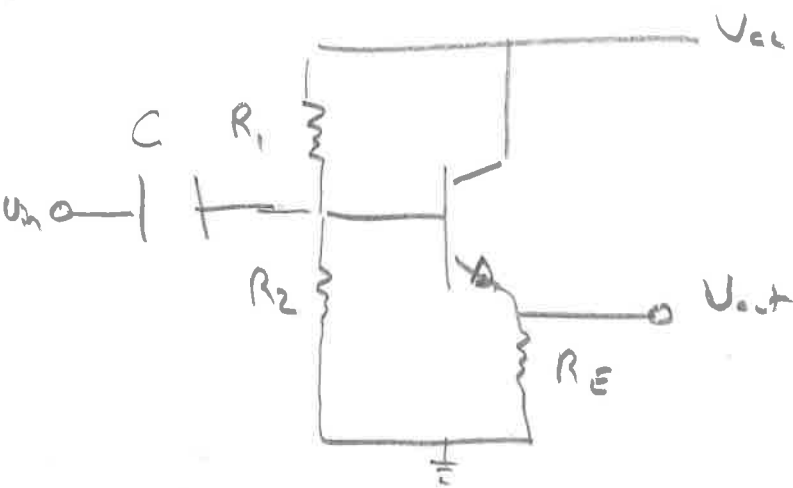



$$I_C^Q = \frac{1}{2} V_{CC} / R_E \quad \checkmark$$

$$g_m = \frac{I_C^Q}{n V_T} \quad \checkmark$$

$$R_\pi = \beta \frac{1}{g_m} \quad \checkmark$$
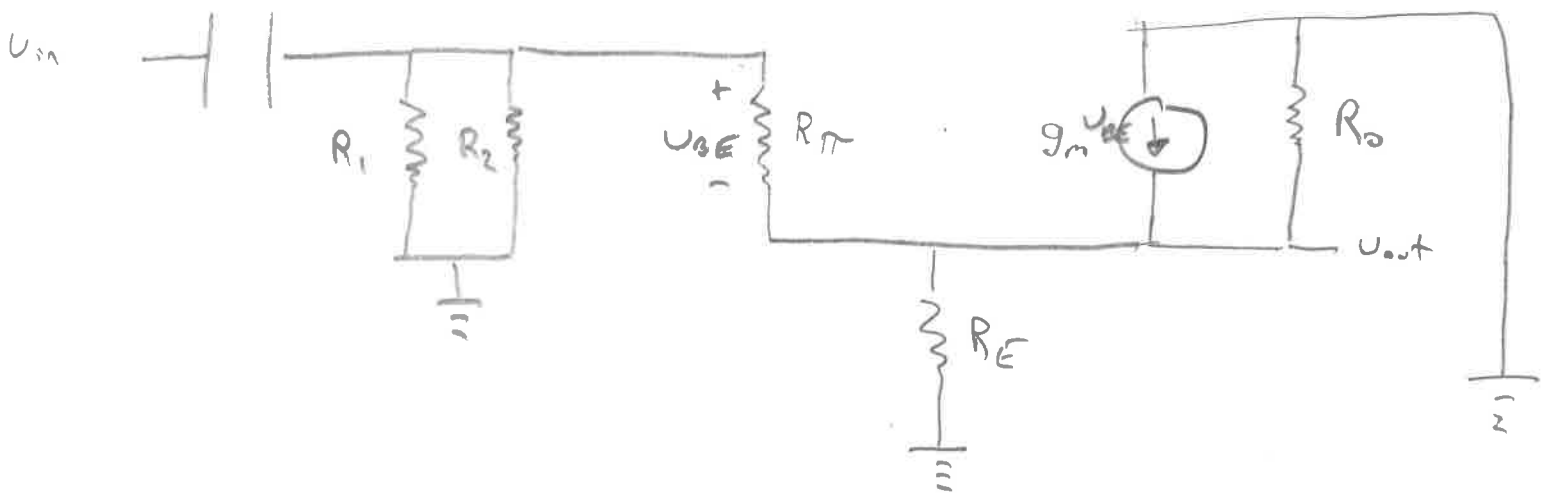
$$R_o = \frac{V_A + \frac{1}{2} V_{CC}}{I_C^Q} \quad \checkmark$$



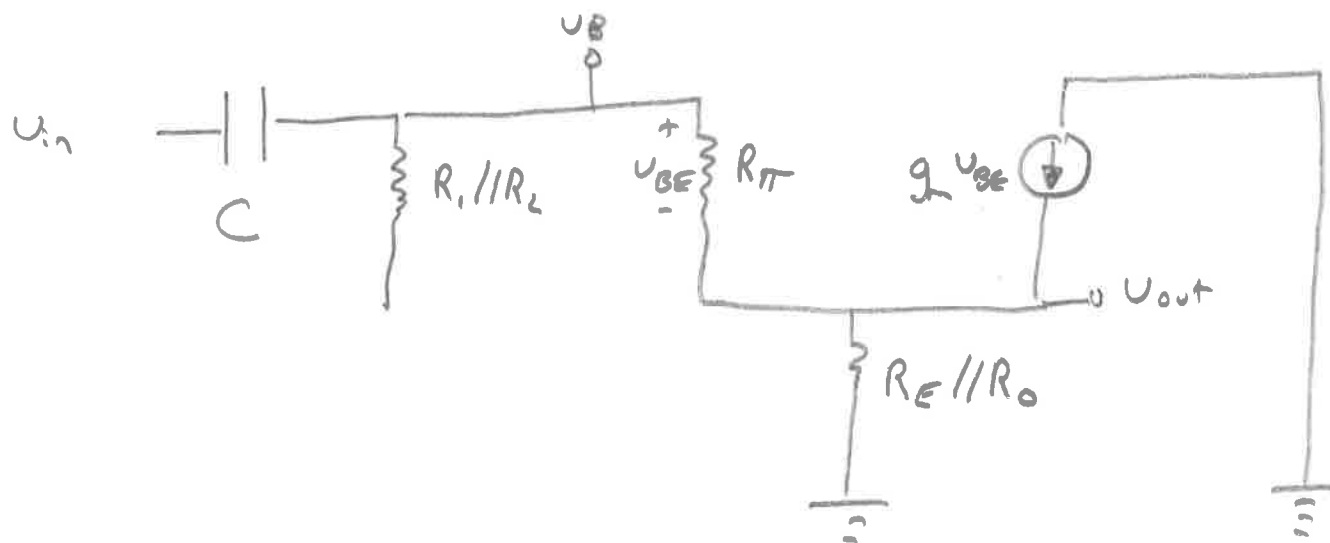

$$U_{out} = (g_m U_{BE}) R_E // R_O$$

$$U_{BE} = U_B - U_{out}$$

$$U_{out} = g_m (U_B - U_{out}) R_E // R_O$$

$$U_{out} (1 + g_m (R_E // R_O)) = g_m R_E // R_O U_B$$

$$U_{out} = \left(\frac{g_m R_E // R_O}{1 + g_m R_E // R_O} \right) U_B$$

$$U_{out} = \left(\frac{A}{1 + A} \right) U_B \quad (\sim U_B)$$

By design, $R_1 // R_2 \ll (R_{\pi} + \beta R_E // R_o)$

So:

$$U_B = \frac{R_1 // R_2}{\frac{1}{\omega C} + R_1 // R_2}$$

$$= \frac{1}{1 + j \frac{\omega_0}{\omega}}$$

$$\omega_0 = \frac{1}{C \cdot (R_1 // R_2)}$$

$$U_{out} = \left(\frac{1}{1 + j \frac{\omega_0}{\omega}} \right) \left(\frac{A}{1 + A} \right) U_{in}$$


$$\rightarrow 1$$

$\Rightarrow C \rightarrow \infty$

$$\rightarrow 1$$

$\Rightarrow A \rightarrow \infty$

Amplifier

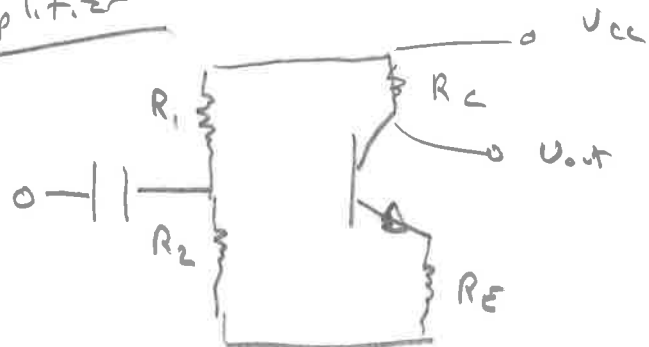

To Id:

$$R_o \rightarrow \infty$$

$$C \rightarrow \infty$$

$$U_{out}^Q = \frac{1}{2} V_{cc}$$



$$\beta = 100$$

$$R_1, R_2 \ll \beta R_E$$

$$I_c^Q = \frac{\frac{1}{2} V_{cc}}{R_c}$$

$$g_m = \frac{I_c^Q}{n V_T}$$

$$R_\pi = \beta \frac{1}{g_m}$$

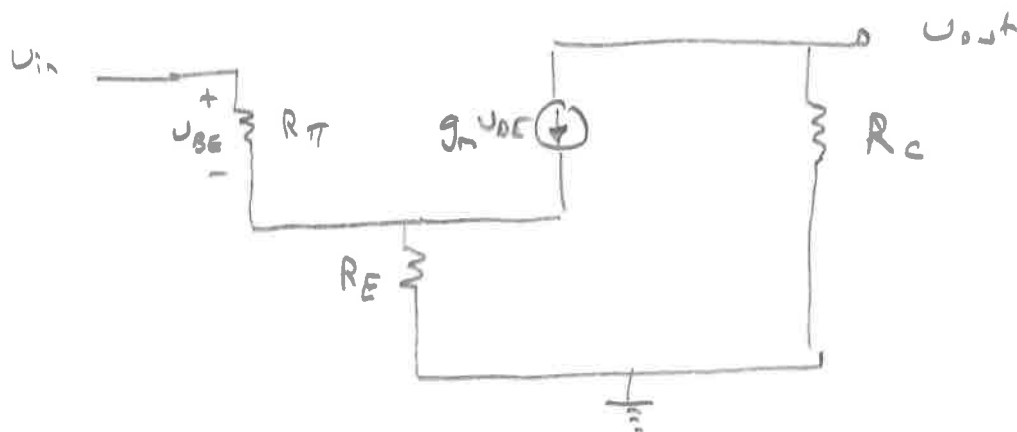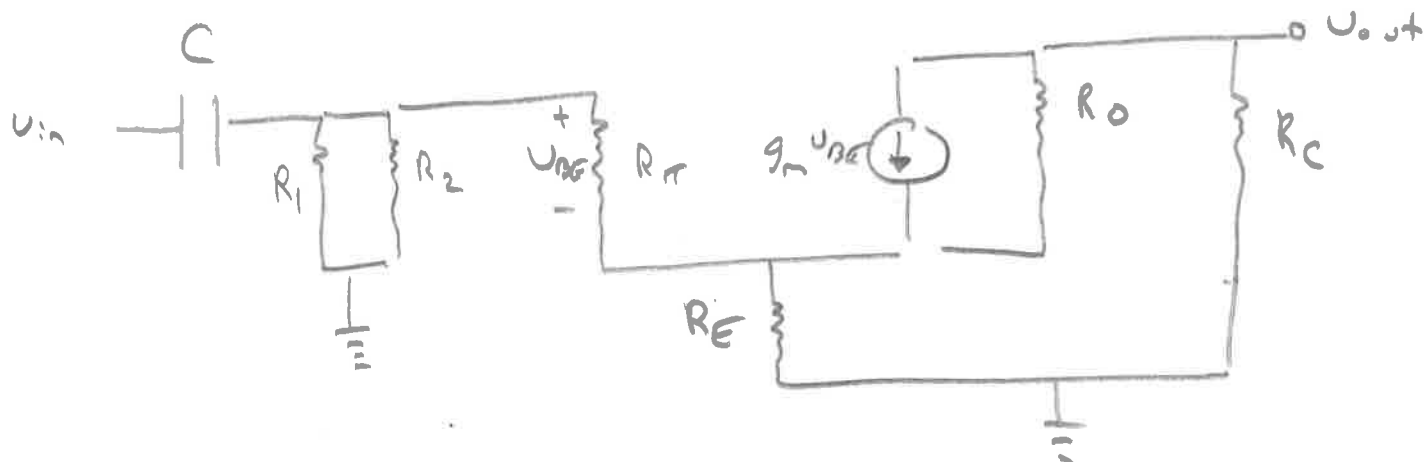

$$U_{out} = -R_c g_m U_{BE}$$

$$U_{BE} = U_B - U_E$$

$$= U_{in} - U_E$$

$$= U_{in} - (R_E g_m) U_{BE}$$

$$U_{BE} = \frac{U_{in}}{1 + R_E g_m} \quad (U_{BE} \rightarrow 0!)$$

$$U_{out} = -R_c g_m \left(\frac{U_{in}}{1 + R_E g_m} \right)$$

$$= -\frac{R_c}{R_E} \left(\frac{g_m R_E}{1 + g_m R_E} \right) U_{in}$$

$$U_{out} = -\frac{R_c}{R_E} \left(\frac{A}{1 + A} \right) U_{in}$$

↑

→ 1

as $\infty \rightarrow \infty$