 


Microprocessors

and

Assembly

Little Man Computer



Input → user input

Output → e.g. to screen

Acc → accumulator (for addition + subtraction)

Program Counter → starts at zero, increments prior to each instruction, but may be overwritten by the instruction.
(Next instruction taken from address in PC)

Mailboxes: Stores data and program.

LMC Instruction Set

1XX	ADD	Add value in mailbox XX to accumulator
2XX	SUB	Subtract value "
3XX	STA	Store contents of Acc into mailbox XX.
5XX	LOA	Load contents of XX into the accumulator
6XX	BRA	Set PC to mailbox XX
7XX	BRZ	Set PC mailbox XX if Acc is zero
8XX	BRP	Set PC mailbox XX if Acc is zero or positive
901	INP	load input to Acc
902	OUT	Send Acc to Out
000	COR	Coffee Break

Example Multiplier

00	901	INP	input "a"
01	350	STA A	store "a"
02	901	INP	input "a"
03	351	STA B	store "b"
04	711	LOOP DRZ DONE	
05	552	LDA SUM	
06	150	ADD A	
07	352	STA SUM	
08	551	LDA B	
09	253	SUB ONE	
10	604	BRA LOOP	
11	552	DONE LDA SUM	
12	902	OUT	
13	000	COB	
---	---		
50	---	A DAT	
51	---	B DAT	
52	0	SUM DAT	0
53	1	ONE DAT	1

* HW LMZ to integer divide A/B

6	3	→	2
5	3	→	1
7	3	→	2

Compu ter

A > B

Example : Adder $(A+B)$

901	INP
350	STA FIRST
901	INP
150	ADD FIRST
902	OUT
000	COB
	FIRST DAT

Example Subtractor $(A-B)$

901	INP
350	STA FIRST
901	INP
351	STA SECOND
550	LDA FIRST
251	SUB SECOND
902	OUT
000	COB

AND



AB

<u>A</u>	<u>B</u>	<u>O</u>
0	0	0
0	1	0
1	0	0
1	1	1


NAND



\overline{AB}

0	0	1
0	1	1
1	0	1
1	1	0

OR

 

$A + B$


0	0	0
0	1	1
1	0	1
1	1	1

NOR




0	0	1
0	1	0
1	0	0
1	1	0

XOR

 

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

XNOR

 


0	0	1
0	1	0
1	0	0
1	1	0 1

For the minimalists...


NAND and NOR are each functionally complete... you can construct all logic from enough of either,

Man tricks, invert:


Ignore:

 

AND:

 


OR:

 


Half Adder

0	1	1	1
0	0	1	1
0	0	0	1
00	0	10	11

 


Full Adder

 

"Trick" to understanding is that
 $1 + 1 + (1) = 11 = 3$ is biggest number possible
 $(\Leftrightarrow Z = 1 \Rightarrow x = 0)$

Buffer

 

A	B
0	0
1	1

Inverter



A	B
1	0
0	1

Buffer from Inverter



Inverter from Buffer




Tri-State Buffer




A	C	Q
0	0	Z
1	0	Z
0	1	0
1	1	1

Multiplexing

 


1-bit Mux

 

A	Q
0	I_0
1	I_1

1-bit Demux

 

A	O_0	O_1
0	I	0
1	0	I

MUX, DEMUX, Tri-State Buffer

MUX


A	B	S	O
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

DEMUX

A	S	C	D
0	0	0	0
1	0	1	0
0	1	0	0
1	1	0	1


S	O
0	A
1	B

S	C	D
0	in	0
1	0	in

 

S	O
0	Z
1	in



De coder

 


3-bit:




A_0	A_1	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

  

2^n inputs

 

A	C
0	I_0
1	I_1
2	I_2
\vdots	\vdots
(2^n-1)	$I_{(2^n-1)}$

 

A	O_0	O_1	O_2, \dots, O_{2^n-1}
0	H	0	0
1	0	H	0
2	0	0	H
\vdots	\vdots	\vdots	\vdots
2^n-1	0	0	H

Multiplexer

Number of inputs: N_i


Number of outputs: $N_o \geq 1$

Number of address bits: N_A

$$2^{N_A} = N_i / N_o$$



eg.

4:1

 

$$2^2 = 4/1$$

4:2

  


$$2^1 = 4/2$$

Width:


Often, we might want to associate m -bits with a particular address,

(Accumulator in LMC requires 10 bits ≤ 1024)
and Mailboxes

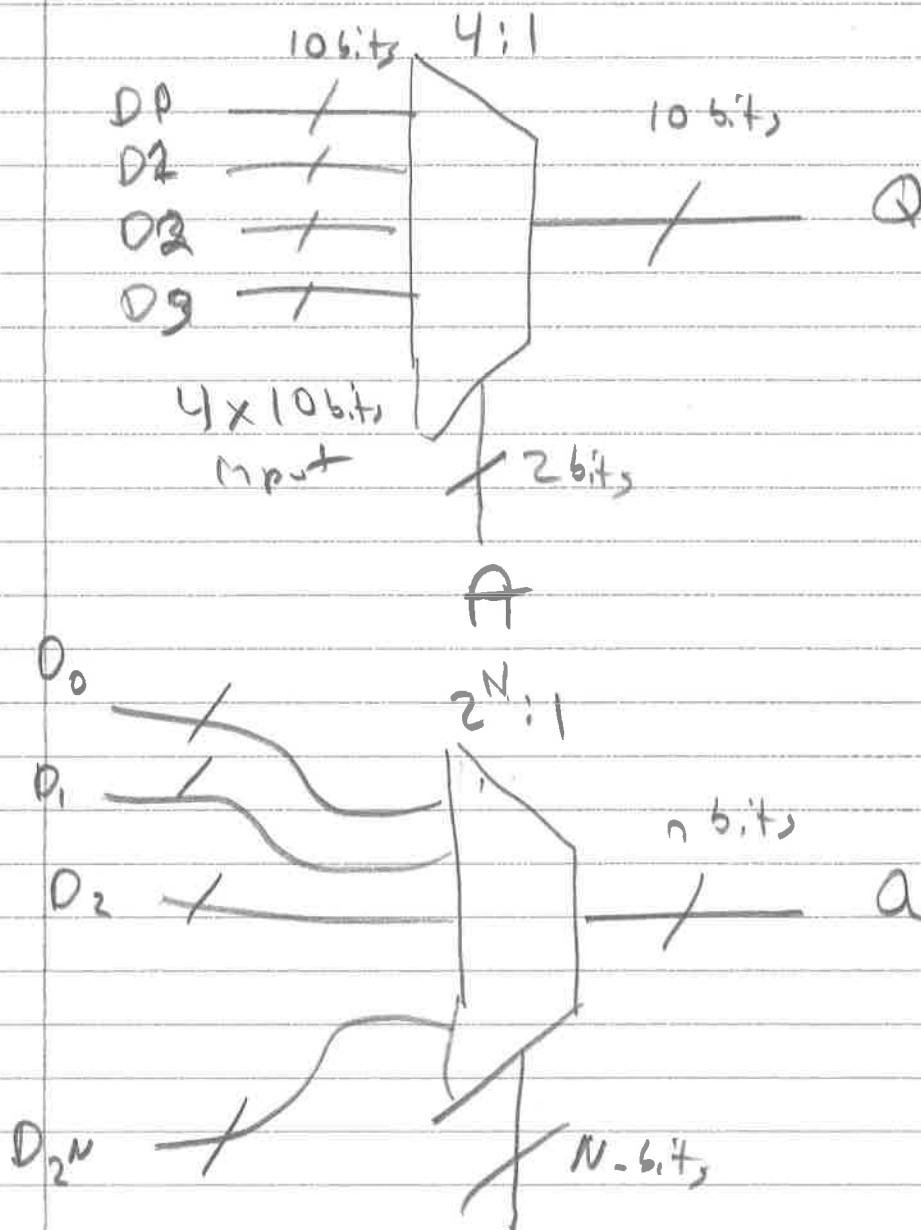→ 10 bits at address $0x3$
10 bits at address $0x2$



Mux \leftrightarrow Generic Logic

 


a	b	Q
0	0	A
0	1	B
1	0	C
1	1	D

Configurable Logic!

Set to
what we
want

RS latch

 


RS both high $Q=0 \quad \bar{Q}=1$ stable
 $Q=1 \quad \bar{Q}=0$ stable
 ($Q=\bar{Q}$ not stable)

$R=1 \quad S=0$, $S=0$ forces $\bar{Q}=1$ (not)
 $\bar{Q}=1$ and $R=1$ forces $Q=0$

$R=0 \quad S=1$ $R=0$ forces $Q=1$
 $Q=1$ and $S=1$ forces $\bar{Q}=0$

RS both 0 $\rightarrow Q=\bar{Q}=0$ invalid state

D-type Flip-Flop

 


$$E = 0 \Rightarrow R = S = 1 \Rightarrow Q \text{ constant}$$

$$E = 1 \Rightarrow R = \bar{D} \quad S = D \Rightarrow Q = D \quad \bar{Q} = \bar{D}$$

Note: $R = S = 0$ is not possible
due to NOT at (*)


(Btw: that $Q = \neg D$ for NAND construction is 5 NANDs per D ff)

Symbol

 



0 3 2 0

Any 0-ff can be set with W, or read

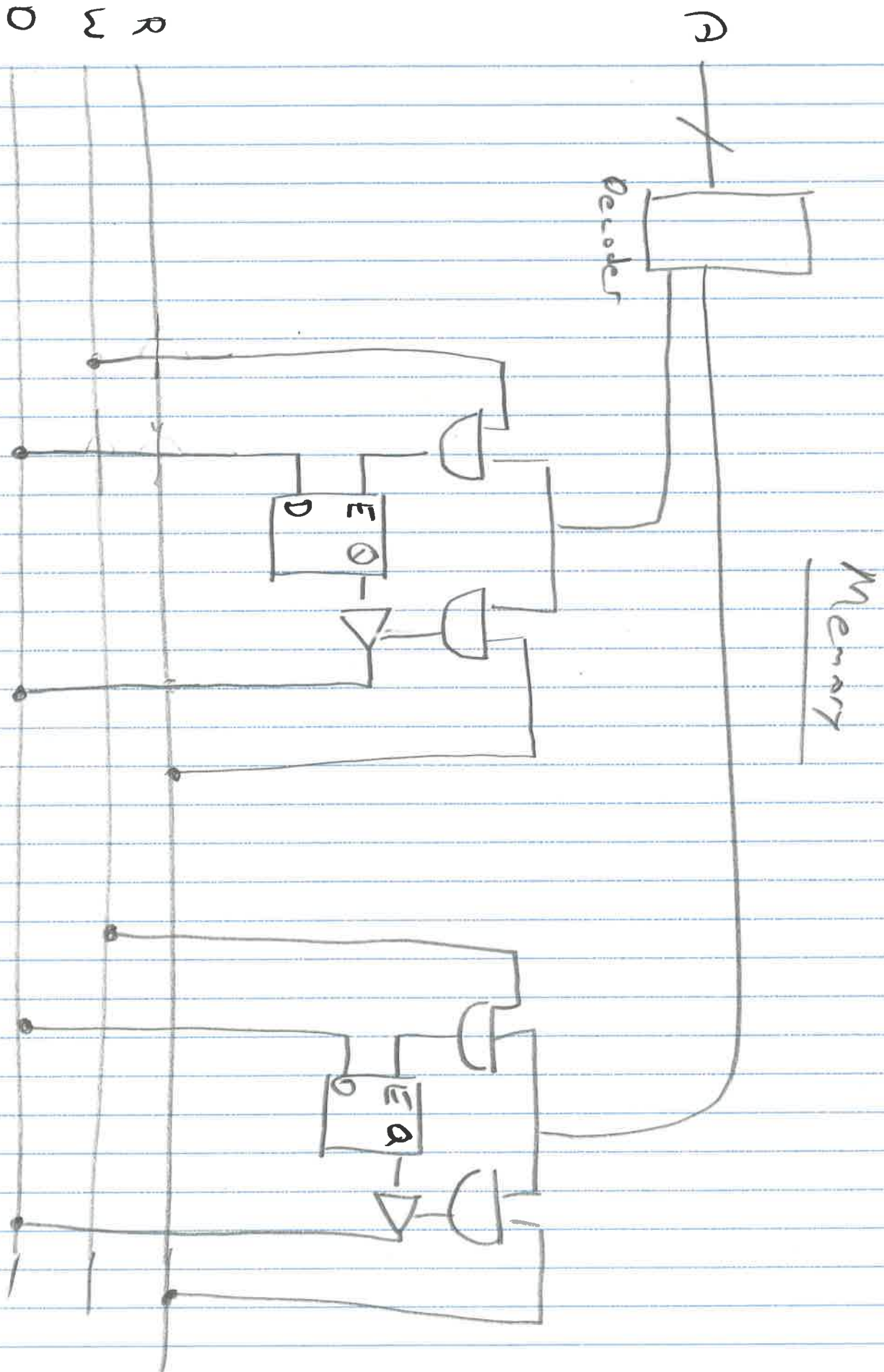

Memory Symbol

 


 


1-bit asynchronous, NAND computer

COF X
 STF X
 WFN X

C6	0	1	0	0	(1)
C5	1	0	1	0	(2)
C4	0	0	0	1	
C3	0	0	1	0	
C2	0	1	0	0	
C1	1	0	0	1	
E	X	X	X	1	

Edge - Triggered D - Flip Flop

  



* Won't see new value until after falling edge, i.e.,

Next Clock Cycle

Symbols




Synchronous Accumulator

  


As long as we feed B $\frac{1}{2}$ cycle ahead, accumulator handles one new input per cycle.

Register

 

CPU: Central Processing Unit

 

By now understood workings of
ALU for each assembly command
w a fixed set of steps:

- moving data into registers
- digital synchronous logic

all driven by control signals (C_i)

Fixed Program Computer

Early computers applied a fixed set of steps to variable input data

C_1	0	0	1
C_2	0	1	0
\vdots			
C_N	0	0	1

} Known by Designer

R_1	?	?	?
R_2	?	?	?
R_3	?	?	?

} Computed at run time.

First computers had a hard-wired CU, no easy way to change it.

Turing / Von Neumann / Zuse

developed idea to

Store Instructions in Memory,

Incredibly powerful:

→ General Purpose Computer

→ New Algorithms Possible,
based on recursion (GOTO)
and branching (conditional)

Control Unit


- fetch instruction word from memory at current address in program counter (IR)
- increment program counter (PC++)
- IR contains both OP code and address.
- For each operation, there are a fixed set of steps that take place.

CLK 

Counter	1	2	3	4	5	6	0	1	2	3	4	5
OP code	0	0	0	0	0	0	3	3	3	3	3	3
C1	1	1	0	0	1	1	1	1	0	0	1	0
C2	0	0	1	1	0	0	1	1	0	1	1	1
C3	1	0	1	0	1	1	1	1	0	1	1	1
C4	1	1	1	0	1	1	1	1	0	0	1	1

Key point: the control operations can, eg. change program counter, providing flow control, and conditional execution.

CU M ROM

 

That's really it...

except for literally Trillions
of \$ invested to improve
performance!

Microsoft	—	\$500 B
Apple	—	\$700 B
Google	—	\$534 B
Amazon	—	\$373 B

Python:

- very different (complementary) to C/C++
- dynamic type checking
(no int x = 2)
- automatic memory management
(no new/delete, no pointers)
- readability → indentation used instead of {}

Great resource at:

www.python.org

For example, tutorials:

<http://developers.google.com/edu/python/>

Intro

Strings (in use)

Lists

(numpy, matplotlib)

Interpreter on Command Line

→ Show Calculator in interactive mode

→ print 'hello world'

As script.py

Subroutines:

def f(x, y)

Conditionals:

if / elif / else
while / break

For:

for x in [1, 2, 3]

for y in range(10)

Lists:


x = []

x.append(5)

x.append(2)


print len(x)

Radioactive Decay

 

After Hydrogen, need a mix of p/n to reach stable nuclei...


→ n are unstable (outside of nuclei)

 

beta decay...

Too many neutrons, beta decay! (B^-)

 
→ p are stable outside nuclei, but too many, Coulomb forces dominates



Too many protons, Electron capture

(B^+)

Too many protons in neutrons,

 

which is really just special case instance of nuclear fission:




Other (rarer) decay processes:

- \rightarrow proton emission
- \rightarrow neutron emission

Excess p or n simply ejected,


- \rightarrow neutron emission is common as result of fission (extra neutrons)
- \rightarrow proton emission rare, but interesting experimentally (quantum tunneling)

z

 


z

z

 

(27) Co 60

 

Radio-active Decay

→ Totally random which (when) particular nucleus decays. (unlike humans!)

→ Equally probable that any nucleus will decay at any time (unlike humans)
(Nuclei don't get old and die!)

$$\Rightarrow \frac{dN}{dt} = -kN$$

$$N(t) = N_0 \exp(-kt)$$

$$N(0) = N_0$$

$$N(\tau_{1/2}) = N_0 / 2$$

$$N(t) = N_0 \exp(-kt)$$

$$N(\tau_{1/2}) = N_0 \exp(-k\tau_{1/2}) = N_0 / 2$$

$$\Rightarrow 2 = \exp(k\tau_{1/2})$$

$$\log 2 = k\tau_{1/2}$$

$$k = \frac{1}{\log 2 \tau_{1/2}}$$

(Fix)

$$N(t) = N_0 \exp\left(\frac{-t}{\log(2) \tau_{1/2}}\right)$$

Passage of charged particles:



As charged particles move through medium, loose energy in a number of ways:

→ Ionize atoms by liberating electrons

→ Multiple Scattering, from nuclei

→ For light particles acceleration causes radiation (bremsstrahlung)


Photons

Energy ↓


(a) Photo-electric effect


(b) Compton Scattering

(c) Pair production

 

Cascades:

 

 

As voltage increases:


- (1) Collect ionized charge
- (2) Voltage accelerates electrons to high enough energy to cause additional collisions, liberating additional electrons
- (3) Saturation

From Plot

$$V = \frac{Q}{C} = \frac{1.6 \times 10^{-19} \text{ C} \times 10^{10}}{10^{-9} \text{ F}} = 1.6 \text{ V}$$

⇒ Proportional Chambers require tiny electrons, small

 Often, nuclear decays result in a nucleus that is not in its ground state. It reaches ground state by γ emission.



$$^{137}_{55}\text{Cs} : 136.40709 \text{ amu}$$

$$^{137}_{56}\text{Ba} : 136.90582 \text{ amu}$$

$$\Delta m = 0.00127 \text{ amu}$$

$$(1 \text{ amu}) c^2 = 931 \times 10^6 \text{ eV}$$

$$\Delta m c^2 \sim 1.18 \text{ MeV}$$

Geiger Counter

